

Code: AE54/AC54/AT54/AE104
Subject: LINEAR ICs & DIGITAL ELECTRONICS

AMIETE – ET/CS/IT (Current & New Scheme)

Time: 3 Hours

JUNE 2018

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- **Question 1 is compulsory and carries 20 marks. Answer to Q. 1 must be written in the space provided for it in the answer book supplied and nowhere else.**
- **The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.**
- **Out of the remaining EIGHT Questions answer any FIVE Questions, selecting at least TWO questions from each part. Each question carries 16 marks.**
- **Any required data not explicitly given, may be suitably assumed and stated.**

Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. An ideal op-amp is an ideal
 (A) voltage controlled current source (B) voltage controlled voltage source
 (C) current controlled current source (D) current controlled voltage source
- b. If the differential voltage gain and common mode voltage gain of a differential amplifier are 48 dB and 2 dB respectively, then its common mode rejection ratio is
 (A) 23 dB (B) 25 db
 (C) 46 dB (D) 50 dB
- c. For a 3 bit R-2R ladder DAC, how many values of resistors are required?
 (A) 2 (B) 3
 (C) 8 (D) 1
- d. A schmitt trigger exhibits
 (A) hysteresis (B) amplification
 (C) oscillation (D) none of these
- e. A 555 timer is an IC that can be used to produce
 (A) square waves (B) triangular waves
 (C) sweep waves (D) sine waves
- f. To derive the compliment of a function, we need to
 (A) take dual of a function (B) complement each literal
 (C) both (A) and (B) (D) none of these
- g. $x \oplus y$ means
 (A) x but not y (B) y but not x
 (C) x or y but not both (D) neither x nor y but both


Code: AE54/AC54/AT54/AE104
Subject: LINEAR ICs & DIGITAL ELECTRONICS

- h. The number of input variables which a NOT gate can have is
 (A) 1 (B) 2
 (C) 3 (D) Any number
- i. The flip-flop which operates in synchronism with external clock pulse is known as ____ flip- flop.
 (A) synchronous (B) asynchronous
 (C) either of the above (D) none of the above
- j. The number of select lines required for 32:1 multiplexer are -----
 (A) 4 (B) 32
 (C) 5 (D) 8

PART A (Linear ICs)

Answer at least TWO questions. Each question carries 16 marks.

 - Q.2** a. Suggest modification in the given circuit of Opamp to make it
 (i) inverting (ii) non inverting. (6)



- b. Discuss the terminal properties of an ideal operational amplifier. (8)
- c. Show diagrammatically classification of integrated circuits (IC). (2)
- Q.3** a. Define slew rate. What causes the slew rate? (4)
- b. Draw and explain the open loop magnitude characteristics for an operational amplifier with single break frequency. (4)
- c. Draw and explain current to voltage converter circuit using op-amp. (8)
- Q.4** a. What is an integrator? Derive the formula for its output voltage. Explain its working with neat and clean waveform in case of square wave input. (10)
- b. Draw and explain Schmitt trigger or squaring circuit. (6)
- Q.5** a. Draw and explain 3 bit weighted resistor DAC. (8)
- b. Draw and explain functional diagram of 555 timer IC. (8)

Code: AE54/AC54/AT54/AE104
Subject: LINEAR ICs & DIGITAL ELECTRONICS

PART B (Digital Electronics)
Answer at least TWO questions. Each question carries 16 marks.

- Q.6** a. (i) Find decimal equivalent of the binary number $(1\ 1\ 1\ 1\ 1)_2$.
(ii) What do you mean by a memory device? What are the two types of memory devices? (4)
- b. Make the following conversions. (Steps are necessary)
- (i) $(111011)_2$ to octal (ii) $(614)_8$ to decimal
(iii) $(496)_{10}$ to BCD (6)
- c. What do you mean by serial and parallel transmission of digital signals? What advantage does parallel have over serial in the transmission of digital signals? (3)
- d. What do you mean by bit, byte and nibble? (3)
- Q.7** a. Draw using NAND gate $F = A B + ABC + ABCD + ABCD$ (5)
- b. Simplify the following:
(i) $A + AB + A\bar{B}$ (ii) $(A+B)BC + A$ (6)
- c. Minimize the logic function $F(A,B,C) = \sum m(0,4) + d(7,2,1)$ using K-maps. (5)
- Q.8** a. What is a full adder? Draw truth-table and logic diagram of full adder. (8)
- b. Add the binary numbers $01101010+00001000+10000001+11111111$ (3)
- c. What is a demultiplexer? How many select lines will be required for an 1:8 demultiplexer? Draw diagram of 1:4 demultiplexer. (5)
- Q.9** a. Describe NAND gate as a latch. (8)
- b. Explain the working of 3 bit synchronous counter using J-K F-F and corresponding waveforms. (8)