

GATE Electronics and Communication Engineering

Sample Paper – 3

Duration: 128 Minutes

Maximum Marks: 72


Instructions

- This paper contains **46 questions** covering the core **Electronics and Communication Engineering** subject of the GATE paper conducted by the IITs and IISc (General Aptitude and Engineering Mathematics are provided as separate papers).
- **Q1–Q20 carry 1 mark each and Q21–Q46 carry 2 marks each**, for a total of **72 marks**.
- Each question carries **negative marking of one-third of its allotted marks**: a wrong 1-mark question costs **0.33** and a wrong 2-mark question costs **0.67**. Unattempted questions carry no penalty.
- Every question here is a single-correct **MCQ**. The real GATE paper also has Multiple Select (MSQ) and Numerical Answer Type (NAT) questions, and **those carry no negative marking**.
- Attempt this paper in one timed sitting of about **128 minutes**, the share this core subject earns at GATE's overall pace of 180 minutes for 65 questions. Unless stated otherwise take $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ for silicon, thermal voltage $V_T = 25 \text{ mV}$ at room temperature, $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$, $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$ and $c = 3 \times 10^8 \text{ m/s}$.

Networks and Circuit Analysis

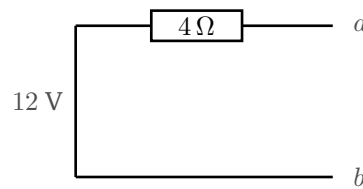- Q1.** A one-port network reduces to an ideal 12 V voltage source in series with a 4Ω resistor at terminals $a-b$, as shown. The Norton equivalent (short-circuit) current seen at $a-b$ is: [1 mark]






- (A) 48 A
- (B) 3 A
- (C) 0.33 A
- (D) 12 A

Q2. To find the Thevenin resistance at terminals $a-b$ of a network, its independent voltage source is replaced by a short circuit. The remaining resistors are a $6\ \Omega$ in series with the parallel combination of two $12\ \Omega$ resistors. The Thevenin resistance R_{th} is: [1 mark]

- (A) $6\ \Omega$
- (B) $18\ \Omega$
- (C) $24\ \Omega$
- (D) $12\ \Omega$

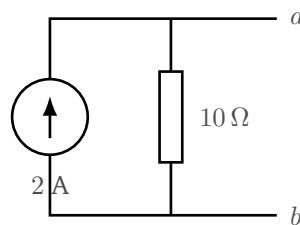Q3. A practical source is modelled as a Norton equivalent of current $I_N = 2\text{ A}$ in parallel with $R_N = 10\ \Omega$, as shown. Its Thevenin equivalent open-circuit voltage $V_{th} = I_N R_N$ is: [1 mark]




- (A) 20 V
- (B) 5 V
- (C) 0.2 V
- (D) 40 V



Q4. In a resistive network the open-circuit (Thevenin) voltage at terminals $a-b$ equals the voltage across the $6\text{ k}\Omega$ resistor of a two-resistor divider made of $2\text{ k}\Omega$ and $6\text{ k}\Omega$ fed by a 16 V source. That Thevenin voltage is:[1 mark]

- (A) 4 V
- (B) 16 V
- (C) 12 V
- (D) 8 V

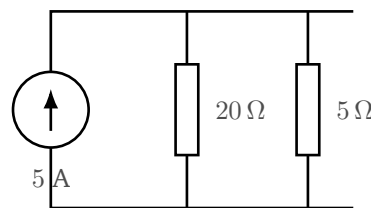Q5. An ideal current source of 5 A is connected in parallel with a $20\text{ }\Omega$ resistor and a $5\text{ }\Omega$ load, as shown. By the current-divider rule the current flowing through the $5\text{ }\Omega$ load is: [1 mark]



- (A) 5 A
- (B) 1 A
- (C) 2 A
- (D) 4 A


Q6. Two capacitors of $4\text{ }\mu\text{F}$ and $12\text{ }\mu\text{F}$ are connected in series between two nodes. The equivalent capacitance of the combination is: [1 mark]

- (A) $16\text{ }\mu\text{F}$
- (B) $3\text{ }\mu\text{F}$
- (C) $8\text{ }\mu\text{F}$
- (D) $48\text{ }\mu\text{F}$


Electronic Devices



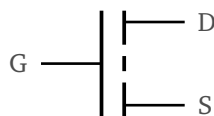- Q7.** An n -channel enhancement MOSFET has threshold voltage $V_t = 1$ V. It is biased with $V_{GS} = 3$ V and $V_{DS} = 0.5$ V, as shown. Comparing V_{DS} with the overdrive $V_{GS} - V_t$, the transistor is operating in the: [1 mark]



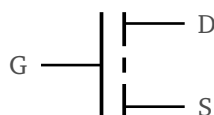- (A) triode (linear) region
 - (B) saturation region
 - (C) cut-off region
 - (D) breakdown region
- Q8.** An n -channel enhancement MOSFET has threshold voltage $V_t = 1$ V. Its gate-to-source voltage is set to $V_{GS} = 0.6$ V while a small drain-to-source voltage is applied. The transistor is operating in the: [1 mark]
- (A) cut-off region
 - (B) saturation region
 - (C) triode (linear) region
 - (D) breakdown region
- Q9.** An n -channel enhancement MOSFET has threshold voltage $V_t = 0.8$ V. It is biased with $V_{GS} = 2.8$ V and $V_{DS} = 3$ V, as shown. Comparing V_{DS} with the overdrive $V_{GS} - V_t$, the transistor is operating in the: [1 mark]



- (A) cut-off region
- (B) triode (linear) region
- (C) saturation region
- (D) breakdown region




- Q10.** An n -channel MOSFET with process transconductance $k_n = 2 \text{ mA/V}^2$ and threshold $V_t = 0.5 \text{ V}$ is biased in saturation with $V_{GS} = 1.5 \text{ V}$. Using $I_D = \frac{1}{2}k_n(V_{GS} - V_t)^2$, the drain current is: [1 mark]
- (A) 1 mA
(B) 2 mA
(C) 0.5 mA
(D) 4 mA
- Q11.** The MOSFET of the previous style operates in saturation with $k_n = 2 \text{ mA/V}^2$ and quiescent drain current $I_D = 1 \text{ mA}$. Its small-signal transconductance $g_m = \sqrt{2k_n I_D}$ is: [1 mark]
- (A) 1 mA/V
(B) 4 mA/V
(C) 2 mA/V
(D) 0.5 mA/V

Analog Circuits

- Q12.** An ideal op-amp inverting amplifier has input resistor $R_1 = 2 \text{ k}\Omega$ and feedback resistor $R_f = 8 \text{ k}\Omega$. The magnitude of the closed-loop voltage gain $|V_o/V_i| = R_f/R_1$ is: [1 mark]
- (A) 8
(B) 0.25
(C) 4
(D) 10
- Q13.** The ideal-op-amp difference (differential) amplifier shown is balanced with $R_1 = R_2 = 10 \text{ k}\Omega$ and $R_f = R_g = 30 \text{ k}\Omega$, so that $V_o = \frac{R_f}{R_1}(V_2 - V_1)$. With $V_1 = 1 \text{ V}$ applied through R_1 and $V_2 = 2 \text{ V}$ applied through R_2 , the output voltage is: [1 mark]



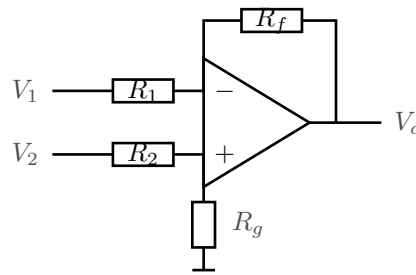

- (A) 7 V
- (B) 3 V
- (C) -3 V
- (D) 10 V

Q14. A differential amplifier has a differential-mode gain $A_d = 100$ and a common-mode gain $A_{cm} = 0.1$. Its common-mode rejection ratio in decibels, $\text{CMRR}_{\text{dB}} = 20 \log_{10}(A_d/A_{cm})$, is: [1 mark]

- (A) 40 dB
- (B) 20 dB
- (C) 60 dB
- (D) 80 dB

Q15. An op-amp has a gain-bandwidth product (unity-gain frequency) of 10 MHz. When it is connected for a closed-loop gain of 50, the resulting -3 dB bandwidth is: [1 mark]


- (A) 10 MHz
- (B) 50 kHz
- (C) 500 kHz
- (D) 200 kHz

Q16. An op-amp has a slew rate of $1 \text{ V}/\mu\text{s}$ and drives a sinusoidal output of peak amplitude 2 V. The full-power bandwidth (maximum frequency before slew-rate limiting), $f = \frac{\text{SR}}{2\pi V_{\text{peak}}}$, is nearest to: [1 mark]




- (A) 159 kHz
- (B) 79.6 kHz
- (C) 500 kHz
- (D) 1 MHz

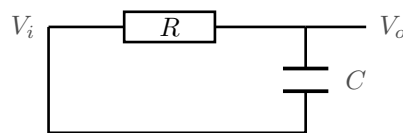Q17. A first-order RC low-pass filter has $R = 1 \text{ k}\Omega$ and $C = 0.1 \text{ }\mu\text{F}$, as shown. Its -3 dB cut-off frequency $f_c = 1/(2\pi RC)$ is nearest to: [1 mark]



- (A) 159 Hz
- (B) 15.9 kHz
- (C) 100 Hz
- (D) 1.59 kHz

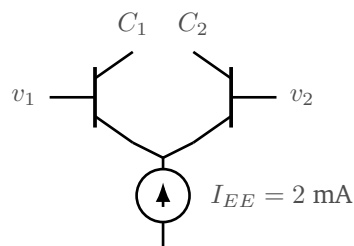Q18. A BJT differential (emitter-coupled) pair is biased by an ideal tail current source $I_{EE} = 2 \text{ mA}$, as shown. Under balanced (zero differential input) conditions the collector current in each transistor is: [1 mark]



- (A) 2 mA
- (B) 1 mA
- (C) 0.5 mA
- (D) 4 mA


Digital Circuits

Q19. The hexadecimal number $(2F)_{16}$ has the decimal (base-10) value: [1 mark]



- (A) 47
(B) 31
(C) 15
(D) 79

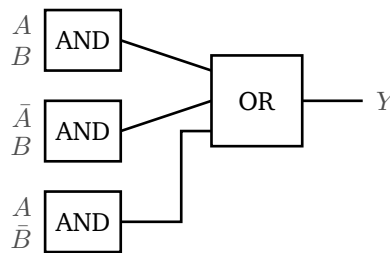Q20. The three-gate combinational network shown realises $Y = AB + \bar{A}B + A\bar{B}$. Applying the rules of Boolean algebra, this simplifies to: [1 mark]



- (A) A
(B) B
(C) AB
(D) $A + B$

Q21. The four-variable function $F(A, B, C, D) = \sum m(0, 1, 2, 3)$ is plotted on the Karnaugh map shown (rows AB , columns CD). The minimal sum-of-products expression for F is: [2 marks]

$AB \backslash CD$	00	01	11	10
00	1	1	1	1
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0


- (A) $\bar{A}\bar{B}$
(B) $\bar{A}\bar{C}$
(C) $\bar{B}\bar{C}$
(D) $\bar{A}B$



- Q22.** The four-variable function $G(A, B, C, D) = \sum m(0, 4, 8, 12)$ is plotted on the Karnaugh map shown (rows AB , columns CD). The minimal sum-of-products expression for G is: [2 marks]

$AB \backslash CD$	00	01	11	10
00	1	0	0	0
01	1	0	0	0
11	1	0	0	0
10	1	0	0	0

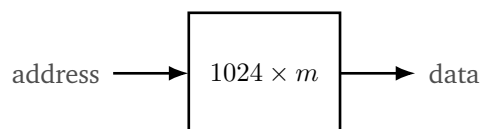- (A) $\bar{A} \bar{B}$
 (B) CD
 (C) $A \bar{B}$
 (D) $\bar{C} \bar{D}$
- Q23.** A random-access memory stores 1024 words, addressed one word at a time through the address block shown. The number of address lines needed to select any one word is: [2 marks]



- (A) 8
 (B) 16
 (C) 32
 (D) 10
- Q24.** A mod-16 asynchronous (ripple) counter is built from four cascaded flip-flops, each with a propagation delay of 5 ns. The worst-case time for the counter outputs to settle after an active clock edge is: [2 marks]

- (A) 5 ns
 (B) 80 ns




- (C) 20 ns
- (D) 10 ns

Signals and Systems

Q25. A periodic signal $x(t)$ is a real, odd function of time (that is, $x(-t) = -x(t)$). Its trigonometric Fourier series contains: [2 marks]

- (A) only sine terms
- (B) only cosine terms
- (C) only a dc term
- (D) only even harmonics

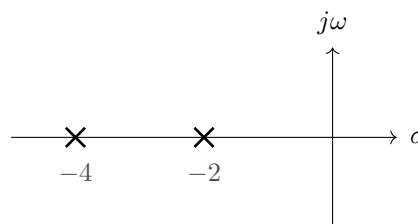Q26. A stable LTI system has the transfer function $H(s) = \frac{20}{s^2 + 6s + 8}$, whose pole-zero plot is shown (poles marked $\times$). The d.c. gain $H(0)$ of the system is: [2 marks]



- (A) 20
- (B) 8
- (C) 2.5
- (D) 5

Q27. A periodic signal is $x(t) = 2 + 3 \cos(\omega_0 t) + 4 \cos(2\omega_0 t)$. The dc (average) value of $x(t)$, i.e. the Fourier-series coefficient a_0 , is: [2 marks]

- (A) 2
- (B) 3
- (C) 9
- (D) 0



Q28. For the same signal $x(t) = 2 + 3 \cos(\omega_0 t) + 4 \cos(2\omega_0 t)$, the average power (by Parseval's theorem, summing the dc power and half the square of each harmonic amplitude) is: [2 marks]

- (A) 29
- (B) 4
- (C) 12.5
- (D) 16.5

Q29. Two finite-length discrete sequences of lengths 5 and 4 samples respectively are linearly convolved. The length (number of samples) of the resulting sequence is: [2 marks]

- (A) 9
- (B) 8
- (C) 20
- (D) 5

Q30. A continuous-time signal contains spectral components at 1 kHz, 2 kHz and 3 kHz only. The minimum sampling rate (Nyquist rate) needed to reconstruct it without aliasing is: [2 marks]

- (A) 3 kHz
- (B) 12 kHz
- (C) 1.5 kHz
- (D) 6 kHz

Control Systems

Q31. A standard second-order system has the characteristic equation $s^2 + 6s + 25 = 0$. The damping ratio ζ of the system is: [2 marks]

- (A) 0.3
- (B) 0.6
- (C) 1.2



(D) 0.5

Q32. The characteristic equation of a feedback system is $s^3 + 6s^2 + 11s + 6 = 0$. Using the Routh–Hurwitz criterion, the number of closed-loop poles lying in the right half of the s -plane is: [2 marks]

(A) 0

(B) 3

(C) 1

(D) 2

Q33. A unity-feedback control system has the open-loop transfer function $G(s) = \frac{10}{s(s+2)}$ (a type-1 system). The steady-state error for a unit-step input is: [2 marks]


(A) 0

(B) 0.5

(C) 1

(D) 0.2

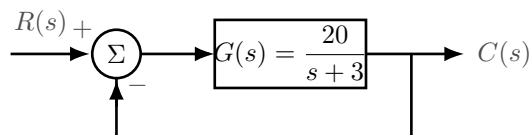Q34. For the unity-feedback control system shown, the forward-path transfer function is $G(s) = \frac{20}{s+3}$. The d.c. gain of the closed-loop transfer function $\frac{C(s)}{R(s)} = \frac{G(s)}{1+G(s)}$ (its value at $s = 0$) is nearest to: [2 marks]



(A) 20

(B) 0.87

(C) 1


(D) 0.5



- Q35.** A unity-feedback second-order system has undamped natural frequency $\omega_n = 10$ rad/s and damping ratio $\zeta = 0.5$. The damped natural frequency $\omega_d = \omega_n \sqrt{1 - \zeta^2}$ of its transient response is nearest to: [2 marks]
- (A) 10 rad/s
(B) 5 rad/s
(C) 8.66 rad/s
(D) 7.5 rad/s

Communications

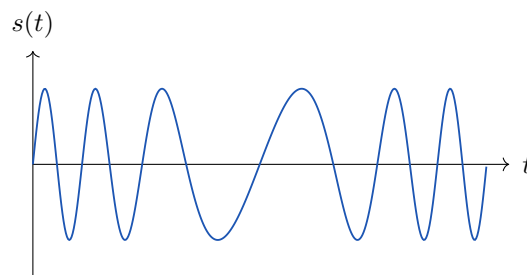- Q36.** A frequency-modulated (FM) signal, whose constant-envelope waveform is shown, is produced by a modulator of frequency sensitivity $k_f = 10$ kHz/V driven by a single tone of peak amplitude $A_m = 5$ V. The peak frequency deviation $\Delta f = k_f A_m$ is: [2 marks]




- (A) 10 kHz
(B) 50 kHz
(C) 2 kHz
(D) 100 kHz
- Q37.** A commercial FM signal has a peak frequency deviation of $\Delta f = 60$ kHz for a modulating tone of frequency $f_m = 10$ kHz. By Carson's rule the transmission bandwidth $B = 2(\Delta f + f_m)$ is: [2 marks]
- (A) 60 kHz
(B) 70 kHz
(C) 120 kHz
(D) 140 kHz



Q38. A phase-modulated (PM) signal is $s(t) = A \cos(\omega_c t + k_p m(t))$ with phase sensitivity $k_p = 2 \text{ rad/V}$. The modulating signal $m(t)$ has a peak amplitude of 3 V. The peak phase deviation $\Delta\phi = k_p m_{peak}$ is: [2 marks]

- (A) 2 rad
- (B) 6 rad
- (C) 3 rad
- (D) 1.5 rad

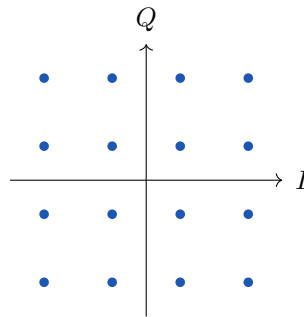Q39. A digital link uses 16-QAM, whose 16-point signal constellation is shown, to carry a bit rate of 8 Mbps. Since 16-QAM transmits 4 bits per symbol, the symbol rate is: [2 marks]



- (A) 4 Msym/s
- (B) 2 Msym/s
- (C) 32 Msym/s
- (D) 0.5 Msym/s

Q40. A discrete memoryless source emits eight symbols that are all equally likely. The entropy of the source is: [2 marks]

- (A) 3 bits/symbol
- (B) 8 bits/symbol
- (C) 1 bit/symbol
- (D) 2 bits/symbol




Q41. A communication channel of bandwidth 4 kHz has a signal-to-noise ratio of 15 (as a power ratio). By the Shannon–Hartley law $C = B \log_2(1 + \text{SNR})$, the channel capacity is: [2 marks]

- (A) 16 kbps
- (B) 4 kbps
- (C) 8 kbps
- (D) 60 kbps

Electromagnetics

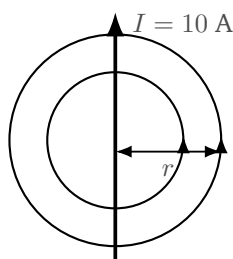Q42. An infinitely long straight wire carries a steady current $I = 10$ A. Using Ampere's circuital law, the magnetic flux density at a radial distance $r = 0.5$ m from the wire, $B = \frac{\mu_0 I}{2\pi r}$, is: [2 marks]



- (A) $1 \mu\text{T}$
- (B) $2 \mu\text{T}$
- (C) $4 \mu\text{T}$
- (D) $8 \mu\text{T}$

Q43. A long air-cored solenoid has $n = 1000$ turns per metre and carries a current $I = 2$ A. By Ampere's law the magnetic flux density on its axis, $B = \mu_0 n I$, is nearest to: [2 marks]


- (A) 1.26 mT
- (B) 2.5 mT
- (C) 5 mT
- (D) 0.8 mT



Q44. An air-cored toroid has $N = 500$ turns wound on a core of mean radius $r = 0.1$ m and carries a current $I = 2$ A. By Ampere's law the magnetic flux density along the mean circumference, $B = \frac{\mu_0 NI}{2\pi r}$, is nearest to: [2 marks]

- (A) 1 mT
- (B) 4 mT
- (C) 2 mT
- (D) 0.5 mT

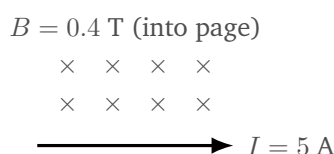Q45. A straight conductor of length $L = 0.2$ m carries a current $I = 5$ A at right angles to a uniform magnetic field $B = 0.4$ T (directed into the page), as shown. The magnitude of the magnetic force on the conductor, $F = BIL$, is: [2 marks]



- (A) 1 N
- (B) 2 N
- (C) 0.4 N
- (D) 0.1 N

Q46. Two long parallel wires spaced $d = 1$ m apart each carry a current of 10 A in the same direction. By Ampere's law the magnitude of the magnetic force per unit length between them, $\frac{F}{L} = \frac{\mu_0 I_1 I_2}{2\pi d}$, is: [2 marks]

- (A) 1×10^{-5} N/m
- (B) 4×10^{-5} N/m
- (C) 8×10^{-5} N/m
- (D) 2×10^{-5} N/m



Detailed Solutions

Q1.

Solution

Concept – Norton current from a Thevenin source: The Norton current is the current that flows when the output terminals are shorted, $I_N = \frac{V_{th}}{R_{th}}$.

Step 1 – identify the Thevenin parameters: $V_{th} = 12 \text{ V}$, $R_{th} = 4 \Omega$.

Step 2 – short the terminals $a-b$: With a and b joined, the full source voltage appears across the 4Ω resistor.

Step 3 – apply Ohm's law: $I_N = \frac{12}{4}$

Step 4 – evaluate: $I_N = 3 \text{ A}$

Final Answer: $I_N = 3 \text{ A} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q1](#)

Q2.

Solution

Concept – Thevenin resistance with sources deactivated: Replace the independent voltage source by a short circuit and reduce the resistor network seen from the terminals.

Step 1 – combine the two parallel resistors: $12 \Omega \parallel 12 \Omega = \frac{12 \times 12}{12 + 12}$

Step 2 – evaluate the parallel value: $= \frac{144}{24} = 6 \Omega$

Step 3 – add the series resistor: $R_{th} = 6 + 6$

Step 4 – evaluate: $R_{th} = 12 \Omega$

Final Answer: $R_{th} = 12 \Omega \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q2](#)

Q3.

Solution

Concept – source transformation (Norton to Thevenin): A Norton source (I_N, R_N) converts to a Thevenin source with $V_{th} = I_N R_N$ and the same resistance $R_{th} = R_N$.

Step 1 – list the Norton data: $I_N = 2 \text{ A}$, $R_N = 10 \Omega$.



Step 2 – multiply to get the open-circuit voltage: $V_{th} = 2 \times 10$

Step 3 – evaluate: $V_{th} = 20 \text{ V}$

Step 4 – note the resistance is unchanged: $R_{th} = R_N = 10 \Omega$.

Final Answer: $V_{th} = 20 \text{ V} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q3](#)

Q4.

Solution

Concept – open-circuit (Thevenin) voltage by voltage division: With the output open, no current flows out, so the terminal voltage equals the divider voltage across the chosen resistor, $V_{th} = V_s \frac{R_2}{R_1 + R_2}$.

Step 1 – list the data: $V_s = 16 \text{ V}$, $R_1 = 2 \text{ k}\Omega$, $R_2 = 6 \text{ k}\Omega$.

Step 2 – form the total series resistance: $R_1 + R_2 = 2 + 6 = 8 \text{ k}\Omega$

Step 3 – form the divider ratio: $\frac{R_2}{R_1 + R_2} = \frac{6}{8} = 0.75$

Step 4 – multiply by the source voltage: $V_{th} = 16 \times 0.75$

Step 5 – evaluate: $V_{th} = 12 \text{ V}$

Final Answer: $V_{th} = 12 \text{ V} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q4](#)

Q5.

Solution

Concept – current-divider rule: For a current source feeding two parallel resistors, the current in one branch is proportional to the *other* resistor, $I_{load} = I \frac{R_{parallel}}{R_{parallel} + R_{load}}$.

Step 1 – list the data: $I = 5 \text{ A}$, parallel resistor $R_p = 20 \Omega$, load $R_L = 5 \Omega$.

Step 2 – form the divider ratio for the load branch: $\frac{R_p}{R_p + R_L} = \frac{20}{20 + 5} = \frac{20}{25}$

Step 3 – simplify the ratio: $= 0.8$

Step 4 – multiply by the source current: $I_{load} = 5 \times 0.8$

Step 5 – evaluate: $I_{load} = 4 \text{ A}$

Final Answer: $I_{load} = 4 \text{ A} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q5](#)



Q6.

Solution

Concept – capacitors in series: Capacitors in series combine like resistors in parallel, $C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$.

Step 1 – list the data: $C_1 = 4 \mu\text{F}$, $C_2 = 12 \mu\text{F}$.

Step 2 – form the product: $C_1 C_2 = 4 \times 12 = 48$

Step 3 – form the sum: $C_1 + C_2 = 4 + 12 = 16$

Step 4 – divide: $C_{eq} = \frac{48}{16}$

Step 5 – evaluate: $C_{eq} = 3 \mu\text{F}$

Final Answer: $C_{eq} = 3 \mu\text{F} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q6](#)

Q7.

Solution

Concept – MOSFET region test: For an n -channel MOSFET with $V_{GS} > V_t$, the device is in the triode region when $V_{DS} < V_{GS} - V_t$ and in saturation when $V_{DS} \geq V_{GS} - V_t$.

Step 1 – check that the channel is on: $V_{GS} = 3 \text{ V}$ is greater than $V_t = 1 \text{ V}$, so the channel exists.

Step 2 – compute the overdrive voltage: $V_{GS} - V_t = 3 - 1 = 2 \text{ V}$

Step 3 – compare V_{DS} with the overdrive: $V_{DS} = 0.5 \text{ V} < 2 \text{ V}$

Step 4 – classify the region: Because V_{DS} is below the overdrive, the MOSFET is in the **triode (linear) region**.

Why the other options are wrong:

- B, saturation: would need $V_{DS} \geq 2 \text{ V}$, but here $V_{DS} = 0.5 \text{ V}$.
- C, cut-off: would need $V_{GS} < V_t$, but $3 > 1$.
- D, breakdown: needs excessive voltage, not present here.

Final Answer: triode (linear) region $\Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q7](#)



Q8.

Solution

Concept – MOSFET cut-off condition: An enhancement MOSFET conducts only when V_{GS} exceeds the threshold V_t ; if $V_{GS} < V_t$ no channel forms and the device is cut off.

Step 1 – read the gate bias: $V_{GS} = 0.6 \text{ V}$.

Step 2 – compare with the threshold: $V_{GS} = 0.6 \text{ V} < V_t = 1 \text{ V}$

Step 3 – conclude the channel state: Since the gate voltage is below threshold, no inversion channel forms.

Step 4 – classify the region: With no channel, the drain current is essentially zero, so the device is in the **cut-off region**.

Final Answer: cut-off region $\Rightarrow$

Answer: (A) [Go Back to Q8](#)

Q9.

Solution

Concept – MOSFET saturation condition: For $V_{GS} > V_t$, the MOSFET saturates when $V_{DS} \geq V_{GS} - V_t$.

Step 1 – check that the channel is on: $V_{GS} = 2.8 \text{ V}$ is greater than $V_t = 0.8 \text{ V}$, so a channel exists.

Step 2 – compute the overdrive voltage: $V_{GS} - V_t = 2.8 - 0.8 = 2 \text{ V}$

Step 3 – compare V_{DS} with the overdrive: $V_{DS} = 3 \text{ V} \geq 2 \text{ V}$

Step 4 – classify the region: Because V_{DS} exceeds the overdrive, the channel pinches off at the drain and the device is in the **saturation region**.

Why the other options are wrong:

- A, cut-off: needs $V_{GS} < V_t$, but $2.8 > 0.8$.
- B, triode: needs $V_{DS} < 2 \text{ V}$, but here $V_{DS} = 3 \text{ V}$.
- D, breakdown: needs a junction voltage beyond its rating, not the case here.

Final Answer: saturation region $\Rightarrow$

Answer: (C) [Go Back to Q9](#)



Q10.

Solution

Concept – saturation drain current of a MOSFET: In saturation $I_D = \frac{1}{2}k_n (V_{GS} - V_t)^2$.

Step 1 – compute the overdrive voltage: $V_{GS} - V_t = 1.5 - 0.5 = 1 \text{ V}$

Step 2 – square the overdrive: $(V_{GS} - V_t)^2 = 1^2 = 1 \text{ V}^2$

Step 3 – substitute into the current equation: $I_D = \frac{1}{2} \times (2 \text{ mA/V}^2) \times 1$

Step 4 – evaluate: $I_D = 1 \text{ mA}$

Final Answer: $I_D = 1 \text{ mA} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q10](#)

Q11.

Solution

Concept – MOSFET transconductance in saturation: The small-signal transconductance can be written as $g_m = \sqrt{2k_n I_D}$.

Step 1 – list the data: $k_n = 2 \text{ mA/V}^2$, $I_D = 1 \text{ mA}$.

Step 2 – form the product $2k_n I_D$: $2 \times 2 \times 1 = 4$

Step 3 – take the square root: $g_m = \sqrt{4}$

Step 4 – evaluate: $g_m = 2 \text{ mA/V}$

Final Answer: $g_m = 2 \text{ mA/V} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q11](#)

Q12.

Solution

Concept – gain of an inverting op-amp: For an ideal inverting amplifier the gain magnitude is $|A_v| = \frac{R_f}{R_1}$.

Step 1 – list the resistor values: $R_f = 8 \text{ k}\Omega$, $R_1 = 2 \text{ k}\Omega$.

Step 2 – form the ratio: $|A_v| = \frac{8 \text{ k}\Omega}{2 \text{ k}\Omega}$

Step 3 – evaluate: $|A_v| = 4$

Final Answer: $|A_v| = 4 \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q12](#)



Q13.

Solution

Concept – balanced difference amplifier: When $R_1 = R_2$ and $R_f = R_g$, the output of the op-amp difference amplifier is $V_o = \frac{R_f}{R_1}(V_2 - V_1)$.

Step 1 – form the resistor ratio: $\frac{R_f}{R_1} = \frac{30 \text{ k}\Omega}{10 \text{ k}\Omega} = 3$

Step 2 – form the input difference: $V_2 - V_1 = 2 - 1 = 1 \text{ V}$

Step 3 – multiply: $V_o = 3 \times 1$

Step 4 – evaluate: $V_o = 3 \text{ V}$

Why the other options are wrong:

- A, 7 V: wrongly adds the inputs instead of subtracting.
- C, -3 V: reverses the sign; the non-inverting input carries the larger voltage, so V_o is positive.
- D, 10 V: ignores the difference and misuses the gain.

Final Answer: $V_o = 3 \text{ V} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q13](#)

Q14.

Solution

Concept – common-mode rejection ratio in decibels: $\text{CMRR} = \frac{A_d}{A_{cm}}$, and in decibels $\text{CMRR}_{\text{dB}} = 20 \log_{10}\left(\frac{A_d}{A_{cm}}\right)$.

Step 1 – form the ratio of gains: $\frac{A_d}{A_{cm}} = \frac{100}{0.1}$

Step 2 – evaluate the ratio: $= 1000$

Step 3 – take the base-10 logarithm: $\log_{10}(1000) = 3$

Step 4 – multiply by 20: $\text{CMRR}_{\text{dB}} = 20 \times 3$

Step 5 – evaluate: $\text{CMRR}_{\text{dB}} = 60 \text{ dB}$

Final Answer: $\text{CMRR}_{\text{dB}} = 60 \text{ dB} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q14](#)



Q15.

Solution

Concept – gain-bandwidth product: For a single-pole op-amp the product of closed-loop gain and bandwidth is constant, so $BW = \frac{GBW}{A_{CL}}$.

Step 1 – list the data: $GBW = 10 \text{ MHz} = 10 \times 10^6 \text{ Hz}$, $A_{CL} = 50$.

Step 2 – divide: $BW = \frac{10 \times 10^6}{50}$

Step 3 – evaluate: $BW = 0.2 \times 10^6 \text{ Hz}$

Step 4 – express in kilohertz: $BW = 200 \text{ kHz}$

Final Answer: $BW = 200 \text{ kHz} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q15](#)

Q16.

Solution

Concept – slew-rate-limited full-power bandwidth: The highest sinusoidal frequency an op-amp can reproduce without slew-rate distortion is $f = \frac{SR}{2\pi V_{peak}}$.

Step 1 – convert the slew rate to base units: $SR = 1 \text{ V}/\mu\text{s} = 1 \times 10^6 \text{ V/s}$

Step 2 – form the denominator: $2\pi V_{peak} = 2\pi \times 2 = 12.566$

Step 3 – divide: $f = \frac{1 \times 10^6}{12.566}$

Step 4 – evaluate: $f = 79.6 \times 10^3 \text{ Hz} = 79.6 \text{ kHz}$

Final Answer: $f \approx 79.6 \text{ kHz} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q16](#)

Q17.

Solution

Concept – cut-off frequency of a first-order RC low-pass filter: $f_c = \frac{1}{2\pi RC}$.

Step 1 – convert the values to base units: $R = 1 \text{ k}\Omega = 1 \times 10^3 \Omega$

$C = 0.1 \mu\text{F} = 0.1 \times 10^{-6} \text{ F} = 1 \times 10^{-7} \text{ F}$

Step 2 – form the product RC: $RC = (1 \times 10^3) \times (1 \times 10^{-7}) = 1 \times 10^{-4} \text{ s}$

Step 3 – form $2\pi RC$: $2\pi RC = 6.2832 \times 10^{-4}$

Step 4 – invert: $f_c = \frac{1}{6.2832 \times 10^{-4}}$



Step 5 – evaluate: $f_c \approx 1591 \text{ Hz} \approx 1.59 \text{ kHz}$

Final Answer: $f_c \approx 1.59 \text{ kHz} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q17](#)

Q18.

Solution

Concept – current split in a balanced differential pair: An emitter-coupled pair driven by a tail current source shares that current equally between the two transistors when the differential input is zero.

Step 1 – read the tail current: $I_{EE} = 2 \text{ mA}$.

Step 2 – apply the balance condition: With $v_1 = v_2$, symmetry forces $I_{C1} = I_{C2}$.

Step 3 – split the tail current equally: $I_{C1} = I_{C2} = \frac{I_{EE}}{2} = \frac{2}{2}$

Step 4 – evaluate: Each collector current = 1 mA.

Final Answer: 1 mA per transistor $\Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q18](#)

Q19.

Solution

Concept – hexadecimal to decimal conversion: Each hex digit is weighted by a power of 16: $(d_1 d_0)_{16} = d_1 \times 16 + d_0$.

Step 1 – identify the digit values: The digit 2 has value 2; the digit F has value 15.

Step 2 – weight the most significant digit: $2 \times 16 = 32$

Step 3 – add the least significant digit: $32 + 15$

Step 4 – evaluate: $(2F)_{16} = 47$

Final Answer: $47 \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q19](#)



Q20.

Solution

Concept – Boolean simplification: Combine like terms using $X + X = X$, $A + \bar{A} = 1$ and $A + \bar{A}B = A + B$.

Step 1 – write the expression: $Y = AB + \bar{A}B + A\bar{B}$

Step 2 – combine the first two terms (factor B): $AB + \bar{A}B = B(A + \bar{A}) = B(1) = B$

Step 3 – substitute back: $Y = B + A\bar{B}$

Step 4 – apply the absorption identity $B + A\bar{B} = B + A$: $Y = A + B$

Final Answer: $Y = A + B \Rightarrow \boxed{D}$

Answer: (D) [Go Back to Q20](#)

Q21.

Solution

Concept – Karnaugh-map grouping: Adjacent 1-cells are grouped in powers of two; the variables that stay constant over the group appear in the product term.

Step 1 – locate the minterms: m_0, m_1, m_2, m_3 all lie in the top row, where $AB = 00$.

Step 2 – group the four cells of that row: A group of four cells spanning all columns of the $AB = 00$ row is formed.

Step 3 – find the constant variables over the group: Across the group $A = 0$ and $B = 0$ throughout, while C and D change.

Step 4 – write the product term: Constant $A = 0$ gives $\bar{A}$ and constant $B = 0$ gives $\bar{B}$, so $F = \bar{A}\bar{B}$.

Final Answer: $F = \bar{A}\bar{B} \Rightarrow \boxed{A}$

Answer: (A) [Go Back to Q21](#)

Q22.

Solution

Concept – Karnaugh-map grouping: Group adjacent 1-cells and keep only the variables that remain constant over the group.

Step 1 – locate the minterms: m_0, m_4, m_8, m_{12} all lie in the left column, where $CD = 00$.



Step 2 – group the four cells of that column: A group of four cells spanning all rows of the $CD = 00$ column is formed.

Step 3 – find the constant variables over the group: Across the group $C = 0$ and $D = 0$ throughout, while A and B change.

Step 4 – write the product term: Constant $C = 0$ gives $\bar{C}$ and constant $D = 0$ gives $\bar{D}$, so $G = \bar{C} \bar{D}$.

Final Answer: $G = \bar{C} \bar{D} \Rightarrow$ D

Answer: (D) [Go Back to Q22](#)

Q23.

Solution

Concept – address lines for a memory: To uniquely select one of N words, the number of address lines is $\lceil \log_2 N \rceil$.

Step 1 – list the data: $N = 1024$ words.

Step 2 – express 1024 as a power of two: $1024 = 2^{10}$

Step 3 – take the base-2 logarithm: $\log_2(2^{10}) = 10$

Step 4 – state the number of lines: 10 address lines are required.

Final Answer: 10 address lines $\Rightarrow$ D

Answer: (D) [Go Back to Q23](#)

Q24.

Solution

Concept – worst-case delay of a ripple counter: In an asynchronous counter each flip-flop clocks the next, so delays add and the worst case is $t_{worst} = (\text{number of stages}) \times t_{pd}$.

Step 1 – list the data: Number of flip-flops = 4 (mod-16 needs $2^4 = 16$ states), $t_{pd} = 5$ ns each.

Step 2 – identify the longest chain: The last flip-flop can change only after all four have toggled in sequence.

Step 3 – add the delays: $t_{worst} = 4 \times 5$

Step 4 – evaluate: $t_{worst} = 20$ ns

Final Answer: $t_{worst} = 20$ ns $\Rightarrow$ C

Answer: (C) [Go Back to Q24](#)



Q25.

Solution

Concept – Fourier series and waveform symmetry: The trigonometric Fourier series of a real signal keeps cosine terms for the even part and sine terms for the odd part; a purely odd signal has no cosine or dc content.

Step 1 – classify the signal: $x(t)$ is odd: $x(-t) = -x(t)$.

Step 2 – test the dc (average) term: The average of an odd function over a full period is zero, so $a_0 = 0$.

Step 3 – test the cosine coefficients: Cosine is even, so the product $x(t) \cos(n\omega_0 t)$ is odd and integrates to zero; all cosine coefficients vanish.

Step 4 – identify what remains: Only the sine terms (the odd basis functions) can be nonzero.

Final Answer: only sine terms $\Rightarrow$ **A**

Answer: (A) [Go Back to Q25](#)

Q26.

Solution

Concept – d.c. gain of a transfer function: The d.c. gain is the value of $H(s)$ at $s = 0$.

Step 1 – substitute $s = 0$: $H(0) = \frac{20}{0^2 + 6(0) + 8}$

Step 2 – evaluate the denominator: $0 + 0 + 8 = 8$

Step 3 – divide: $H(0) = \frac{20}{8}$

Step 4 – evaluate: $H(0) = 2.5$

Final Answer: $H(0) = 2.5 \Rightarrow$ **C**

Answer: (C) [Go Back to Q26](#)

Q27.

Solution

Concept – dc term of a Fourier series: In $x(t) = a_0 + \sum a_n \cos(n\omega_0 t) + \dots$, the constant a_0 is the time-average (dc) value.

Step 1 – write the signal: $x(t) = 2 + 3 \cos(\omega_0 t) + 4 \cos(2\omega_0 t)$

Step 2 – note the average of each cosine: Each cosine term averages to zero over a full period.



Step 3 – keep only the constant term: The time-average of $x(t)$ equals the constant 2.

Step 4 – state the coefficient: $a_0 = 2$

Final Answer: $a_0 = 2 \Rightarrow \boxed{A}$

Answer: (A) [Go Back to Q27](#)

Q28.

Solution

Concept – average power by Parseval's theorem: For a sum of a dc term and cosines, $P = a_0^2 + \sum \frac{A_k^2}{2}$, where A_k is each harmonic amplitude.

Step 1 – compute the dc power: $a_0^2 = 2^2 = 4$

Step 2 – compute the power of the first harmonic: $\frac{3^2}{2} = \frac{9}{2} = 4.5$

Step 3 – compute the power of the second harmonic: $\frac{4^2}{2} = \frac{16}{2} = 8$

Step 4 – add the contributions: $P = 4 + 4.5 + 8$

Step 5 – evaluate: $P = 16.5$

Final Answer: $P = 16.5 \Rightarrow \boxed{D}$

Answer: (D) [Go Back to Q28](#)

Q29.

Solution

Concept – length of a linear convolution: Convolution of sequences of lengths L_1 and L_2 gives a sequence of length $L_1 + L_2 - 1$.

Step 1 – list the lengths: $L_1 = 5, L_2 = 4$.

Step 2 – add the lengths: $L_1 + L_2 = 5 + 4 = 9$

Step 3 – subtract one: $9 - 1 = 8$

Step 4 – state the result: The output has 8 samples.

Final Answer: 8 samples $\Rightarrow \boxed{B}$

Answer: (B) [Go Back to Q29](#)



Q30.

Solution

Concept – Nyquist rate: A band-limited signal must be sampled at at least twice its highest frequency component.

Step 1 – identify the highest frequency: The components are at 1, 2 and 3 kHz, so $f_{max} = 3$ kHz.

Step 2 – double the highest frequency: $f_s^{min} = 2 \times 3$

Step 3 – evaluate: $f_s^{min} = 6$ kHz

Final Answer: $f_s^{min} = 6$ kHz $\Rightarrow$ **D**

Answer: (D) [Go Back to Q30](#)

Q31.

Solution

Concept – damping ratio from the characteristic equation: Comparing $s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$ with the given equation gives $\omega_n = \sqrt{\text{constant}}$ and $\zeta = \frac{\text{coefficient of } s}{2\omega_n}$.

Step 1 – read the constant term: $\omega_n^2 = 25$, so $\omega_n = 5$ rad/s.

Step 2 – read the coefficient of s : $2\zeta\omega_n = 6$

Step 3 – solve for ζ : $\zeta = \frac{6}{2 \times 5} = \frac{6}{10}$

Step 4 – evaluate: $\zeta = 0.6$

Final Answer: $\zeta = 0.6 \Rightarrow$ **B**

Answer: (B) [Go Back to Q31](#)

Q32.

Solution

Concept – Routh–Hurwitz stability test: The number of right-half-plane poles equals the number of sign changes in the first column of the Routh array.

Step 1 – write the coefficients: For $s^3 + 6s^2 + 11s + 6$: row s^3 gives [1, 11], row s^2 gives [6, 6].

Step 2 – compute the s^1 row: $\frac{6 \times 11 - 1 \times 6}{6} = \frac{66 - 6}{6} = \frac{60}{6} = 10$

Step 3 – compute the s^0 row: The last entry carries down as 6.

Step 4 – inspect the first column: The first column is 1, 6, 10, 6: all positive,



with no sign changes.

Step 5 – conclude: Zero sign changes means zero poles in the right half-plane; the system is stable.

Final Answer: 0 RHP poles $\Rightarrow$ **A**

Answer: (A) [Go Back to Q32](#)

Q33.

Solution

Concept – steady-state error of a type-1 system to a step: For a step input the error is $e_{ss} = \frac{1}{1 + K_p}$ with $K_p = \lim_{s \rightarrow 0} G(s)$; a type-1 system (a pole at the origin) makes K_p infinite.

Step 1 – evaluate the position error constant: $K_p = \lim_{s \rightarrow 0} \frac{10}{s(s+2)}$

Step 2 – take the limit: As $s \rightarrow 0$ the factor s in the denominator drives $K_p \rightarrow \infty$.

Step 3 – substitute into the error formula: $e_{ss} = \frac{1}{1 + \infty}$

Step 4 – evaluate: $e_{ss} = 0$

Why it makes sense: A type-1 open loop has one integrator, which drives the steady-state step error to exactly zero.

Final Answer: $e_{ss} = 0 \Rightarrow$ **A**

Answer: (A) [Go Back to Q33](#)

Q34.

Solution

Concept – d.c. gain of a closed loop: The closed-loop transfer function is $\frac{C}{R} = \frac{G}{1 + G}$; its d.c. gain is obtained at $s = 0$.

Step 1 – evaluate the forward gain at $s = 0$: $G(0) = \frac{20}{0+3} = \frac{20}{3} = 6.667$

Step 2 – form the numerator of the closed-loop gain: Numerator = $G(0) = 6.667$

Step 3 – form the denominator: $1 + G(0) = 1 + 6.667 = 7.667$

Step 4 – divide: $\frac{C}{R} \Big|_{s=0} = \frac{6.667}{7.667}$

Step 5 – evaluate: ≈ 0.87



Final Answer: d.c. gain $\approx 0.87 \Rightarrow$ **B**

Answer: (B) [Go Back to Q34](#)

Q35.

Solution

Concept – damped natural frequency: For an underdamped second-order system $\omega_d = \omega_n \sqrt{1 - \zeta^2}$.

Step 1 – list the data: $\omega_n = 10 \text{ rad/s}$, $\zeta = 0.5$.

Step 2 – square the damping ratio: $\zeta^2 = 0.5^2 = 0.25$

Step 3 – form $1 - \zeta^2$: $1 - 0.25 = 0.75$

Step 4 – take the square root: $\sqrt{0.75} = 0.866$

Step 5 – multiply by ω_n : $\omega_d = 10 \times 0.866 = 8.66 \text{ rad/s}$

Final Answer: $\omega_d \approx 8.66 \text{ rad/s} \Rightarrow$ **C**

Answer: (C) [Go Back to Q35](#)

Q36.

Solution

Concept – peak frequency deviation in FM: The instantaneous frequency of an FM signal deviates from the carrier by $\Delta f = k_f A_m$ for a tone of amplitude A_m .

Step 1 – list the data: $k_f = 10 \text{ kHz/V}$, $A_m = 5 \text{ V}$.

Step 2 – multiply: $\Delta f = 10 \times 5$

Step 3 – evaluate: $\Delta f = 50 \text{ kHz}$

Final Answer: $\Delta f = 50 \text{ kHz} \Rightarrow$ **B**

Answer: (B) [Go Back to Q36](#)

Q37.

Solution

Concept – Carson's rule for FM bandwidth: The transmission bandwidth is $B = 2(\Delta f + f_m)$.

Step 1 – list the data: $\Delta f = 60 \text{ kHz}$, $f_m = 10 \text{ kHz}$.

Step 2 – add the deviation and modulating frequency: $\Delta f + f_m = 60 + 10 = 70 \text{ kHz}$



Step 3 – multiply by two: $B = 2 \times 70$

Step 4 – evaluate: $B = 140 \text{ kHz}$

Final Answer: $B = 140 \text{ kHz} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q37](#)

Q38.

Solution

Concept – peak phase deviation in PM: For $s(t) = A \cos(\omega_c t + k_p m(t))$ the peak phase deviation is $\Delta\phi = k_p m_{peak}$.

Step 1 – list the data: $k_p = 2 \text{ rad/V}$, $m_{peak} = 3 \text{ V}$.

Step 2 – multiply: $\Delta\phi = 2 \times 3$

Step 3 – evaluate: $\Delta\phi = 6 \text{ rad}$

Final Answer: $\Delta\phi = 6 \text{ rad} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q38](#)

Q39.

Solution

Concept – symbol rate from bit rate: $R_s = \frac{R_b}{\log_2 M}$, where M is the number of constellation points.

Step 1 – find the bits per symbol: 16-QAM has $M = 16$, so $\log_2 16 = 4$ bits per symbol.

Step 2 – list the bit rate: $R_b = 8 \text{ Mbps}$.

Step 3 – divide: $R_s = \frac{8}{4}$

Step 4 – evaluate: $R_s = 2 \text{ Msym/s}$

Final Answer: $R_s = 2 \text{ Msym/s} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q39](#)



Q40.

Solution

Concept – entropy of an equiprobable source: For M equally likely symbols the entropy is $H = \log_2 M$ bits/symbol.

Step 1 – list the data: $M = 8$ equally likely symbols.

Step 2 – express 8 as a power of two: $8 = 2^3$

Step 3 – take the base-2 logarithm: $H = \log_2(2^3) = 3$

Step 4 – state the result: $H = 3$ bits/symbol

Final Answer: $H = 3$ bits/symbol $\Rightarrow$ A

Answer: (A) [Go Back to Q40](#)

Q41.

Solution

Concept – Shannon–Hartley channel capacity: $C = B \log_2(1 + \text{SNR})$.

Step 1 – list the data: $B = 4$ kHz, $\text{SNR} = 15$.

Step 2 – form the term inside the logarithm: $1 + \text{SNR} = 1 + 15 = 16$

Step 3 – take the base-2 logarithm: $\log_2(16) = 4$

Step 4 – multiply by the bandwidth: $C = 4$ kHz $\times 4$

Step 5 – evaluate: $C = 16$ kbps

Final Answer: $C = 16$ kbps $\Rightarrow$ A

Answer: (A) [Go Back to Q41](#)

Q42.

Solution

Concept – Ampere’s law for a long straight wire: The field encircling a long straight wire is $B = \frac{\mu_0 I}{2\pi r}$.

Step 1 – list the data: $\mu_0 = 4\pi \times 10^{-7}$ H/m, $I = 10$ A, $r = 0.5$ m.

Step 2 – form the numerator: $\mu_0 I = (4\pi \times 10^{-7}) \times 10 = 4\pi \times 10^{-6}$

Step 3 – form the denominator: $2\pi r = 2\pi \times 0.5 = \pi$

Step 4 – divide: $B = \frac{4\pi \times 10^{-6}}{\pi} = 4 \times 10^{-6}$ T

Step 5 – express in microtesla: $B = 4 \mu\text{T}$



Final Answer: $B = 4 \mu\text{T} \Rightarrow$

Answer: (C) [Go Back to Q42](#)

Q43.

Solution

Concept – Ampere’s law for a long solenoid: The axial field of a long solenoid is $B = \mu_0 nI$, with n the turns per metre.

Step 1 – list the data: $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$, $n = 1000 \text{ turns/m}$, $I = 2 \text{ A}$.

Step 2 – multiply n and I : $nI = 1000 \times 2 = 2000$

Step 3 – multiply by μ_0 : $B = (4\pi \times 10^{-7}) \times 2000 = 8\pi \times 10^{-4}$

Step 4 – evaluate numerically: $B = 8 \times 3.1416 \times 10^{-4} = 2.51 \times 10^{-3} \text{ T}$

Step 5 – express in millitesla: $B \approx 2.5 \text{ mT}$

Final Answer: $B \approx 2.5 \text{ mT} \Rightarrow$

Answer: (B) [Go Back to Q43](#)

Q44.

Solution

Concept – Ampere’s law for a toroid: Along the mean circumference of a toroid $B = \frac{\mu_0 NI}{2\pi r}$.

Step 1 – list the data: $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$, $N = 500$, $I = 2 \text{ A}$, $r = 0.1 \text{ m}$.

Step 2 – form the numerator: $\mu_0 NI = (4\pi \times 10^{-7}) \times 500 \times 2 = 4\pi \times 10^{-4}$

Step 3 – form the denominator: $2\pi r = 2\pi \times 0.1 = 0.2\pi$

Step 4 – divide: $B = \frac{4\pi \times 10^{-4}}{0.2\pi} = 20 \times 10^{-4} \text{ T}$

Step 5 – express in millitesla: $B = 2 \times 10^{-3} \text{ T} = 2 \text{ mT}$

Final Answer: $B = 2 \text{ mT} \Rightarrow$

Answer: (C) [Go Back to Q44](#)



Q45.

Solution

Concept – force on a current-carrying conductor: For a conductor perpendicular to a uniform field, $F = BIL$.

Step 1 – list the data: $B = 0.4 \text{ T}$, $I = 5 \text{ A}$, $L = 0.2 \text{ m}$.

Step 2 – multiply the field and the current: $BI = 0.4 \times 5 = 2$

Step 3 – multiply by the length: $F = 2 \times 0.2$

Step 4 – evaluate: $F = 0.4 \text{ N}$

Final Answer: $F = 0.4 \text{ N} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q45](#)

Q46.

Solution

Concept – force per unit length between parallel currents: Two long parallel wires exert $\frac{F}{L} = \frac{\mu_0 I_1 I_2}{2\pi d}$ on each other.

Step 1 – list the data: $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$, $I_1 = I_2 = 10 \text{ A}$, $d = 1 \text{ m}$.

Step 2 – form the numerator: $\mu_0 I_1 I_2 = (4\pi \times 10^{-7}) \times 10 \times 10 = 4\pi \times 10^{-5}$

Step 3 – form the denominator: $2\pi d = 2\pi \times 1 = 2\pi$

Step 4 – divide: $\frac{F}{L} = \frac{4\pi \times 10^{-5}}{2\pi} = 2 \times 10^{-5}$

Step 5 – state the result with units: $\frac{F}{L} = 2 \times 10^{-5} \text{ N/m}$

Final Answer: $\frac{F}{L} = 2 \times 10^{-5} \text{ N/m} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q46](#)



Answer Key

Q	Ans	Q	Ans	Q	Ans	Q	Ans	Q	Ans
1	B	2	D	3	A	4	C	5	D
6	B	7	A	8	A	9	C	10	A
11	C	12	C	13	B	14	C	15	D
16	B	17	D	18	B	19	A	20	D
21	A	22	D	23	D	24	C	25	A
26	C	27	A	28	D	29	B	30	D
31	B	32	A	33	A	34	B	35	C
36	B	37	D	38	B	39	B	40	A
41	A	42	C	43	B	44	C	45	C
46	D								

