

GATE Electronics and Communication Engineering

Sample Paper – 7

Duration: 128 Minutes

Maximum Marks: 72


Instructions

- This paper contains **46 questions** covering the core **Electronics and Communication Engineering** subject of the GATE paper conducted by the IITs and IISc (General Aptitude and Engineering Mathematics are provided as separate papers).
- **Q1–Q20 carry 1 mark each and Q21–Q46 carry 2 marks each**, for a total of **72 marks**.
- Each question carries **negative marking of one-third of its allotted marks**: a wrong 1-mark question costs **0.33** and a wrong 2-mark question costs **0.67**. Unattempted questions carry no penalty.
- Every question here is a single-correct **MCQ**. The real GATE paper also has Multiple Select (MSQ) and Numerical Answer Type (NAT) questions, and **those carry no negative marking**.
- Attempt this paper in one timed sitting of about **128 minutes**, the share this core subject earns at GATE's overall pace of 180 minutes for 65 questions. Unless stated otherwise take $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ for silicon, thermal voltage $V_T = 25 \text{ mV}$ at room temperature, $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$, $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$ and $c = 3 \times 10^8 \text{ m/s}$.

Networks and Circuit Analysis

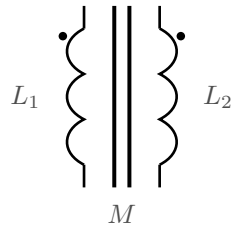
- Q1.** Two magnetically coupled coils have self-inductances $L_1 = 2 \text{ H}$ and $L_2 = 8 \text{ H}$ and a mutual inductance $M = 3 \text{ H}$, as shown by the dot markings. The coefficient of coupling $k = M/\sqrt{L_1 L_2}$ is: [1 mark]






- (A) 0.375
- (B) 0.5
- (C) 0.75
- (D) 1.0

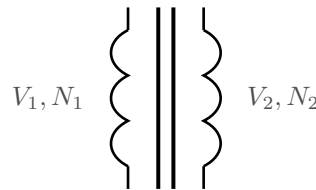Q2. An ideal transformer has primary and secondary turns $N_1 = 200$ and $N_2 = 1000$, as shown. If the primary is driven by $V_1 = 12$ V, the secondary voltage $V_2 = V_1(N_2/N_1)$ is: [1 mark]



- (A) 2.4 V
- (B) 12 V
- (C) 6 V
- (D) 60 V

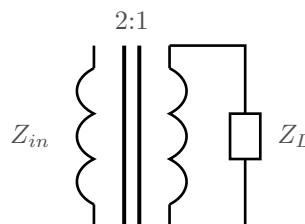Q3. An ideal transformer with turns ratio $N_1 : N_2 = 2 : 1$ is terminated in a load $Z_L = 100 \Omega$ on its secondary, as shown. The impedance Z_{in} seen at the primary, $Z_{in} = (N_1/N_2)^2 Z_L$, is: [1 mark]




- (A) 25Ω
- (B) 100Ω



(C) $400\ \Omega$

(D) $50\ \Omega$

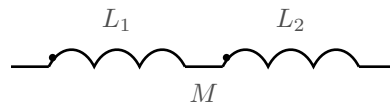- Q4.** Two series-connected coupled coils are wound so that their fluxes aid (dots at the same end), as shown. With $L_1 = 3\text{ H}$, $L_2 = 5\text{ H}$ and $M = 2\text{ H}$, the equivalent inductance $L_{eq} = L_1 + L_2 + 2M$ is: [1 mark]



(A) 8 H

(B) 12 H

(C) 4 H

(D) 10 H

- Q5.** The same two coils of the previous type are now connected in series-opposing (one dot reversed). With $L_1 = 6\text{ H}$, $L_2 = 4\text{ H}$ and $M = 3\text{ H}$, the equivalent inductance $L_{eq} = L_1 + L_2 - 2M$ is: [1 mark]

(A) 16 H

(B) 4 H

(C) 10 H

(D) 7 H

- Q6.** An ideal transformer is used to match a source of internal resistance $R_s = 50\ \Omega$ to a load $R_L = 8\ \Omega$ for maximum power transfer. The required turns ratio $N_1 : N_2 = \sqrt{R_s/R_L}$ is nearest to: [1 mark]

(A) 6.25


(B) 0.4

(C) 1.25

(D) 2.5



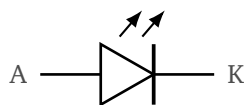
- Q7.** A light-emitting diode (LED) is fabricated from a direct-gap semiconductor of band gap $E_g = 2.0$ eV, as symbolised below. The peak wavelength of the emitted light, $\lambda = 1240/E_g(\text{eV})$ nm, is nearest to: [1 mark]



- (A) 1240 nm
(B) 248 nm
(C) 310 nm
(D) 620 nm
- Q8.** A silicon solar cell has open-circuit voltage $V_{oc} = 0.5$ V, short-circuit current $I_{sc} = 35$ mA, and at its maximum-power point $V_{mp} = 0.4$ V, $I_{mp} = 30$ mA. The fill factor $FF = (V_{mp}I_{mp})/(V_{oc}I_{sc})$ is nearest to: [1 mark]

- (A) 0.50
(B) 0.686
(C) 0.343
(D) 0.857

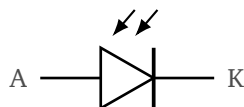- Q9.** A reverse-biased photodiode (symbol shown) receives an optical power of 2 mW and produces a photocurrent of 0.9 mA. Its responsivity $R = I_{ph}/P_{opt}$ is: [1 mark]



- (A) 0.9 A/W
(B) 2.22 A/W
(C) 0.45 A/W
(D) 0.18 A/W
- Q10.** A photodiode has a responsivity of $R = 0.5$ A/W at an operating wavelength of $\lambda = 800$ nm. Using $\eta = R(1.24/\lambda_{\mu\text{m}})$ with λ in micrometres, the external quantum efficiency η is nearest to: [1 mark]




- (A) 0.50
- (B) 0.775
- (C) 0.62
- (D) 1.00

Q11. A silicon photodetector must respond to photons whose energy exceeds the band gap $E_g = 1.1$ eV. The longest wavelength it can detect (the cut-off wavelength), $\lambda_c = 1240/E_g(\text{eV})$ nm, is nearest to: [1 mark]

- (A) $0.55 \mu\text{m}$
- (B) $1.13 \mu\text{m}$
- (C) $2.26 \mu\text{m}$
- (D) $0.89 \mu\text{m}$

Analog Circuits

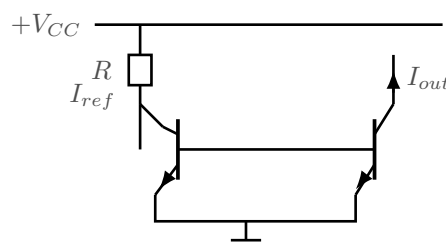Q12. In the basic BJT current mirror shown, the reference resistor $R = 93 \text{ k}\Omega$ is tied from $V_{CC} = 10 \text{ V}$ to the diode-connected transistor ($V_{BE} = 0.7 \text{ V}$). Neglecting base currents, the output (mirrored) current $I_{out} \approx I_{ref} = (V_{CC} - V_{BE})/R$ is: [1 mark]



- (A) 1 mA
- (B) $10 \mu\text{A}$
- (C) $50 \mu\text{A}$
- (D) $100 \mu\text{A}$


Q13. The output transistor of a current mirror has an Early voltage $V_A = 50 \text{ V}$ and carries a collector current $I_C = 0.5 \text{ mA}$. Its small-signal output



resistance $r_o = V_A/I_C$ (which sets the mirror's output resistance) is: [1 mark]


- (A) 25 k Ω
- (B) 50 k Ω
- (C) 100 k Ω
- (D) 250 k Ω

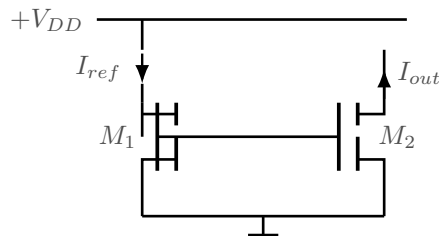Q14. In the MOSFET current mirror shown, both devices share the same V_{GS} , and the output transistor has an aspect ratio four times that of the reference transistor. With $I_{ref} = 100 \mu\text{A}$, the output current $I_{out} = (W/L)_2/(W/L)_1 \times I_{ref}$ is: [1 mark]



- (A) 25 μA
- (B) 100 μA
- (C) 200 μA
- (D) 400 μA

Q15. A common-source amplifier uses an ideal current source as an active load, as shown. The transistor has $g_m = 1 \text{ mA/V}$ and output resistance $r_{on} = 100 \text{ k}\Omega$, and the load presents $r_{op} = 100 \text{ k}\Omega$. The small-signal gain magnitude $|A_v| = g_m(r_{on} \parallel r_{op})$ is: [1 mark]

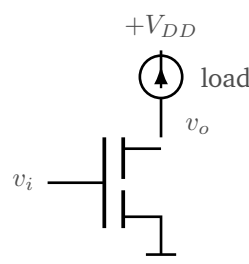

- (A) 50



- (B) 100
- (C) 25
- (D) 10

Q16. A cascode current mirror boosts the output resistance to $R_{out} \approx g_m r_o^2$. Taking $g_m = 2 \text{ mA/V}$ and $r_o = 100 \text{ k}\Omega$ for the cascode device, the output resistance is nearest to: [1 mark]

- (A) $100 \text{ k}\Omega$
- (B) $20 \text{ M}\Omega$
- (C) $200 \text{ k}\Omega$
- (D) $2 \text{ M}\Omega$

Q17. In a basic two-transistor BJT current mirror the finite current gain β introduces a base-current error, giving $I_{out}/I_{ref} = 1/(1 + 2/\beta)$. For $\beta = 100$ and $I_{ref} = 1 \text{ mA}$, the output current is nearest to: [1 mark]

- (A) 1.00 mA
- (B) 1.02 mA
- (C) 0.50 mA
- (D) 0.98 mA

Q18. A common-source amplifier loaded by a current-source (active) load has a small-signal voltage gain magnitude $|A_v| = g_m r_o$, where r_o is the net output resistance. With $g_m = 5 \text{ mA/V}$ and $r_o = 40 \text{ k}\Omega$, the gain magnitude is: [1 mark]

- (A) 50
- (B) 200
- (C) 100
- (D) 40




Q19. A ring counter is built by connecting flip-flops in a loop so that a single 1 circulates through them. The number of distinct states of a 4-flip-flop ring counter is: [1 mark]

- (A) 4
- (B) 16
- (C) 8
- (D) 2

Q20. A Johnson (twisted-ring) counter feeds the complemented output of the last flip-flop back to the first. The number of distinct states of a 4-flip-flop Johnson counter, $2n$, is: [1 mark]

- (A) 8
- (B) 4
- (C) 16
- (D) 3

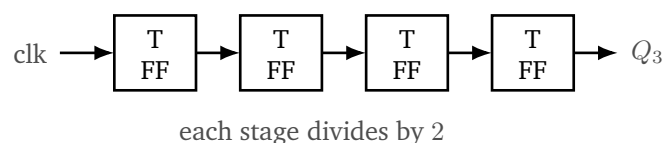Q21. Four negative-edge-triggered T flip-flops (each with $T = 1$) are cascaded so that each one clocks the next, as shown. If the input clock frequency is 16 kHz, the frequency at the output of the last flip-flop is: [2 marks]




- (A) 4 kHz
- (B) 16 kHz
- (C) 1 kHz
- (D) 8 kHz

Q22. A finite-state machine (Mealy type) requires 5 distinct internal states. Using binary state encoding, the minimum number of flip-flops needed is $\lceil \log_2 5 \rceil$, which equals: [2 marks]



- (A) 3
- (B) 5
- (C) 2
- (D) 4

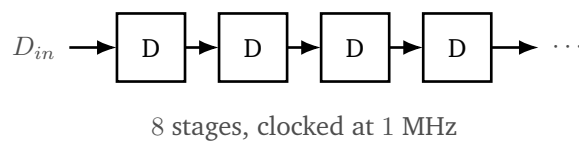Q23. A serial-in serial-out shift register is made of 8 flip-flops, as shown; a data bit entering the input appears at the output after passing through all stages. If the shift clock runs at 1 MHz, the input-to-output delay is:
[2 marks]



- (A) $8 \mu s$
- (B) $1 \mu s$
- (C) $16 \mu s$
- (D) $4 \mu s$

Q24. A synchronous counter uses 5 flip-flops. The maximum number of distinct states it can pass through, 2^5 , is:
[2 marks]

- (A) 10
- (B) 32
- (C) 5
- (D) 25

Signals and Systems

Q25. Two finite-length discrete sequences of lengths 5 and 4 samples are linearly convolved. The length of the resulting sequence, $N_1 + N_2 - 1$, is:[2 marks]

- (A) 8



- (B) 9
- (C) 20
- (D) 5

Q26. Two discrete sequences $x[n] = \{1, 2, 3\}$ and $h[n] = \{1, 1\}$ are convolved. The sum of all samples of the output equals the product of the two sample sums, $(\sum x)(\sum h)$, which is: [2 marks]

- (A) 6
- (B) 12
- (C) 5
- (D) 36

Q27. A 4-point DFT is taken of the unit impulse sequence $x[n] = \delta[n] = \{1, 0, 0, 0\}$. The value of the DFT coefficient $X[3]$ is: [2 marks]

- (A) 0
- (B) 4
- (C) 1
- (D) N

Q28. A 4-point DFT is taken of the constant sequence $x[n] = \{1, 1, 1, 1\}$. The zero-frequency (d.c.) coefficient $X[0] = \sum_{n=0}^3 x[n]$ is: [2 marks]


- (A) 4
- (B) 0
- (C) 1
- (D) 16

Q29. The linear convolution of two length-6 sequences is to be computed exactly using an N -point circular convolution (DFT method). The minimum DFT length N that avoids time-domain aliasing, $N \geq N_1 + N_2 - 1$, is: [2 marks]



- (A) 6
- (B) 12
- (C) 36
- (D) 11

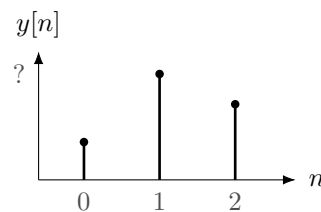Q30. The sequences $x[n] = \{1, 2\}$ and $h[n] = \{3, 4\}$ (both starting at $n = 0$) are linearly convolved to give $y[n]$. The stem plot form of the result is indicated. The sample $y[1]$ is: [2 marks]



- (A) 10
- (B) 3
- (C) 8
- (D) 11

Control Systems

Q31. A linear system is described in state-space form with system matrix $A = \begin{bmatrix} 0 & 1 \\ -6 & -5 \end{bmatrix}$. The eigenvalues of A (equal to the system poles) are: [2 marks]

- (A) $\{+2, +3\}$
- (B) $\{-5, -6\}$
- (C) $\{0, -5\}$
- (D) $\{-2, -3\}$

Q32. A second-order system has state matrix $A = \begin{bmatrix} 0 & 1 \\ 0 & -2 \end{bmatrix}$ and input matrix $B = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$. From the controllability matrix $Q_c = [B \ AB]$ with $\det Q_c \neq 0$, the system is: [2 marks]



- (A) unstable
- (B) uncontrollable
- (C) controllable
- (D) marginally stable

Q33. A single-input single-output system has the scalar state-space model $\dot{x} = -2x + u$, $y = 3x$ (so $A = -2$, $B = 1$, $C = 3$, $D = 0$). Its transfer function is $H(s) = C(sI - A)^{-1}B = 3/(s + 2)$. The d.c. gain $H(0)$ is: [2 marks]

- (A) 3
- (B) 0.5
- (C) 1.5
- (D) 2

Q34. A system has state matrix $A = \begin{bmatrix} 0 & 1 \\ -8 & -4 \end{bmatrix}$. Comparing its characteristic equation $s^2 + 4s + 8 = 0$ with $s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$, the undamped natural frequency $\omega_n = \sqrt{8}$ is nearest to: [2 marks]

- (A) 8 rad/s
- (B) 4 rad/s
- (C) 2 rad/s
- (D) 2.83 rad/s

Q35. A system has state matrix $A = \begin{bmatrix} 0 & 1 \\ -2 & -3 \end{bmatrix}$ and output matrix $C = [1 \ 0]$. From the observability matrix $Q_o = \begin{bmatrix} C \\ CA \end{bmatrix}$ with $\det Q_o \neq 0$, the system is: [2 marks]

- (A) unobservable
- (B) unstable
- (C) observable
- (D) uncontrollable




Communications

Q36. A discrete memoryless source emits three symbols with probabilities $\{0.5, 0.25, 0.25\}$. Its entropy $H = -\sum p_i \log_2 p_i$ is: [2 marks]

- (A) 1.5 bits/symbol
- (B) 2.0 bits/symbol
- (C) 1.0 bit/symbol
- (D) 3.0 bits/symbol

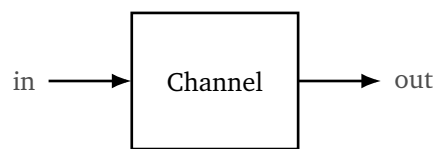Q37. A channel of bandwidth $B = 4$ kHz has a signal-to-noise ratio of 15 (power ratio). By the Shannon–Hartley law $C = B \log_2(1 + \text{SNR})$, the channel capacity is: [2 marks]



$B = 4$ kHz, $\text{SNR} = 15$

- (A) 4 kbps
- (B) 32 kbps
- (C) 8 kbps
- (D) 16 kbps

Q38. In a message from a discrete source, one particular symbol occurs with probability 0.125. The self-information (information content) it carries, $I = \log_2(1/p)$, is: [2 marks]

- (A) 3 bits
- (B) 8 bits
- (C) 0.125 bits
- (D) 1 bit

Q39. A discrete memoryless source emits 16 symbols that are all equally likely. The maximum entropy of the source, $\log_2 16$, is: [2 marks]



- (A) 4 bits/symbol
- (B) 16 bits/symbol
- (C) 8 bits/symbol
- (D) 2 bits/symbol

Q40. A channel of bandwidth $B = 1$ kHz has a signal-to-noise ratio of 3 (power ratio). By the Shannon–Hartley law $C = B \log_2(1 + \text{SNR})$, the channel capacity is: [2 marks]


- (A) 1 kbps
- (B) 2 kbps
- (C) 4 kbps
- (D) 3 kbps

Q41. A source of entropy $H = 1.5$ bits/symbol is encoded with a code whose average codeword length is $L = 2$ bits/symbol. The coding efficiency $\eta = H/L$ is: [2 marks]

- (A) 0.50
- (B) 1.00
- (C) 0.75
- (D) 0.60

Electromagnetics

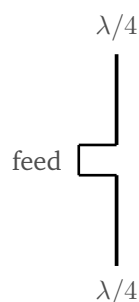Q42. A thin half-wave dipole antenna (length $\lambda/2$), fed at its centre as shown, is a standard reference radiator. Its radiation resistance (input resistance at resonance) is closest to: [2 marks]



- (A) 73Ω
- (B) 377Ω
- (C) 50Ω
- (D) 36.5Ω

Q43. An antenna has a directivity $D = 20$ (dimensionless) and a radiation efficiency $\eta = 0.5$. Its power gain $G = \eta D$ is: [2 marks]

- (A) 20
- (B) 40
- (C) 10
- (D) 0.5

Q44. A half-wave dipole antenna is designed to operate at a frequency of 300 MHz in free space. Its physical length ($\lambda/2$, with $\lambda = c/f$) is: [2 marks]

- (A) 1 m
- (B) 0.5 m
- (C) 0.25 m
- (D) 2 m

Q45. A short (Hertzian) dipole of length dl radiates with radiation resistance $R_r = 80\pi^2(dl/\lambda)^2$. For a dipole whose length is $dl/\lambda = 0.01$, the radiation resistance is nearest to: [2 marks]

- (A) 73Ω
- (B) 0.79Ω
- (C) 7.9Ω
- (D) 0.079Ω

Q46. An antenna has a directivity $D = 4$ (dimensionless). Expressed in decibels relative to an isotropic radiator, $D_{\text{dBi}} = 10 \log_{10} D$, its directivity is nearest to: [2 marks]



- (A) 4 dBi
- (B) 6 dBi
- (C) 16 dBi
- (D) 2 dBi



Detailed Solutions

Q1.

Solution

Concept – coefficient of coupling: The coefficient of coupling links the mutual inductance to the two self-inductances by $k = \frac{M}{\sqrt{L_1 L_2}}$, and it always lies between 0 and 1.

Step 1 – list the data: $L_1 = 2 \text{ H}$, $L_2 = 8 \text{ H}$, $M = 3 \text{ H}$.

Step 2 – form the product of the self-inductances: $L_1 L_2 = 2 \times 8 = 16$

Step 3 – take the square root: $\sqrt{L_1 L_2} = \sqrt{16} = 4$

Step 4 – divide the mutual inductance by this root: $k = \frac{3}{4}$

$$k = 0.75$$

Step 5 – sanity check: The value 0.75 lies between 0 and 1, so it is a physically valid coupling.

Final Answer: $k = 0.75 \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q1](#)

Q2.

Solution

Concept – ideal transformer voltage ratio: In an ideal transformer voltages scale with the turns, $\frac{V_2}{V_1} = \frac{N_2}{N_1}$.

Step 1 – list the data: $N_1 = 200$, $N_2 = 1000$, $V_1 = 12 \text{ V}$.

Step 2 – form the turns ratio: $\frac{N_2}{N_1} = \frac{1000}{200} = 5$

Step 3 – multiply the primary voltage by this ratio: $V_2 = 12 \times 5$

Step 4 – evaluate: $V_2 = 60 \text{ V}$

Why the other options are wrong:

- A, 2.4 V: divides instead of multiplies (uses N_1/N_2).
- C, 6 V: halves the primary voltage, unrelated to the turns.

Final Answer: $V_2 = 60 \text{ V} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q2](#)



Q3.

Solution

Concept – impedance reflection through an ideal transformer: An impedance on the secondary is seen at the primary scaled by the square of the turns ratio, $Z_{in} = \left(\frac{N_1}{N_2}\right)^2 Z_L$.

Step 1 – list the data: $\frac{N_1}{N_2} = 2$, $Z_L = 100 \Omega$.

Step 2 – square the turns ratio: $\left(\frac{N_1}{N_2}\right)^2 = 2^2 = 4$

Step 3 – multiply by the load: $Z_{in} = 4 \times 100$

Step 4 – evaluate: $Z_{in} = 400 \Omega$

Final Answer: $Z_{in} = 400 \Omega \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q3](#)

Q4.

Solution

Concept – series-aiding coupled coils: When two coupled coils are in series with their fluxes aiding, the mutual term adds, $L_{eq} = L_1 + L_2 + 2M$.

Step 1 – list the data: $L_1 = 3 \text{ H}$, $L_2 = 5 \text{ H}$, $M = 2 \text{ H}$.

Step 2 – add the self-inductances: $L_1 + L_2 = 3 + 5 = 8$

Step 3 – form the mutual term: $2M = 2 \times 2 = 4$

Step 4 – add for the aiding connection: $L_{eq} = 8 + 4$

$L_{eq} = 12 \text{ H}$

Final Answer: $L_{eq} = 12 \text{ H} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q4](#)

Q5.

Solution

Concept – series-opposing coupled coils: When the two coupled coils are connected so their fluxes oppose, the mutual term subtracts, $L_{eq} = L_1 + L_2 - 2M$.

Step 1 – list the data: $L_1 = 6 \text{ H}$, $L_2 = 4 \text{ H}$, $M = 3 \text{ H}$.

Step 2 – add the self-inductances: $L_1 + L_2 = 6 + 4 = 10$

Step 3 – form the mutual term: $2M = 2 \times 3 = 6$



Step 4 – subtract for the opposing connection: $L_{eq} = 10 - 6$

$$L_{eq} = 4 \text{ H}$$

Final Answer: $L_{eq} = 4 \text{ H} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q5](#)

Q6.

Solution

Concept – impedance matching with an ideal transformer: The transformer reflects the load as $R_s = (N_1/N_2)^2 R_L$, so the matching turns ratio is $\frac{N_1}{N_2} = \sqrt{\frac{R_s}{R_L}}$.

Step 1 – list the data: $R_s = 50 \Omega$, $R_L = 8 \Omega$.

Step 2 – form the resistance ratio: $\frac{R_s}{R_L} = \frac{50}{8} = 6.25$

Step 3 – take the square root: $\frac{N_1}{N_2} = \sqrt{6.25}$

Step 4 – evaluate: $\frac{N_1}{N_2} = 2.5$

Why the other options are wrong:

- A, 6.25: is the resistance ratio itself, before taking the square root.
- B, 0.4: is the reciprocal N_2/N_1 .

Final Answer: $N_1 : N_2 = 2.5 \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q6](#)

Q7.

Solution

Concept – photon energy and emission wavelength of an LED: The emitted photon energy equals the band gap, and wavelength and energy are related by $\lambda(\text{nm}) = \frac{1240}{E_g(\text{eV})}$.

Step 1 – list the data: $E_g = 2.0 \text{ eV}$.

Step 2 – substitute into the relation: $\lambda = \frac{1240}{2.0}$

Step 3 – evaluate: $\lambda = 620 \text{ nm}$

Step 4 – interpret: 620 nm lies in the red part of the visible spectrum, consistent with a 2.0 eV LED.



Final Answer: $\lambda = 620 \text{ nm} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q7](#)

Q8.

Solution

Concept – fill factor of a solar cell: The fill factor compares the maximum-power-point product with the product of open-circuit voltage and short-circuit current, $FF = \frac{V_{mp}I_{mp}}{V_{oc}I_{sc}}$.

Step 1 – form the maximum-power-point product: $V_{mp}I_{mp} = 0.4 \times 30 \text{ mW} = 12 \text{ mW}$

Step 2 – form the reference product: $V_{oc}I_{sc} = 0.5 \times 35 \text{ mW} = 17.5 \text{ mW}$

Step 3 – divide: $FF = \frac{12}{17.5}$

Step 4 – evaluate: $FF = 0.686$

Final Answer: $FF \approx 0.686 \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q8](#)

Q9.

Solution

Concept – responsivity of a photodiode: Responsivity is the photocurrent generated per unit of incident optical power, $R = \frac{I_{ph}}{P_{opt}}$.

Step 1 – list the data: $I_{ph} = 0.9 \text{ mA} = 0.9 \times 10^{-3} \text{ A}$, $P_{opt} = 2 \text{ mW} = 2 \times 10^{-3} \text{ W}$.

Step 2 – form the ratio: $R = \frac{0.9 \times 10^{-3}}{2 \times 10^{-3}}$

Step 3 – cancel the powers of ten: $R = \frac{0.9}{2}$

Step 4 – evaluate: $R = 0.45 \text{ A/W}$

Final Answer: $R = 0.45 \text{ A/W} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q9](#)



Q10.

Solution

Concept – quantum efficiency from responsivity: The external quantum efficiency and responsivity are related by $R = \frac{\eta \lambda_{\mu\text{m}}}{1.24}$, so $\eta = R \frac{1.24}{\lambda_{\mu\text{m}}}$.

Step 1 – convert the wavelength to micrometres: $\lambda = 800 \text{ nm} = 0.8 \mu\text{m}$

Step 2 – form the factor $1.24/\lambda$: $\frac{1.24}{0.8} = 1.55$

Step 3 – multiply by the responsivity: $\eta = 0.5 \times 1.55$

Step 4 – evaluate: $\eta = 0.775$

Step 5 – interpret: $\eta = 0.775$ means about 77.5% of the incident photons produce collected carriers, a valid value below unity.

Final Answer: $\eta \approx 0.775 \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q10](#)

Q11.

Solution

Concept – cut-off wavelength of a photodetector: A photon is absorbed only if its energy exceeds the band gap; the longest detectable wavelength corresponds to $E = E_g$, giving $\lambda_c(\text{nm}) = \frac{1240}{E_g(\text{eV})}$.

Step 1 – list the data: $E_g = 1.1 \text{ eV}$.

Step 2 – substitute: $\lambda_c = \frac{1240}{1.1}$

Step 3 – evaluate: $\lambda_c = 1127 \text{ nm}$

Step 4 – convert to micrometres: $\lambda_c = 1.13 \mu\text{m}$

Final Answer: $\lambda_c \approx 1.13 \mu\text{m} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q11](#)

Q12.

Solution

Concept – basic BJT current mirror: The diode-connected transistor sets a reference current $I_{ref} = \frac{V_{CC} - V_{BE}}{R}$, and the matched output transistor copies it, $I_{out} \approx I_{ref}$.

Step 1 – form the numerator (voltage across R): $V_{CC} - V_{BE} = 10 - 0.7 = 9.3 \text{ V}$

Step 2 – write the resistance: $R = 93 \text{ k}\Omega = 93 \times 10^3 \Omega$



Step 3 – divide: $I_{ref} = \frac{9.3}{93 \times 10^3}$

Step 4 – evaluate: $I_{ref} = 0.1 \times 10^{-3} \text{ A} = 100 \text{ } \mu\text{A}$

Step 5 – copy through the mirror: $I_{out} \approx I_{ref} = 100 \text{ } \mu\text{A}$

Final Answer: $I_{out} \approx 100 \text{ } \mu\text{A} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q12](#)

Q13.

Solution

Concept – output resistance of the mirror transistor: The Early effect gives the small-signal output resistance $r_o = \frac{V_A}{I_C}$.

Step 1 – list the data: $V_A = 50 \text{ V}$, $I_C = 0.5 \text{ mA} = 0.5 \times 10^{-3} \text{ A}$.

Step 2 – divide: $r_o = \frac{50}{0.5 \times 10^{-3}}$

Step 3 – simplify the division: $r_o = \frac{50}{0.5} \times 10^3$

$r_o = 100 \times 10^3 \text{ } \Omega$

Step 4 – express in kilo-ohms: $r_o = 100 \text{ k}\Omega$

Final Answer: $r_o = 100 \text{ k}\Omega \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q13](#)

Q14.

Solution

Concept – ratioed MOSFET current mirror: Two MOSFETs sharing the same V_{GS} carry currents in proportion to their aspect ratios, $\frac{I_{out}}{I_{ref}} = \frac{(W/L)_2}{(W/L)_1}$.

Step 1 – read the aspect-ratio scaling: $\frac{(W/L)_2}{(W/L)_1} = 4$

Step 2 – write the reference current: $I_{ref} = 100 \text{ } \mu\text{A}$

Step 3 – multiply: $I_{out} = 4 \times 100 \text{ } \mu\text{A}$

Step 4 – evaluate: $I_{out} = 400 \text{ } \mu\text{A}$

Final Answer: $I_{out} = 400 \text{ } \mu\text{A} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q14](#)



Q15.

Solution

Concept – gain of a common-source stage with an active load: The gain magnitude is the transconductance times the total resistance at the output node, $|A_v| = g_m(r_{on} \parallel r_{op})$.

Step 1 – combine the two output resistances in parallel: $r_{on} \parallel r_{op} = \frac{100 \times 100}{100 + 100} \text{ k}\Omega$

Step 2 – evaluate the parallel combination: $r_{on} \parallel r_{op} = \frac{10000}{200} \text{ k}\Omega = 50 \text{ k}\Omega$

Step 3 – multiply by the transconductance: $|A_v| = (1 \text{ mA/V}) \times (50 \text{ k}\Omega)$

Step 4 – evaluate (mA times kΩ is dimensionless): $|A_v| = 1 \times 10^{-3} \times 50 \times 10^3$
 $|A_v| = 50$

Final Answer: $|A_v| = 50 \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q15](#)

Q16.

Solution

Concept – output resistance of a cascode mirror: Cascoding multiplies the plain output resistance by roughly the intrinsic gain, $R_{out} \approx g_m r_o \cdot r_o = g_m r_o^2$.

Step 1 – square the transistor output resistance: $r_o^2 = (100 \times 10^3)^2 = 1 \times 10^{10} \Omega^2$

Step 2 – multiply by the transconductance: $R_{out} = (2 \times 10^{-3}) \times (1 \times 10^{10})$

Step 3 – combine the powers of ten: $R_{out} = 2 \times 10^7 \Omega$

Step 4 – express in mega-ohms: $R_{out} = 20 \text{ M}\Omega$

Step 5 – interpret: This is 200 times the plain $r_o = 100 \text{ k}\Omega$, which is exactly why cascoding is used to make near-ideal current sources.

Final Answer: $R_{out} \approx 20 \text{ M}\Omega \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q16](#)

Q17.

Solution

Concept – base-current error of a two-transistor mirror: The two base currents are drawn from the reference branch, giving $\frac{I_{out}}{I_{ref}} = \frac{1}{1 + 2/\beta}$.



Step 1 – form the correction term: $\frac{2}{\beta} = \frac{2}{100} = 0.02$

Step 2 – form the denominator: $1 + 0.02 = 1.02$

Step 3 – take the ratio: $\frac{I_{out}}{I_{ref}} = \frac{1}{1.02} = 0.9804$

Step 4 – multiply by the reference current: $I_{out} = 0.9804 \times 1 \text{ mA}$

$$I_{out} = 0.98 \text{ mA}$$

Final Answer: $I_{out} \approx 0.98 \text{ mA} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q17](#)

Q18.

Solution

Concept – gain of a common-source stage with a current-source load: The intrinsic gain magnitude is $|A_v| = g_m r_o$.

Step 1 – list the data: $g_m = 5 \text{ mA/V} = 5 \times 10^{-3} \text{ A/V}$, $r_o = 40 \text{ k}\Omega = 40 \times 10^3 \Omega$.

Step 2 – multiply: $|A_v| = (5 \times 10^{-3}) \times (40 \times 10^3)$

Step 3 – combine the powers of ten: $|A_v| = 5 \times 40 = 200$

Final Answer: $|A_v| = 200 \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q18](#)

Q19.

Solution

Concept – states of a ring counter: In a ring counter a single 1 (or 0) is circulated through the n flip-flops, so it visits exactly n distinct states before repeating.

Step 1 – read the number of flip-flops: $n = 4$.

Step 2 – apply the ring-counter state count: number of states = $n = 4$

Why the other options are wrong:

- B, 16: is 2^4 , the count for a full binary counter, not a ring counter.
- C, 8: is $2n$, the count for a Johnson counter.

Final Answer: 4 states $\Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q19](#)



Q20.

Solution

Concept – states of a Johnson counter: Feeding back the complement of the last flip-flop makes the pattern fill and then empty, giving $2n$ distinct states for n flip-flops.

Step 1 – read the number of flip-flops: $n = 4$.

Step 2 – apply the Johnson-counter state count: number of states $= 2n = 2 \times 4$

Step 3 – evaluate: number of states $= 8$

Final Answer: 8 states $\Rightarrow$ **A**

Answer: (A) [Go Back to Q20](#)

Q21.

Solution

Concept – frequency division by cascaded toggle flip-flops: Each T flip-flop with $T = 1$ toggles once per input edge, dividing the frequency by 2. A chain of m such stages divides by 2^m .

Step 1 – read the number of stages: $m = 4$.

Step 2 – form the total division factor: $2^m = 2^4 = 16$

Step 3 – divide the input frequency: $f_{out} = \frac{16 \text{ kHz}}{16}$

Step 4 – evaluate: $f_{out} = 1 \text{ kHz}$

Final Answer: $f_{out} = 1 \text{ kHz} \Rightarrow$ **C**

Answer: (C) [Go Back to Q21](#)

Q22.

Solution

Concept – minimum flip-flops for a state machine: With binary encoding, k flip-flops give 2^k states, so the minimum number for N states is $k = \lceil \log_2 N \rceil$.

Step 1 – list the data: $N = 5$ states.

Step 2 – take the base-2 logarithm: $\log_2 5 = 2.32$

Step 3 – round up to the next integer: $k = \lceil 2.32 \rceil = 3$

Step 4 – verify: $2^3 = 8 \geq 5$, while $2^2 = 4 < 5$, so 3 is indeed the minimum.

Final Answer: $k = 3$ flip-flops $\Rightarrow$ **A**



Answer: (A) [Go Back to Q22](#)

Q23.

Solution

Concept – delay through a shift register: A bit advances one flip-flop per clock period, so passing through m stages takes m clock periods, a delay of $t_d = m T_{clk} = m/f_{clk}$.

Step 1 – find the clock period: $T_{clk} = \frac{1}{f_{clk}} = \frac{1}{1 \times 10^6} = 1 \mu s$

Step 2 – read the number of stages: $m = 8$.

Step 3 – multiply: $t_d = 8 \times 1 \mu s$

Step 4 – evaluate: $t_d = 8 \mu s$

Final Answer: $t_d = 8 \mu s \Rightarrow \boxed{A}$

Answer: (A) [Go Back to Q23](#)

Q24.

Solution

Concept – maximum states of a binary counter: With n flip-flops the counter has 2^n distinct binary combinations, which is the largest possible modulus.

Step 1 – read the number of flip-flops: $n = 5$.

Step 2 – raise two to that power: $2^5 = 32$

Why the other options are wrong:

- A, 10: would be a decade (mod-10) count, not the maximum.
- D, 25: confuses 5^2 with 2^5 .

Final Answer: 32 states $\Rightarrow \boxed{B}$

Answer: (B) [Go Back to Q24](#)



Q25.

Solution

Concept – length of a linear convolution: The convolution of sequences of lengths N_1 and N_2 has length $N_1 + N_2 - 1$.

Step 1 – list the data: $N_1 = 5, N_2 = 4$.

Step 2 – add the lengths: $N_1 + N_2 = 5 + 4 = 9$

Step 3 – subtract one: length = $9 - 1$

Step 4 – evaluate: length = 8

Final Answer: 8 samples $\Rightarrow$ **A**

Answer: (A) [Go Back to Q25](#)

Q26.

Solution

Concept – sum of a convolution: Summing all samples of $y = x * h$ gives the product of the individual sums, $\sum_n y[n] = (\sum_n x[n])(\sum_n h[n])$.

Step 1 – sum the first sequence: $\sum x = 1 + 2 + 3 = 6$

Step 2 – sum the second sequence: $\sum h = 1 + 1 = 2$

Step 3 – multiply the two sums: $\sum y = 6 \times 2$

Step 4 – evaluate: $\sum y = 12$

Step 5 – cross-check by direct convolution: $y = \{1, 3, 5, 3\}$, and $1+3+5+3 = 12$, which agrees.

Final Answer: $\sum y = 12 \Rightarrow$ **B**

Answer: (B) [Go Back to Q26](#)

Q27.

Solution

Concept – DFT of a unit impulse: The N -point DFT is $X[k] = \sum_{n=0}^{N-1} x[n] e^{-j2\pi kn/N}$. For $x[n] = \delta[n]$ only the $n = 0$ term survives.

Step 1 – write the DFT sum for $k = 3, N = 4$: $X[3] = \sum_{n=0}^3 \delta[n] e^{-j2\pi \cdot 3 \cdot n/4}$

Step 2 – keep only the non-zero sample ($n = 0$): $X[3] = \delta[0] e^{-j2\pi \cdot 3 \cdot 0/4}$

Step 3 – evaluate the exponential at $n = 0$: $e^0 = 1$

Step 4 – combine: $X[3] = 1 \times 1 = 1$



Step 5 – interpret: The DFT of an impulse is flat (all coefficients equal 1), so every $X[k] = 1$.

Final Answer: $X[3] = 1 \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q27](#)

Q28.

Solution

Concept – d.c. coefficient of the DFT: The zero-frequency coefficient is just the sum of the samples, $X[0] = \sum_{n=0}^{N-1} x[n]$.

Step 1 – write the samples: $x[n] = \{1, 1, 1, 1\}$.

Step 2 – add them: $X[0] = 1 + 1 + 1 + 1$

Step 3 – evaluate: $X[0] = 4$

Step 4 – interpret: A constant sequence has energy only at d.c., so $X[0] = 4$ while $X[1] = X[2] = X[3] = 0$.

Final Answer: $X[0] = 4 \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q28](#)

Q29.

Solution

Concept – avoiding aliasing in DFT-based convolution: N -point circular convolution equals the linear convolution only if N is at least the linear-convolution length $N_1 + N_2 - 1$.

Step 1 – list the data: $N_1 = 6, N_2 = 6$.

Step 2 – add the lengths: $N_1 + N_2 = 6 + 6 = 12$

Step 3 – subtract one: $N_1 + N_2 - 1 = 12 - 1 = 11$

Step 4 – state the minimum DFT length: $N_{\min} = 11$

Final Answer: $N = 11 \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q29](#)



Q30.

Solution

Concept – one output sample of a convolution: The convolution sum is $y[n] = \sum_k x[k] h[n - k]$; the sample $y[1]$ takes the overlapping products at shift 1.

Step 1 – list the sequences: $x = \{x[0], x[1]\} = \{1, 2\}$, $h = \{h[0], h[1]\} = \{3, 4\}$.

Step 2 – write the terms that contribute to $y[1]$: $y[1] = x[0] h[1] + x[1] h[0]$

Step 3 – substitute the values: $y[1] = (1)(4) + (2)(3)$

Step 4 – multiply each product: $y[1] = 4 + 6$

Step 5 – add: $y[1] = 10$

Final Answer: $y[1] = 10 \Rightarrow \boxed{A}$

Answer: (A) [Go Back to Q30](#)

Q31.

Solution

Concept – eigenvalues of the state matrix: The system poles are the eigenvalues of A , found from $\det(sI - A) = 0$.

Step 1 – form $sI - A$: $sI - A = \begin{bmatrix} s & -1 \\ 6 & s + 5 \end{bmatrix}$

Step 2 – take the determinant: $\det(sI - A) = s(s + 5) - (-1)(6)$

Step 3 – expand: $\det(sI - A) = s^2 + 5s + 6$

Step 4 – factor the characteristic polynomial: $s^2 + 5s + 6 = (s + 2)(s + 3)$

Step 5 – read off the roots: $s = -2$ and $s = -3$

Final Answer: eigenvalues $\{-2, -3\} \Rightarrow \boxed{D}$

Answer: (D) [Go Back to Q31](#)

Q32.

Solution

Concept – controllability test: A second-order system is controllable if its controllability matrix $Q_c = [B \ AB]$ is non-singular (its determinant is non-zero).

Step 1 – compute AB : $AB = \begin{bmatrix} 0 & 1 \\ 0 & -2 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 1 \\ -2 \end{bmatrix}$



Step 2 – assemble the controllability matrix: $Q_c = \begin{bmatrix} 0 & 1 \\ 1 & -2 \end{bmatrix}$

Step 3 – take its determinant: $\det Q_c = (0)(-2) - (1)(1) = -1$

Step 4 – apply the test: $\det Q_c = -1 \neq 0$, so Q_c has full rank.

Step 5 – conclude: Full rank means the system is controllable.

Final Answer: controllable $\Rightarrow$

Answer: (C) [Go Back to Q32](#)

Q33.

Solution

Concept – d.c. gain from a state-space model: For $H(s) = C(sI - A)^{-1}B + D$, the d.c. gain is the value at $s = 0$.

Step 1 – write the scalar transfer function: $H(s) = \frac{CB}{s - A} = \frac{3}{s + 2}$

Step 2 – substitute $s = 0$: $H(0) = \frac{3}{0 + 2}$

Step 3 – evaluate: $H(0) = \frac{3}{2}$
 $H(0) = 1.5$

Final Answer: $H(0) = 1.5 \Rightarrow$

Answer: (C) [Go Back to Q33](#)

Q34.

Solution

Concept – natural frequency from the state matrix: The characteristic equation $\det(sI - A) = 0$ is compared with the standard form $s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$, so $\omega_n = \sqrt{\text{constant term}}$.

Step 1 – form the characteristic equation: $\det(sI - A) = s(s+4)+8 = s^2+4s+8 = 0$

Step 2 – identify ω_n^2 : $\omega_n^2 = 8$

Step 3 – take the square root: $\omega_n = \sqrt{8}$

Step 4 – evaluate: $\omega_n = 2.83 \text{ rad/s}$

Step 5 – interpret: The middle term gives $2\zeta\omega_n = 4$, so $\zeta = 4/(2 \times 2.83) = 0.707$, a well-damped system, but the question asks only for ω_n .



Final Answer: $\omega_n \approx 2.83 \text{ rad/s} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q34](#)

Q35.

Solution

Concept – observability test: A second-order system is observable if its observability matrix $Q_o = \begin{bmatrix} C \\ CA \end{bmatrix}$ is non-singular.

Step 1 – compute CA : $CA = [1 \ 0] \begin{bmatrix} 0 & 1 \\ -2 & -3 \end{bmatrix} = [0 \ 1]$

Step 2 – assemble the observability matrix: $Q_o = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$

Step 3 – take its determinant: $\det Q_o = (1)(1) - (0)(0) = 1$

Step 4 – apply the test: $\det Q_o = 1 \neq 0$, so Q_o has full rank.

Step 5 – conclude: Full rank means the system is observable.

Final Answer: observable $\Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q35](#)

Q36.

Solution

Concept – entropy of a discrete source: $H = -\sum_i p_i \log_2 p_i$, with each term measuring the information of a symbol weighted by its probability.

Step 1 – list the probabilities: $p_1 = 0.5, p_2 = 0.25, p_3 = 0.25$.

Step 2 – evaluate each log term: $\log_2(1/0.5) = 1, \log_2(1/0.25) = 2, \log_2(1/0.25) = 2$

Step 3 – weight each by its probability: $0.5 \times 1 = 0.5$

$$0.25 \times 2 = 0.5$$

$$0.25 \times 2 = 0.5$$

Step 4 – add the contributions: $H = 0.5 + 0.5 + 0.5$

$$H = 1.5 \text{ bits/symbol}$$

Final Answer: $H = 1.5 \text{ bits/symbol} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q36](#)



Q37.

Solution

Concept – Shannon–Hartley channel capacity: $C = B \log_2(1 + \text{SNR})$.

Step 1 – list the data: $B = 4 \text{ kHz}$, $\text{SNR} = 15$.

Step 2 – form $1 + \text{SNR}$: $1 + 15 = 16$

Step 3 – take the base-2 logarithm: $\log_2 16 = 4$

Step 4 – multiply by the bandwidth: $C = 4 \text{ kHz} \times 4$

Step 5 – evaluate: $C = 16 \text{ kbps}$

Final Answer: $C = 16 \text{ kbps} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q37](#)

Q38.

Solution

Concept – self-information of a symbol: A symbol of probability p carries $I = \log_2(1/p)$ bits; rarer symbols carry more information.

Step 1 – list the data: $p = 0.125$.

Step 2 – form the reciprocal: $\frac{1}{0.125} = 8$

Step 3 – take the base-2 logarithm: $\log_2 8 = 3$

Step 4 – state the result: $I = 3 \text{ bits}$

Final Answer: $I = 3 \text{ bits} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q38](#)

Q39.

Solution

Concept – maximum entropy of a source: Entropy is maximised when all M symbols are equally likely, giving $H_{\max} = \log_2 M$.

Step 1 – list the data: $M = 16$ equally likely symbols.

Step 2 – take the base-2 logarithm: $\log_2 16 = 4$

Step 3 – state the result: $H_{\max} = 4 \text{ bits/symbol}$

Why the other options are wrong:

- B, 16: is the number of symbols, not its logarithm.



- C, 8: would correspond to $M = 256$.

Final Answer: $H_{\max} = 4$ bits/symbol $\Rightarrow$ A

Answer: (A) [Go Back to Q39](#)

Q40.

Solution

Concept – Shannon–Hartley channel capacity: $C = B \log_2(1 + \text{SNR})$.

Step 1 – list the data: $B = 1$ kHz, $\text{SNR} = 3$.

Step 2 – form $1 + \text{SNR}$: $1 + 3 = 4$

Step 3 – take the base-2 logarithm: $\log_2 4 = 2$

Step 4 – multiply by the bandwidth: $C = 1$ kHz $\times 2$

Step 5 – evaluate: $C = 2$ kbps

Final Answer: $C = 2$ kbps $\Rightarrow$ B

Answer: (B) [Go Back to Q40](#)

Q41.

Solution

Concept – coding efficiency: Efficiency compares the source entropy with the average codeword length, $\eta = \frac{H}{L}$.

Step 1 – list the data: $H = 1.5$ bits/symbol, $L = 2$ bits/symbol.

Step 2 – form the ratio: $\eta = \frac{1.5}{2}$

Step 3 – evaluate: $\eta = 0.75$

Step 4 – interpret: The code uses 2 bits per symbol to carry 1.5 bits of information, so it is 75% efficient with 0.5 bit of redundancy per symbol.

Final Answer: $\eta = 0.75 \Rightarrow$ C

Answer: (C) [Go Back to Q41](#)



Q42.

Solution

Concept – radiation resistance of a half-wave dipole: The centre-fed resonant half-wave dipole is a standard reference antenna with a well-known radiation resistance.

Step 1 – recall the standard result: For an ideal thin half-wave dipole, $R_r \approx 73 \Omega$.

Step 2 – match to the options: The nearest listed value is 73Ω .

Why the other options are wrong:

- B, 377Ω : is the intrinsic impedance of free space, not an antenna's radiation resistance.
- C, 50Ω : is a common feed-line impedance, chosen for a rough match to (but not equal to) the dipole.
- D, 36.5Ω : is the radiation resistance of a quarter-wave monopole over a ground plane, half the dipole value.

Final Answer: $R_r \approx 73 \Omega \Rightarrow \boxed{A}$

Answer: (A) [Go Back to Q42](#)

Q43.

Solution

Concept – gain, directivity and efficiency: An antenna's power gain is its directivity reduced by the radiation efficiency, $G = \eta D$.

Step 1 – list the data: $D = 20$, $\eta = 0.5$.

Step 2 – multiply: $G = 0.5 \times 20$

Step 3 – evaluate: $G = 10$

Step 4 – interpret: Half the power is lost, so the gain is half the directivity.

Final Answer: $G = 10 \Rightarrow \boxed{C}$

Answer: (C) [Go Back to Q43](#)



Q44.

Solution

Concept – physical length of a half-wave dipole: The dipole length is half a free-space wavelength, $\ell = \lambda/2$ with $\lambda = c/f$.

Step 1 – find the wavelength: $\lambda = \frac{c}{f} = \frac{3 \times 10^8}{300 \times 10^6}$

Step 2 – evaluate: $\lambda = 1 \text{ m}$

Step 3 – halve it: $\ell = \frac{1}{2} = 0.5 \text{ m}$

Final Answer: $\ell = 0.5 \text{ m} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q44](#)

Q45.

Solution

Concept – radiation resistance of a short dipole: For a Hertzian (short) dipole, $R_r = 80\pi^2 \left(\frac{dl}{\lambda}\right)^2$.

Step 1 – list the data: $\frac{dl}{\lambda} = 0.01$.

Step 2 – square the length ratio: $\left(\frac{dl}{\lambda}\right)^2 = (0.01)^2 = 1 \times 10^{-4}$

Step 3 – evaluate the constant: $80\pi^2 = 80 \times 9.87 = 789.6$

Step 4 – multiply: $R_r = 789.6 \times 1 \times 10^{-4}$

Step 5 – evaluate: $R_r = 0.079 \Omega$

Step 6 – interpret: The very small radiation resistance is why electrically short antennas are inefficient radiators.

Final Answer: $R_r \approx 0.079 \Omega \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q45](#)

Q46.

Solution

Concept – directivity in decibels: A dimensionless directivity is expressed relative to an isotropic source as $D_{\text{dBi}} = 10 \log_{10} D$.

Step 1 – list the data: $D = 4$.

Step 2 – take the base-10 logarithm: $\log_{10} 4 = 0.602$

Step 3 – multiply by ten: $D_{\text{dBi}} = 10 \times 0.602$



Step 4 – evaluate: $D_{\text{dBi}} = 6.02 \approx 6 \text{ dBi}$

Final Answer: $D_{\text{dBi}} \approx 6 \text{ dBi} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q46](#)



Answer Key

Q	Ans	Q	Ans	Q	Ans	Q	Ans	Q	Ans
1	C	2	D	3	C	4	B	5	B
6	D	7	D	8	B	9	C	10	B
11	B	12	D	13	C	14	D	15	A
16	B	17	D	18	B	19	A	20	A
21	C	22	A	23	A	24	B	25	A
26	B	27	C	28	A	29	D	30	A
31	D	32	C	33	C	34	D	35	C
36	A	37	D	38	A	39	A	40	B
41	C	42	A	43	C	44	B	45	D
46	B								

