

GATE Electrical Engineering

Sample Paper – 1

Duration: 128 Minutes


Maximum Marks: 72

Instructions

- This paper contains **46 questions** covering the core **Electrical Engineering** subject of the GATE paper conducted by the IITs and IISc (General Aptitude and Engineering Mathematics are provided as separate papers).
- **Q1–Q20 carry 1 mark each and Q21–Q46 carry 2 marks each**, for a total of **72 marks**.
- Each question carries **negative marking of one-third of its allotted marks**: a wrong 1-mark question costs **0.33** and a wrong 2-mark question costs **0.67**. Unattempted questions carry no penalty.
- Every question here is a single-correct **MCQ**. The real GATE paper also has Multiple Select (MSQ) and Numerical Answer Type (NAT) questions, and **those carry no negative marking**.
- Attempt this paper in one timed sitting of about **128 minutes**, the share this core subject earns at GATE's overall pace of 180 minutes for 65 questions. Unless stated otherwise take $\epsilon_0 = 8.854 \times 10^{-12}$ F/m, $\mu_0 = 4\pi \times 10^{-7}$ H/m and $c = 3 \times 10^8$ m/s.

Electric Circuits

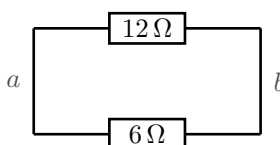- Q1.** Two resistors of $12\ \Omega$ and $6\ \Omega$ are connected in parallel between nodes a and b , as shown. The equivalent resistance seen between a and b is: [1 mark]




(A) $18\ \Omega$




- (B) $6\ \Omega$
- (C) $2\ \Omega$
- (D) $4\ \Omega$

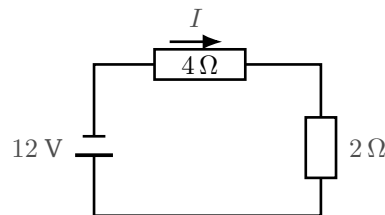Q2. In the single-loop circuit shown, a 12 V d.c. source drives a series combination of $4\ \Omega$ and $2\ \Omega$. Using mesh (loop) analysis, the loop current I is: [1 mark]



- (A) 3 A
- (B) 2 A
- (C) 1 A
- (D) 6 A

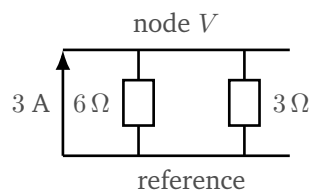Q3. In the circuit shown, an ideal 3 A current source feeds two resistors of $6\ \Omega$ and $3\ \Omega$ connected in parallel to the reference node. By nodal analysis the node voltage V is: [1 mark]



- (A) 3 V
- (B) 9 V
- (C) 18 V
- (D) 6 V

Q4. A series RC circuit is switched on to a d.c. source at $t = 0$, with $R = 2\ \text{k}\Omega$ and $C = 5\ \mu\text{F}$. The time constant of the charging transient is: [1 mark]



- (A) 1 ms
- (B) 100 ms
- (C) 10 ms
- (D) 0.1 ms


Q5. A source-free series RL circuit has $L = 100$ mH and $R = 25 \Omega$. The time constant of the natural (transient) response is: [1 mark]

- (A) 2.5 ms
- (B) 0.25 ms
- (C) 40 ms
- (D) 4 ms

Q6. A one-port network is reduced to its Thevenin equivalent with open-circuit voltage $V_{th} = 10$ V and Thevenin resistance $R_{th} = 5 \Omega$. When a load is connected for maximum power transfer, the power delivered to the load is: [1 mark]

- (A) 20 W
- (B) 10 W
- (C) 5 W
- (D) 2.5 W

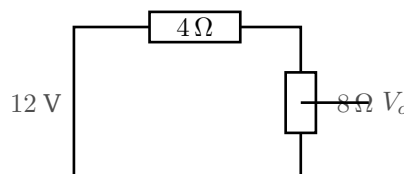Q7. For the resistive voltage divider shown, a 12 V source is applied across the series combination of 4Ω and 8Ω . The voltage V_o across the 8Ω resistor is: [1 mark]




- (A) 4 V
- (B) 6 V
- (C) 12 V



(D) 8 V

Electromagnetic Fields

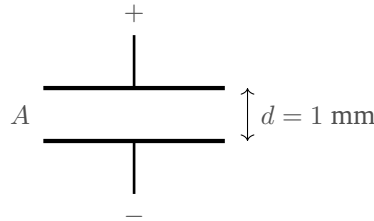- Q8.** A parallel-plate capacitor has plate area $A = 0.01 \text{ m}^2$ and plate separation $d = 1 \text{ mm}$ with air (vacuum) dielectric, as shown. Using $C = \epsilon_0 A/d$, the capacitance is nearest to: [1 mark]




- (A) 8.85 pF
(B) 885 pF
(C) 88.5 pF
(D) 0.885 pF
- Q9.** By Gauss's law, a point charge $Q = 1 \mu\text{C}$ in free space produces a radial electric field of magnitude $E = \frac{Q}{4\pi\epsilon_0 r^2}$. At a distance $r = 3 \text{ m}$ (take $\frac{1}{4\pi\epsilon_0} = 9 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2$), the field magnitude is: [1 mark]
- (A) 1000 V/m
(B) 3000 V/m
(C) 333 V/m
(D) 9000 V/m
- Q10.** A capacitor of $C = 100 \mu\text{F}$ is charged to a voltage of 100 V. The electrostatic energy stored in the capacitor, $W = \frac{1}{2}CV^2$, is: [1 mark]
- (A) 0.5 J
(B) 1 J
(C) 0.05 J



(D) 5 J

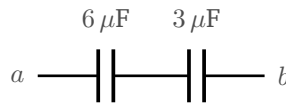- Q11.** Two capacitors of $6\ \mu\text{F}$ and $3\ \mu\text{F}$ are connected in series, as shown. The equivalent capacitance of the combination is: [1 mark]




- (A) $9\ \mu\text{F}$
(B) $2\ \mu\text{F}$
(C) $18\ \mu\text{F}$
(D) $4.5\ \mu\text{F}$

Signals and Systems

- Q12.** Two finite-length discrete sequences of lengths 5 and 4 samples respectively are linearly convolved. The length (number of samples) of the resulting sequence is: [1 mark]

- (A) 9
(B) 20
(C) 5
(D) 8

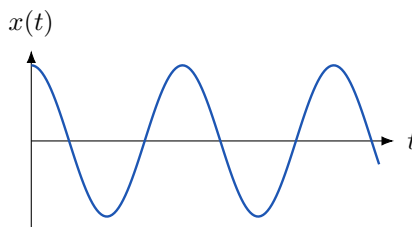- Q13.** A continuous-time signal is $x(t) = \cos(100\pi t)$, one cycle of which is sketched below. Its fundamental period T is: [1 mark]



- (A) 10 ms
(B) 20 ms
(C) 5 ms



(D) 100 ms

Q14. An input $x(t)$ is applied to an LTI system whose impulse response is a shifted impulse $h(t) = \delta(t - 3)$. Using the sifting property of convolution, the output $y(t) = x(t) * \delta(t - 3)$ is: [1 mark]

(A) $x(t + 3)$

(B) $x(t - 3)$

(C) $x(t)$

(D) $x(3t)$

Q15. The Fourier-series (average or d.c.) value of the periodic signal $x(t) = 5 + 4 \cos(\omega_0 t)$ over one period is: [1 mark]


(A) 5

(B) 4

(C) 9

(D) 0

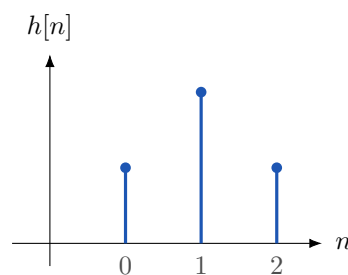Q16. A discrete-time LTI system has the finite impulse response $h[n]$ shown ($h[0] = 1$, $h[1] = 2$, $h[2] = 1$). Its d.c. gain, $\sum_n h[n]$, is: [1 mark]



(A) 1


(B) 2

(C) 4

(D) 0



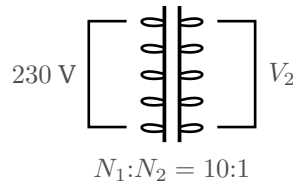- Q17.** An ideal single-phase transformer has a turns ratio $N_1/N_2 = 10$ and is supplied at 230 V on the primary, as shown. The secondary (open-circuit) voltage is: [1 mark]



- (A) 2300 V
(B) 23 V
(C) 230 V
(D) 46 V
- Q18.** A d.c. shunt motor is supplied at $V = 220\text{ V}$ and draws an armature current $I_a = 20\text{ A}$. The armature-circuit resistance is $R_a = 0.5\ \Omega$. The back e.m.f. $E_b = V - I_a R_a$ is: [1 mark]
- (A) 230 V
(B) 200 V
(C) 210 V
(D) 10 V
- Q19.** An ideal single-phase transformer has a turns ratio $N_1/N_2 = 2$. When the secondary delivers a load current of 10 A, the primary current (from $I_1/I_2 = N_2/N_1$) is: [1 mark]
- (A) 5 A
(B) 20 A
(C) 10 A
(D) 2 A
- Q20.** A 5 kVA single-phase transformer has a rated secondary voltage of 250 V. The rated (full-load) secondary current is: [1 mark]



- (A) 5 A
- (B) 10 A
- (C) 2 A
- (D) 20 A


Q21. A d.c. motor develops a back e.m.f. of $E_b = 200$ V while carrying an armature current of $I_a = 25$ A. The gross mechanical power developed in the armature, $P = E_b I_a$, is: [2 marks]

- (A) 5 kW
- (B) 8 kW
- (C) 0.2 kW
- (D) 10 kW

Q22. A single-phase transformer delivers an output of 4 kW. Its core (iron) loss is 100 W and its copper loss at this load is 100 W. The efficiency $\eta = \frac{P_{out}}{P_{out} + P_{loss}}$ is nearest to: [2 marks]

- (A) 90%
- (B) 98%
- (C) 95.2%
- (D) 80%

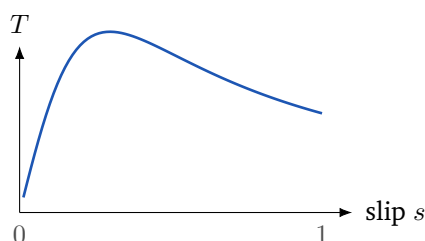Q23. A 4-pole, 50 Hz three-phase induction motor runs at a rotor speed of 1440 rpm. Its torque-slip characteristic is sketched below. The per-unit slip $s = \frac{N_s - N}{N_s}$ is: [2 marks]



- (A) 2%




- (B) 4%
- (C) 6%
- (D) 8%

Power Systems

Q24. In per-unit analysis, a base of 100 MVA and 11 kV is chosen. The base impedance $Z_{base} = \frac{(kV_{base})^2}{MVA_{base}}$ is: [2 marks]

- (A) 0.121 Ω
- (B) 1.21 Ω
- (C) 12.1 Ω
- (D) 121 Ω

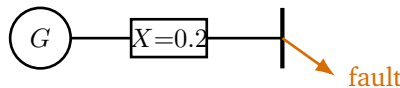Q25. A generator is connected to a bus of base 100 MVA through a reactance of $X = 0.2$ pu, as shown by the single-line diagram. For a three-phase symmetrical fault at the bus the fault level $MVA_{fault} = \frac{MVA_{base}}{X_{pu}}$ is: [2 marks]



- (A) 100 MVA
- (B) 20 MVA
- (C) 500 MVA
- (D) 200 MVA


Q26. A generator reactance is given as 0.1 pu on a base of 50 MVA. Converting it to a new base of 100 MVA at the same voltage, using $X_{new} = X_{old} \times \frac{MVA_{new}}{MVA_{old}}$, gives: [2 marks]

- (A) 0.2 pu
- (B) 0.05 pu
- (C) 0.1 pu



(D) 0.4 pu

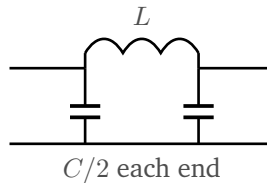- Q27.** A lossless transmission line is modelled by the π -section shown with series inductance $L = 0.9$ mH/km and shunt capacitance $C = 0.01$ μ F/km. Its surge (characteristic) impedance $Z_c = \sqrt{L/C}$ is: [2 marks]




- (A) 150 Ω
 (B) 300 Ω
 (C) 400 Ω
 (D) 75 Ω

- Q28.** Two buses of a lossless line are held at $V_1 = V_2 = 1.0$ pu, and the line reactance is $X = 0.5$ pu. The theoretical maximum power transferable, $P_{max} = \frac{V_1 V_2}{X}$ (at $\delta = 90^\circ$), is: [2 marks]

- (A) 2 pu
 (B) 0.5 pu
 (C) 1 pu
 (D) 4 pu

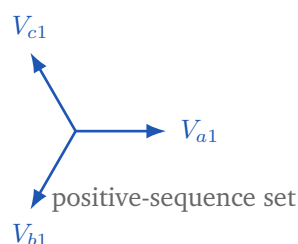- Q29.** A single-line-to-ground fault occurs on an unloaded generator. The sequence reactances are $Z_1 = Z_2 = Z_0 = 0.1$ pu and the pre-fault e.m.f. is $E = 1.0$ pu. The fault current $I_f = \frac{3E}{Z_1 + Z_2 + Z_0}$ is: [2 marks]



- (A) 10 pu
- (B) 3.33 pu
- (C) 30 pu
- (D) 1 pu

Q30. A three-phase system has a base of 100 MVA and a line voltage of 132 kV. The base current $I_{base} = \frac{\text{MVA}_{base}}{\sqrt{3} \text{ kV}_{base}}$ is nearest to: [2 marks]

- (A) 758 A
- (B) 437 A
- (C) 220 A
- (D) 100 A

Control Systems

Q31. A standard second-order system has the characteristic equation $s^2 + 6s + 25 = 0$. Comparing with $s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$, the damping ratio ζ is: [2 marks]


- (A) 0.3
- (B) 1
- (C) 0.5
- (D) 0.6

Q32. The characteristic equation of a closed-loop system is $s^3 + 6s^2 + 11s + 6 = 0$. Using the Routh–Hurwitz criterion, the number of closed-loop poles in the right half of the s -plane is: [2 marks]


- (A) 0
- (B) 1
- (C) 2
- (D) 3



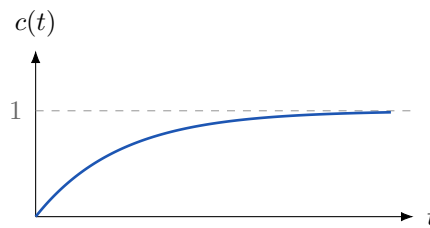- Q33.** A unity-feedback second-order system has damping ratio $\zeta = 0.5$. For a unit-step input the peak percentage overshoot $M_p = e^{-\pi\zeta/\sqrt{1-\zeta^2}} \times 100\%$ (illustrated below) is nearest to: [2 marks]



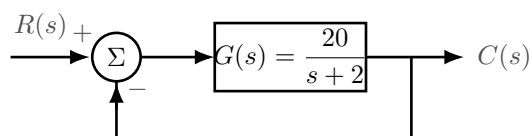- (A) 5%
 (B) 25%
 (C) 16.3%
 (D) 50%
- Q34.** A unity-feedback system has open-loop transfer function $G(s) = \frac{10}{s(s+2)}$. For a unit-step input the steady-state error (a type-1 system, $e_{ss} = 1/(1+K_p)$ with $K_p = \lim_{s \rightarrow 0} G(s) = \infty$) is: [2 marks]
- (A) 0
 (B) 0.5
 (C) 0.1
 (D) 1
- Q35.** For the unity-feedback control system shown, the forward-path transfer function is $G(s) = \frac{20}{s+2}$. The d.c. gain of the closed-loop transfer function $\frac{C(s)}{R(s)} = \frac{G(s)}{1+G(s)}$ (its value at $s = 0$) is nearest to: [2 marks]




- (A) 10
 (B) 1



- (C) 0.5
(D) 0.909


Analog, Digital and Measurements

- Q36.** For the ideal-op-amp inverting amplifier shown, $R_1 = 10 \text{ k}\Omega$ and $R_f = 50 \text{ k}\Omega$. The magnitude of the closed-loop voltage gain $|V_o/V_i| = R_f/R_1$ is: [2 marks]

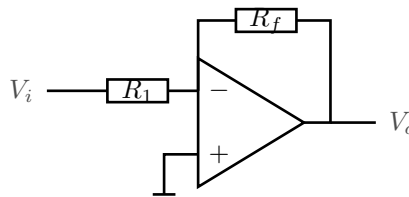

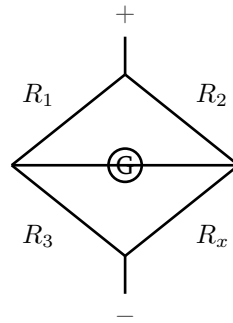- (A) 0.2
(B) 6
(C) 5
(D) 50
- Q37.** The unsigned binary number $(10110)_2$ has the decimal (base-10) value: [2 marks]
- (A) 11
(B) 44
(C) 26
(D) 22
- Q38.** The Wheatstone bridge shown is balanced with $R_1 = 100 \Omega$, $R_2 = 200 \Omega$ and $R_3 = 300 \Omega$. The unknown resistance, from the balance condition $R_x = \frac{R_2 R_3}{R_1}$, is: [2 marks]






- (A) $150\ \Omega$
- (B) $600\ \Omega$
- (C) $66.7\ \Omega$
- (D) $900\ \Omega$

Q39. The hexadecimal number $(1A)_{16}$ has the decimal (base-10) value: [2 marks]

- (A) 26
- (B) 16
- (C) 10
- (D) 32

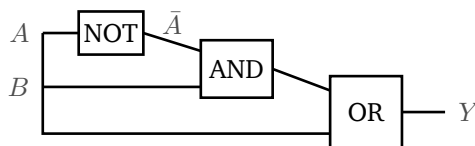Q40. The Boolean output of the gate network shown is $Y = A + \bar{A}B$. Applying the absorption/redundancy law, the simplified expression is: [2 marks]



- (A) A
- (B) B
- (C) AB
- (D) $A + B$


Q41. A sinusoidal voltage has a peak (amplitude) value of $V_m = 10\text{ V}$. Its true root-mean-square (RMS) value, as read by a true-RMS meter, is $V_{rms} = V_m/\sqrt{2}$, which is: [2 marks]



- (A) 10 V
- (B) 14.14 V
- (C) 7.07 V
- (D) 5 V


Power Electronics

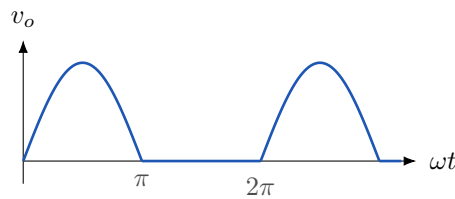- Q42.** A single-phase half-wave diode rectifier feeds a resistive load from a supply of peak voltage $V_m = 100$ V, giving the output waveform shown. The average (d.c.) output voltage $V_{dc} = V_m/\pi$ is: [2 marks]



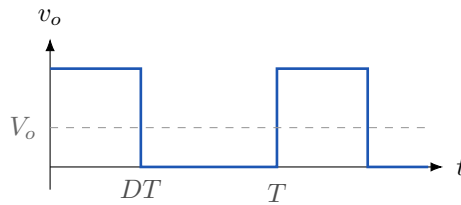- (A) 63.66 V
 - (B) 31.83 V
 - (C) 45 V
 - (D) 100 V
- Q43.** A single-phase full-wave (centre-tapped or bridge) diode rectifier feeds a resistive load from a supply of peak voltage $V_m = 100$ V. The average (d.c.) output voltage $V_{dc} = \frac{2V_m}{\pi}$ is: [2 marks]
- (A) 63.66 V
 - (B) 31.83 V
 - (C) 45 V
 - (D) 70.7 V
- Q44.** A step-down (buck) d.c. chopper operates from a supply $V_s = 200$ V at a duty ratio $D = 0.4$, producing the output-voltage waveform shown. The average output voltage $V_o = D V_s$ is: [2 marks]





- (A) 200 V
- (B) 120 V
- (C) 500 V
- (D) 80 V

Q45. A step-down d.c. chopper supplies an average output voltage of 150 V from an input of 300 V. The required duty ratio, $D = V_o/V_s$, is: [2 marks]

- (A) 0.25
- (B) 0.5
- (C) 0.75
- (D) 2

Q46. A single-phase full-wave controlled rectifier (fully controlled bridge) feeds a highly inductive load from a supply of peak voltage $V_m = 100$ V, at a firing angle $\alpha = 60^\circ$. The average output voltage $V_{dc} = \frac{2V_m}{\pi} \cos \alpha$ is: [2 marks]

- (A) 63.66 V
- (B) 45 V
- (C) 31.83 V
- (D) 0 V



Detailed Solutions**Q1.****Solution**

Concept – two resistors in parallel: The equivalent of two parallel resistors is their product over their sum, $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$.

Step 1 – list the data: $R_1 = 12 \Omega$, $R_2 = 6 \Omega$.

Step 2 – form the product of the resistances: $R_1 R_2 = 12 \times 6 = 72$

Step 3 – form the sum of the resistances: $R_1 + R_2 = 12 + 6 = 18$

Step 4 – divide: $R_{eq} = \frac{72}{18}$

$$R_{eq} = 4 \Omega$$

Step 5 – sanity check: A parallel combination is always smaller than the smallest branch (6Ω), and $4 < 6$, so the result is consistent.

Final Answer: $R_{eq} = 4 \Omega \Rightarrow$ D

Answer: (D) [Go Back to Q1](#)

Q2.**Solution**

Concept – mesh analysis of a single loop: For one loop, Kirchhoff's voltage law gives the source equal to the sum of the resistive drops, $V = I(R_1 + R_2)$.

Step 1 – add the series resistances: $R_{total} = 4 + 2$

$$R_{total} = 6 \Omega$$

Step 2 – write KVL around the loop: $12 = I \times 6$

Step 3 – solve for the loop current: $I = \frac{12}{6}$

$$I = 2 \text{ A}$$

Final Answer: $I = 2 \text{ A} \Rightarrow$ B

Answer: (B) [Go Back to Q2](#)



Q3.

Solution

Concept – nodal analysis with a current source: The current source current all flows into the parallel resistors, so $V = I_s R_{eq}$ where R_{eq} is the parallel combination.

Step 1 – combine the two resistors in parallel: $R_{eq} = \frac{6 \times 3}{6 + 3}$

$$R_{eq} = \frac{18}{9}$$

$$R_{eq} = 2 \Omega$$

Step 2 – apply the node equation (all source current through R_{eq}): $V = I_s \times R_{eq}$

Step 3 – substitute the values: $V = 3 \times 2$

$$V = 6 \text{ V}$$

Final Answer: $V = 6 \text{ V} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q3](#)

Q4.

Solution

Concept – time constant of an RC circuit: For a first-order RC circuit the time constant is $\tau = RC$.

Step 1 – convert the values to base units: $R = 2 \text{ k}\Omega = 2 \times 10^3 \Omega$

$$C = 5 \mu\text{F} = 5 \times 10^{-6} \text{ F}$$

Step 2 – multiply: $\tau = (2 \times 10^3) \times (5 \times 10^{-6})$

Step 3 – combine the numbers and the powers of ten: $\tau = 10 \times 10^{-3}$

$$\tau = 0.01 \text{ s} = 10 \text{ ms}$$

Final Answer: $\tau = 10 \text{ ms} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q4](#)

Q5.

Solution

Concept – time constant of an RL circuit: For a first-order RL circuit the time constant is $\tau = \frac{L}{R}$.

Step 1 – convert the inductance to base units: $L = 100 \text{ mH} = 100 \times 10^{-3} \text{ H} = 0.1 \text{ H}$



Step 2 – substitute the values: $\tau = \frac{0.1}{25}$

Step 3 – evaluate: $\tau = 0.004 \text{ s} = 4 \text{ ms}$

Final Answer: $\tau = 4 \text{ ms} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q5](#)

Q6.

Solution

Concept – maximum power transfer theorem: Maximum power is delivered when the load equals the Thevenin resistance, and then $P_{\max} = \frac{V_{th}^2}{4R_{th}}$.

Step 1 – list the data: $V_{th} = 10 \text{ V}$, $R_{th} = 5 \Omega$.

Step 2 – square the Thevenin voltage: $V_{th}^2 = 10^2 = 100$

Step 3 – form the denominator: $4R_{th} = 4 \times 5 = 20$

Step 4 – divide: $P_{\max} = \frac{100}{20}$

$P_{\max} = 5 \text{ W}$

Final Answer: $P_{\max} = 5 \text{ W} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q6](#)

Q7.

Solution

Concept – resistive voltage divider: For two series resistors across a source, the voltage across one of them is $V_o = V \times \frac{R_2}{R_1 + R_2}$.

Step 1 – add the two resistances: $R_1 + R_2 = 4 + 8 = 12 \Omega$

Step 2 – form the divider ratio for the 8Ω resistor: $\frac{R_2}{R_1 + R_2} = \frac{8}{12}$

Step 3 – multiply by the source voltage: $V_o = 12 \times \frac{8}{12}$

Step 4 – evaluate: $V_o = 8 \text{ V}$

Final Answer: $V_o = 8 \text{ V} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q7](#)



Q8.

Solution

Concept – capacitance of a parallel-plate capacitor: $C = \frac{\epsilon_0 A}{d}$ for a vacuum (air) dielectric.

Step 1 – list the data in base units: $\epsilon_0 = 8.854 \times 10^{-12}$ F/m, $A = 0.01$ m², $d = 1$ mm = 1×10^{-3} m.

Step 2 – form the numerator $\epsilon_0 A$: $\epsilon_0 A = (8.854 \times 10^{-12}) \times (0.01)$

$$\epsilon_0 A = 8.854 \times 10^{-14}$$

Step 3 – divide by the plate separation: $C = \frac{8.854 \times 10^{-14}}{1 \times 10^{-3}}$

Step 4 – combine the powers of ten: $C = 8.854 \times 10^{-11}$ F

Step 5 – convert to picofarads: $C = 88.54$ pF ≈ 88.5 pF

Final Answer: $C \approx 88.5$ pF $\Rightarrow$ **C**

Answer: (C) [Go Back to Q8](#)

Q9.

Solution

Concept – Gauss's law for a point charge: The radial field of a point charge is $E = \frac{1}{4\pi\epsilon_0} \cdot \frac{Q}{r^2}$.

Step 1 – list the data: $\frac{1}{4\pi\epsilon_0} = 9 \times 10^9$, $Q = 1$ μ C = 1×10^{-6} C, $r = 3$ m.

Step 2 – square the distance: $r^2 = 3^2 = 9$ m²

Step 3 – substitute into the field equation: $E = \frac{(9 \times 10^9) \times (1 \times 10^{-6})}{9}$

Step 4 – evaluate the numerator: $(9 \times 10^9) \times (1 \times 10^{-6}) = 9 \times 10^3$

Step 5 – divide by r^2 : $E = \frac{9 \times 10^3}{9}$

$$E = 1000 \text{ V/m}$$

Final Answer: $E = 1000$ V/m $\Rightarrow$ **A**

Answer: (A) [Go Back to Q9](#)



Q10.

Solution

Concept – energy stored in a capacitor: $W = \frac{1}{2}CV^2$.

Step 1 – list the data in base units: $C = 100 \mu\text{F} = 100 \times 10^{-6} \text{ F}$, $V = 100 \text{ V}$.

Step 2 – square the voltage: $V^2 = 100^2 = 10000 \text{ V}^2$

Step 3 – substitute into the energy equation: $W = \frac{1}{2} \times (100 \times 10^{-6}) \times 10000$

Step 4 – multiply the capacitance by V^2 : $(100 \times 10^{-6}) \times 10000 = 1$

Step 5 – take one-half: $W = \frac{1}{2} \times 1$

$$W = 0.5 \text{ J}$$

Final Answer: $W = 0.5 \text{ J} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q10](#)

Q11.

Solution

Concept – capacitors in series: For two series capacitors the equivalent is $C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$.

Step 1 – list the data: $C_1 = 6 \mu\text{F}$, $C_2 = 3 \mu\text{F}$.

Step 2 – form the product: $C_1 C_2 = 6 \times 3 = 18$

Step 3 – form the sum: $C_1 + C_2 = 6 + 3 = 9$

Step 4 – divide: $C_{eq} = \frac{18}{9}$

$$C_{eq} = 2 \mu\text{F}$$

Step 5 – sanity check: A series capacitance is smaller than the smallest capacitor ($3 \mu\text{F}$), and $2 < 3$, so the result is consistent.

Final Answer: $C_{eq} = 2 \mu\text{F} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q11](#)



Q12.

Solution

Concept – length of a linear convolution: If two sequences have lengths L_1 and L_2 , their linear convolution has length $L_1 + L_2 - 1$.

Step 1 – list the lengths: $L_1 = 5, L_2 = 4$.

Step 2 – add the lengths: $L_1 + L_2 = 5 + 4 = 9$

Step 3 – subtract one: $L = 9 - 1$

$$L = 8$$

Final Answer: length = 8 samples $\Rightarrow$ **D**

Answer: (D) [Go Back to Q12](#)

Q13.

Solution

Concept – period of a cosine: For $x(t) = \cos(\omega_0 t)$ the fundamental period is $T = \frac{2\pi}{\omega_0}$.

Step 1 – identify the angular frequency: $\omega_0 = 100\pi$ rad/s.

Step 2 – substitute into the period formula: $T = \frac{2\pi}{100\pi}$

Step 3 – cancel π : $T = \frac{2}{100}$

Step 4 – evaluate: $T = 0.02$ s = 20 ms

Final Answer: $T = 20$ ms $\Rightarrow$ **B**

Answer: (B) [Go Back to Q13](#)

Q14.

Solution

Concept – convolution with a shifted impulse (sifting property): Convolution any signal with $\delta(t - t_0)$ simply shifts it: $x(t) * \delta(t - t_0) = x(t - t_0)$.

Step 1 – identify the shift: Here $h(t) = \delta(t - 3)$, so $t_0 = 3$.

Step 2 – apply the sifting property: $y(t) = x(t) * \delta(t - 3)$

Step 3 – write the result: $y(t) = x(t - 3)$

Why the other options are wrong:

- A, $x(t + 3)$: an advance; convolving with $\delta(t - 3)$ delays, not advances.



- C, $x(t)$: would require $h(t) = \delta(t)$ (no shift).
- D, $x(3t)$: time-scaling is not produced by convolution with an impulse.

Final Answer: $y(t) = x(t - 3) \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q14](#)

Q15.

Solution

Concept – d.c. term of a Fourier series: The average value of a signal is the constant (a_0) term; a pure cosine averages to zero over a period.

Step 1 – separate the signal: $x(t) = 5 + 4 \cos(\omega_0 t)$

Step 2 – average the constant part: The average of the constant 5 over a period is 5.

Step 3 – average the cosine part: $\frac{1}{T} \int_0^T 4 \cos(\omega_0 t) dt = 0$

Step 4 – add the two contributions: average = $5 + 0$

average = 5

Final Answer: average value = 5 $\Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q15](#)

Q16.

Solution

Concept – d.c. gain of a discrete FIR system: The d.c. (zero-frequency) gain equals the sum of all impulse-response samples, $H(e^{j0}) = \sum_n h[n]$.

Step 1 – read the samples from the stem plot: $h[0] = 1, h[1] = 2, h[2] = 1$.

Step 2 – add the first two: $1 + 2 = 3$

Step 3 – add the last sample: $3 + 1 = 4$

Step 4 – state the d.c. gain: $\sum_n h[n] = 4$

Final Answer: d.c. gain = 4 $\Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q16](#)



Q17.

Solution

Concept – ideal transformer voltage ratio: For an ideal transformer $\frac{V_1}{V_2} = \frac{N_1}{N_2}$,
so $V_2 = V_1 \cdot \frac{N_2}{N_1}$.

Step 1 – list the data: $V_1 = 230 \text{ V}$, $\frac{N_1}{N_2} = 10$.

Step 2 – write the secondary voltage: $V_2 = \frac{V_1}{N_1/N_2}$

Step 3 – substitute: $V_2 = \frac{230}{10}$

Step 4 – evaluate: $V_2 = 23 \text{ V}$

Why the other options are wrong:

- A, 2300 V: multiplies instead of divides (that would be a step-up ratio).
- C, 230 V: assumes a 1:1 ratio.
- D, 46 V: uses a ratio of 5 instead of 10.

Final Answer: $V_2 = 23 \text{ V} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q17](#)

Q18.

Solution

Concept – back e.m.f. of a d.c. motor: The armature back e.m.f. is $E_b = V - I_a R_a$.

Step 1 – list the data: $V = 220 \text{ V}$, $I_a = 20 \text{ A}$, $R_a = 0.5 \Omega$.

Step 2 – compute the armature resistive drop: $I_a R_a = 20 \times 0.5$

$$I_a R_a = 10 \text{ V}$$

Step 3 – subtract from the supply voltage: $E_b = 220 - 10$

$$E_b = 210 \text{ V}$$

Final Answer: $E_b = 210 \text{ V} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q18](#)



Q19.

Solution

Concept – ideal transformer current ratio: For an ideal transformer the currents scale inversely with the turns, $\frac{I_1}{I_2} = \frac{N_2}{N_1}$.

Step 1 – list the data: $\frac{N_1}{N_2} = 2, I_2 = 10 \text{ A}$.

Step 2 – write the primary current: $I_1 = I_2 \times \frac{N_2}{N_1}$

Step 3 – substitute the inverse ratio: $I_1 = 10 \times \frac{1}{2}$

Step 4 – evaluate: $I_1 = 5 \text{ A}$

Step 5 – sanity check with power: A step-down in current means a step-up in voltage, keeping $V_1 I_1 = V_2 I_2$; the ampere-turns balance holds.

Final Answer: $I_1 = 5 \text{ A} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q19](#)

Q20.

Solution

Concept – rated current from kVA rating: For a single-phase transformer the rated current on a winding is $I = \frac{\text{VA rating}}{\text{winding voltage}}$.

Step 1 – convert the rating to volt-amperes: $5 \text{ kVA} = 5000 \text{ VA}$

Step 2 – write the secondary current: $I_2 = \frac{5000}{250}$

Step 3 – evaluate: $I_2 = 20 \text{ A}$

Final Answer: $I_2 = 20 \text{ A} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q20](#)

Q21.

Solution

Concept – gross mechanical power in a d.c. machine: The power converted from electrical to mechanical form in the armature is $P = E_b I_a$.

Step 1 – list the data: $E_b = 200 \text{ V}, I_a = 25 \text{ A}$.

Step 2 – multiply: $P = 200 \times 25$

Step 3 – evaluate: $P = 5000 \text{ W}$



Step 4 – convert to kilowatts: $P = 5 \text{ kW}$

Final Answer: $P = 5 \text{ kW} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q21](#)

Q22.

Solution

Concept – transformer efficiency: $\eta = \frac{P_{out}}{P_{out} + P_{loss}}$, where P_{loss} is the sum of core loss and copper loss.

Step 1 – list the data: $P_{out} = 4 \text{ kW} = 4000 \text{ W}$, core loss = 100 W, copper loss = 100 W.

Step 2 – add the losses: $P_{loss} = 100 + 100 = 200 \text{ W}$

Step 3 – form the input power: $P_{in} = 4000 + 200 = 4200 \text{ W}$

Step 4 – divide output by input: $\eta = \frac{4000}{4200}$

Step 5 – evaluate as a percentage: $\eta = 0.952 = 95.2\%$

Final Answer: $\eta \approx 95.2\% \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q22](#)

Q23.

Solution

Concept – slip of an induction motor: First find the synchronous speed $N_s = \frac{120f}{P}$, then the slip $s = \frac{N_s - N}{N_s}$.

Step 1 – compute the synchronous speed: $N_s = \frac{120 \times 50}{4}$

$$N_s = \frac{6000}{4} = 1500 \text{ rpm}$$

Step 2 – form the difference of speeds: $N_s - N = 1500 - 1440 = 60 \text{ rpm}$

Step 3 – divide by the synchronous speed: $s = \frac{60}{1500}$

Step 4 – evaluate: $s = 0.04 = 4\%$

Final Answer: $s = 4\% \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q23](#)



Q24.

Solution

Concept – base impedance in per-unit analysis: $Z_{base} = \frac{(kV_{base})^2}{MVA_{base}}$.

Step 1 – list the data: $kV_{base} = 11 \text{ kV}$, $MVA_{base} = 100 \text{ MVA}$.

Step 2 – square the base voltage: $(11)^2 = 121$

Step 3 – divide by the base MVA: $Z_{base} = \frac{121}{100}$

Step 4 – evaluate: $Z_{base} = 1.21 \Omega$

Final Answer: $Z_{base} = 1.21 \Omega \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q24](#)

Q25.

Solution

Concept – fault level from per-unit reactance: For a three-phase symmetrical fault, $MVA_{fault} = \frac{MVA_{base}}{X_{pu}}$.

Step 1 – list the data: $MVA_{base} = 100 \text{ MVA}$, $X_{pu} = 0.2$.

Step 2 – substitute into the fault-level formula: $MVA_{fault} = \frac{100}{0.2}$

Step 3 – evaluate: $MVA_{fault} = 500 \text{ MVA}$

Final Answer: $MVA_{fault} = 500 \text{ MVA} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q25](#)

Q26.

Solution

Concept – changing the per-unit base: At the same base voltage, per-unit impedance scales directly with the base MVA: $X_{new} = X_{old} \times \frac{MVA_{new}}{MVA_{old}}$.

Step 1 – list the data: $X_{old} = 0.1 \text{ pu}$, $MVA_{old} = 50$, $MVA_{new} = 100$.

Step 2 – form the MVA ratio: $\frac{MVA_{new}}{MVA_{old}} = \frac{100}{50} = 2$

Step 3 – multiply: $X_{new} = 0.1 \times 2$

Step 4 – evaluate: $X_{new} = 0.2 \text{ pu}$

Final Answer: $X_{new} = 0.2 \text{ pu} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q26](#)



Q27.

Solution

Concept – surge (characteristic) impedance of a lossless line: $Z_c = \sqrt{\frac{L}{C}}$, using the per-unit-length inductance and capacitance.

Step 1 – list the data in base units: $L = 0.9 \text{ mH/km} = 0.9 \times 10^{-3} \text{ H/km}$,
 $C = 0.01 \text{ } \mu\text{F/km} = 0.01 \times 10^{-6} \text{ F/km}$.

Step 2 – form the ratio L/C : $\frac{L}{C} = \frac{0.9 \times 10^{-3}}{0.01 \times 10^{-6}}$

Step 3 – simplify the powers of ten: $\frac{0.9 \times 10^{-3}}{1 \times 10^{-8}} = 0.9 \times 10^5 = 90000$

Step 4 – take the square root: $Z_c = \sqrt{90000}$

$$Z_c = 300 \Omega$$

Final Answer: $Z_c = 300 \Omega \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q27](#)

Q28.

Solution

Concept – maximum power transfer over a line: For a lossless line, $P = \frac{V_1 V_2}{X} \sin \delta$, which is greatest at $\delta = 90^\circ$ where $\sin \delta = 1$.

Step 1 – list the data: $V_1 = V_2 = 1.0 \text{ pu}$, $X = 0.5 \text{ pu}$.

Step 2 – form the numerator: $V_1 V_2 = 1.0 \times 1.0 = 1.0$

Step 3 – divide by the reactance: $P_{max} = \frac{1.0}{0.5}$

Step 4 – evaluate: $P_{max} = 2 \text{ pu}$

Final Answer: $P_{max} = 2 \text{ pu} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q28](#)

Q29.

Solution

Concept – single-line-to-ground fault current: Using symmetrical components,

$$I_f = \frac{3E}{Z_1 + Z_2 + Z_0}$$

Step 1 – list the data: $E = 1.0 \text{ pu}$, $Z_1 = Z_2 = Z_0 = 0.1 \text{ pu}$.

Step 2 – add the sequence impedances: $Z_1 + Z_2 + Z_0 = 0.1 + 0.1 + 0.1 = 0.3$



Step 3 – form the numerator: $3E = 3 \times 1.0 = 3$

Step 4 – divide: $I_f = \frac{3}{0.3}$

Step 5 – evaluate: $I_f = 10$ pu

Final Answer: $I_f = 10$ pu $\Rightarrow$ **A**

Answer: (A) [Go Back to Q29](#)

Q30.

Solution

Concept – base current of a three-phase system: $I_{base} = \frac{\text{MVA}_{base} \times 10^6}{\sqrt{3} \times \text{kV}_{base} \times 10^3}$.

Step 1 – list the data: $\text{MVA}_{base} = 100$, $\text{kV}_{base} = 132$, $\sqrt{3} = 1.732$.

Step 2 – form the denominator: $\sqrt{3} \times \text{kV} = 1.732 \times 132$
 $= 228.6$

Step 3 – divide (in matching units of MVA and kV, current comes out in kA):

$$I_{base} = \frac{100}{228.6}$$

$$= 0.4374 \text{ kA}$$

Step 4 – convert to amperes: $I_{base} = 437.4 \text{ A} \approx 437 \text{ A}$

Final Answer: $I_{base} \approx 437 \text{ A} \Rightarrow$ **B**

Answer: (B) [Go Back to Q30](#)

Q31.

Solution

Concept – damping ratio of a second-order system: Comparing $s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$ with the given equation gives ω_n from the constant term and ζ from the middle term.

Step 1 – read the constant term for ω_n : $\omega_n^2 = 25$

$$\omega_n = \sqrt{25} = 5 \text{ rad/s}$$

Step 2 – read the middle term: $2\zeta\omega_n = 6$

Step 3 – solve for ζ : $\zeta = \frac{6}{2\omega_n} = \frac{6}{2 \times 5}$

Step 4 – evaluate: $\zeta = \frac{6}{10} = 0.6$

Final Answer: $\zeta = 0.6 \Rightarrow$ **D**



Answer: (D) [Go Back to Q31](#)

Q32.

Solution

Concept – Routh–Hurwitz criterion: The number of sign changes in the first column of the Routh array equals the number of right-half-plane roots.

Step 1 – write the coefficients of $s^3 + 6s^2 + 11s + 6$: Row s^3 : 1, 11

Row s^2 : 6, 6

Step 2 – compute the s^1 row: $b_1 = \frac{(6 \times 11) - (1 \times 6)}{6} = \frac{66 - 6}{6} = \frac{60}{6} = 10$

Step 3 – compute the s^0 row: $c_1 = \frac{(10 \times 6) - (6 \times 0)}{10} = \frac{60}{10} = 6$

Step 4 – list the first column: 1, 6, 10, 6 – all positive.

Step 5 – count sign changes: There are no sign changes, so there are 0 poles in the right half-plane (the system is stable).

Final Answer: 0 RHP poles $\Rightarrow$ **A**

Answer: (A) [Go Back to Q32](#)

Q33.

Solution

Concept – peak overshoot of a second-order system: $M_p = e^{-\pi\zeta/\sqrt{1-\zeta^2}} \times 100\%$.

Step 1 – compute $1 - \zeta^2$: $1 - (0.5)^2 = 1 - 0.25 = 0.75$

Step 2 – take the square root: $\sqrt{0.75} = 0.866$

Step 3 – form the exponent: $-\frac{\pi \times 0.5}{0.866} = -\frac{1.5708}{0.866} = -1.814$

Step 4 – take the exponential: $e^{-1.814} = 0.163$

Step 5 – convert to a percentage: $M_p = 0.163 \times 100 = 16.3\%$

Final Answer: $M_p \approx 16.3\% \Rightarrow$ **C**

Answer: (C) [Go Back to Q33](#)



Q34.

Solution

Concept – steady-state error of a type-1 system to a step: For a step input, $e_{ss} = \frac{1}{1 + K_p}$ with $K_p = \lim_{s \rightarrow 0} G(s)$. A pole at the origin makes K_p infinite.

Step 1 – evaluate the position error constant: $K_p = \lim_{s \rightarrow 0} \frac{10}{s(s+2)}$

Step 2 – observe the behaviour as $s \rightarrow 0$: The s in the denominator drives $G(s) \rightarrow \infty$, so $K_p = \infty$.

Step 3 – substitute into the error formula: $e_{ss} = \frac{1}{1 + \infty}$

Step 4 – evaluate the limit: $e_{ss} = 0$

Final Answer: $e_{ss} = 0 \Rightarrow \boxed{A}$

Answer: (A) [Go Back to Q34](#)

Q35.

Solution

Concept – d.c. gain of a unity-feedback closed loop: $\frac{C(s)}{R(s)} = \frac{G(s)}{1 + G(s)}$; evaluate at $s = 0$.

Step 1 – evaluate the forward gain at $s = 0$: $G(0) = \frac{20}{0+2} = \frac{20}{2} = 10$

Step 2 – form the closed-loop expression at $s = 0$: $\left. \frac{C}{R} \right|_{s=0} = \frac{G(0)}{1 + G(0)} = \frac{10}{1+10}$

Step 3 – simplify the denominator: $1 + 10 = 11$

Step 4 – divide: $\left. \frac{C}{R} \right|_{s=0} = \frac{10}{11}$

Step 5 – evaluate: $= 0.909$

Final Answer: d.c. gain $\approx 0.909 \Rightarrow \boxed{D}$

Answer: (D) [Go Back to Q35](#)

Q36.

Solution

Concept – gain of an inverting op-amp: For an ideal inverting amplifier the magnitude of the gain is $|A_v| = \frac{R_f}{R_1}$.

Step 1 – list the resistor values: $R_f = 50 \text{ k}\Omega$, $R_1 = 10 \text{ k}\Omega$.



Step 2 – form the ratio: $|A_v| = \frac{50 \text{ k}\Omega}{10 \text{ k}\Omega}$

Step 3 – evaluate: $|A_v| = 5$

Final Answer: $|A_v| = 5 \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q36](#)

Q37.

Solution

Concept – binary-to-decimal conversion: Each bit contributes its place value 2^k where the least-significant bit is $k = 0$.

Step 1 – write the bits with their weights $(10110)_2$: $1 \rightarrow 2^4$, $0 \rightarrow 2^3$, $1 \rightarrow 2^2$, $1 \rightarrow 2^1$, $0 \rightarrow 2^0$

Step 2 – evaluate each nonzero weight: $2^4 = 16$

$$2^2 = 4$$

$$2^1 = 2$$

Step 3 – add the contributions: $16 + 4 + 2 = 22$

Final Answer: $(10110)_2 = 22 \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q37](#)

Q38.

Solution

Concept – balanced Wheatstone bridge: At balance the ratio arms satisfy $\frac{R_1}{R_2} = \frac{R_3}{R_x}$, giving $R_x = \frac{R_2 R_3}{R_1}$.

Step 1 – list the data: $R_1 = 100 \Omega$, $R_2 = 200 \Omega$, $R_3 = 300 \Omega$.

Step 2 – form the numerator $R_2 R_3$: $R_2 R_3 = 200 \times 300 = 60000$

Step 3 – divide by R_1 : $R_x = \frac{60000}{100}$

Step 4 – evaluate: $R_x = 600 \Omega$

Final Answer: $R_x = 600 \Omega \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q38](#)



Q39.

Solution

Concept – hexadecimal-to-decimal conversion: Each hex digit has weight 16^k ; the digit A equals 10.

Step 1 – write the digits with weights for $(1A)_{16}$: $1 \rightarrow 16^1$, $A \rightarrow 16^0$

Step 2 – convert the digit A: $A = 10$

Step 3 – evaluate each term: $1 \times 16 = 16$

$$10 \times 1 = 10$$

Step 4 – add: $16 + 10 = 26$

Final Answer: $(1A)_{16} = 26 \Rightarrow \boxed{A}$

Answer: (A) [Go Back to Q39](#)

Q40.

Solution

Concept – redundancy (absorption) law of Boolean algebra: The identity $A + \bar{A}B = A + B$ removes the redundant $\bar{A}$.

Step 1 – start from the expression: $Y = A + \bar{A}B$

Step 2 – expand A using $A = A + AB$ (since $A + AB = A$): $Y = A + AB + \bar{A}B$

Step 3 – group the B terms: $Y = A + B(A + \bar{A})$

Step 4 – apply $A + \bar{A} = 1$: $Y = A + B(1)$

Step 5 – simplify: $Y = A + B$

Why the other options are wrong:

- A, A: drops the B contribution that survives when $A = 0, B = 1$.
- B, B: drops the A contribution.
- C, AB: is the AND, not the OR, of the variables.

Final Answer: $Y = A + B \Rightarrow \boxed{D}$

Answer: (D) [Go Back to Q40](#)



Q41.

Solution

Concept – RMS value of a sinusoid: For a sine wave the RMS value is the peak divided by $\sqrt{2}$, $V_{rms} = \frac{V_m}{\sqrt{2}}$.

Step 1 – list the data: $V_m = 10 \text{ V}$, $\sqrt{2} = 1.414$.

Step 2 – substitute: $V_{rms} = \frac{10}{1.414}$

Step 3 – evaluate: $V_{rms} = 7.07 \text{ V}$

Why the other options are wrong:

- A, 10 V: is the peak value, not the RMS.
- B, 14.14 V: multiplies by $\sqrt{2}$ instead of dividing.
- D, 5 V: is the average of a half-cycle-ish guess, not $V_m/\sqrt{2}$.

Final Answer: $V_{rms} = 7.07 \text{ V} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q41](#)

Q42.

Solution

Concept – average output of a half-wave rectifier: For a single-phase half-wave rectifier with resistive load, $V_{dc} = \frac{V_m}{\pi}$.

Step 1 – list the data: $V_m = 100 \text{ V}$, $\pi = 3.1416$.

Step 2 – substitute: $V_{dc} = \frac{100}{3.1416}$

Step 3 – evaluate: $V_{dc} = 31.83 \text{ V}$

Why the other options are wrong:

- A, 63.66 V: is $\frac{2V_m}{\pi}$, the *full-wave* average.
- C, 45 V: is close to the RMS of a half sine, not the average.
- D, 100 V: is the peak value.

Final Answer: $V_{dc} = 31.83 \text{ V} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q42](#)



Q43.

Solution

Concept – average output of a full-wave rectifier: For a single-phase full-wave rectifier with resistive load, $V_{dc} = \frac{2V_m}{\pi}$.

Step 1 – list the data: $V_m = 100 \text{ V}$, $\pi = 3.1416$.

Step 2 – form the numerator: $2V_m = 2 \times 100 = 200$

Step 3 – divide by π : $V_{dc} = \frac{200}{3.1416}$

Step 4 – evaluate: $V_{dc} = 63.66 \text{ V}$

Final Answer: $V_{dc} = 63.66 \text{ V} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q43](#)

Q44.

Solution

Concept – output of a step-down (buck) chopper: The average output voltage is $V_o = D V_s$, with D the duty ratio.

Step 1 – list the data: $V_s = 200 \text{ V}$, $D = 0.4$.

Step 2 – multiply: $V_o = 0.4 \times 200$

Step 3 – evaluate: $V_o = 80 \text{ V}$

Final Answer: $V_o = 80 \text{ V} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q44](#)

Q45.

Solution

Concept – duty ratio of a step-down chopper: From $V_o = D V_s$, the required duty ratio is $D = \frac{V_o}{V_s}$.

Step 1 – list the data: $V_o = 150 \text{ V}$, $V_s = 300 \text{ V}$.

Step 2 – form the ratio: $D = \frac{150}{300}$

Step 3 – evaluate: $D = 0.5$

Step 4 – sanity check: A duty ratio must lie between 0 and 1; 0.5 is valid and gives half the input as output.

Final Answer: $D = 0.5 \Rightarrow \boxed{\text{B}}$



Answer: (B) [Go Back to Q45](#)

Q46.

Solution

Concept – average output of a full-wave controlled rectifier: For a single-phase fully controlled bridge with a highly inductive (continuous) load, $V_{dc} = \frac{2V_m}{\pi} \cos \alpha$.

Step 1 – list the data: $V_m = 100 \text{ V}$, $\alpha = 60^\circ$, $\pi = 3.1416$.

Step 2 – evaluate the uncontrolled part: $\frac{2V_m}{\pi} = \frac{200}{3.1416} = 63.66 \text{ V}$

Step 3 – evaluate the cosine of the firing angle: $\cos 60^\circ = 0.5$

Step 4 – multiply: $V_{dc} = 63.66 \times 0.5$

Step 5 – evaluate: $V_{dc} = 31.83 \text{ V}$

Why the other options are wrong:

- A, 63.66 V: forgets the $\cos \alpha$ factor ($\alpha = 0$ case).
- B, 45 V: uses an incorrect firing-angle factor.
- D, 0 V: would need $\alpha = 90^\circ$, where $\cos \alpha = 0$.

Final Answer: $V_{dc} = 31.83 \text{ V} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q46](#)



Answer Key

Q	Ans	Q	Ans	Q	Ans	Q	Ans	Q	Ans
1	D	2	B	3	D	4	C	5	D
6	C	7	D	8	C	9	A	10	A
11	B	12	D	13	B	14	B	15	A
16	C	17	B	18	C	19	A	20	D
21	A	22	C	23	B	24	B	25	C
26	A	27	B	28	A	29	A	30	B
31	D	32	A	33	C	34	A	35	D
36	C	37	D	38	B	39	A	40	D
41	C	42	B	43	A	44	D	45	B
46	C								

