

GATE Electrical Engineering

Sample Paper – 4

Duration: 128 Minutes

Maximum Marks: 72

Instructions

- This paper contains **46 questions** covering the core **Electrical Engineering** subject of the GATE paper conducted by the IITs and IISc (General Aptitude and Engineering Mathematics are provided as separate papers).
- **Q1–Q20 carry 1 mark each and Q21–Q46 carry 2 marks each**, for a total of **72 marks**.
- Each question carries **negative marking of one-third of its allotted marks**: a wrong 1-mark question costs **0.33** and a wrong 2-mark question costs **0.67**. Unattempted questions carry no penalty.
- Every question here is a single-correct **MCQ**. The real GATE paper also has Multiple Select (MSQ) and Numerical Answer Type (NAT) questions, and **those carry no negative marking**.
- Attempt this paper in one timed sitting of about **128 minutes**, the share this core subject earns at GATE's overall pace of 180 minutes for 65 questions. Unless stated otherwise take $\epsilon_0 = 8.854 \times 10^{-12}$ F/m, $\mu_0 = 4\pi \times 10^{-7}$ H/m and $c = 3 \times 10^8$ m/s.

Electric Circuits


Q1. A one-port source network is reduced to its Thevenin equivalent with open-circuit voltage $V_{th} = 20$ V and Thevenin resistance $R_{th} = 10 \Omega$. For maximum power transfer, the value of the load resistance to be connected across the terminals is: [1 mark]

- (A) 20Ω
- (B) 5Ω



(C) $10\ \Omega$ (D) $40\ \Omega$

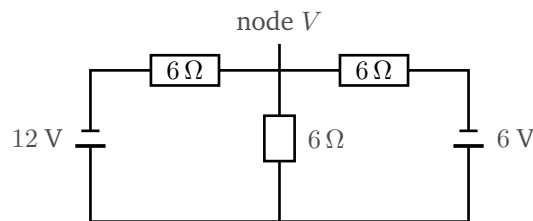- Q2.** In the circuit shown, a 12 V source (through a $6\ \Omega$ resistor) and a 6 V source (through a $6\ \Omega$ resistor) feed a common node that has a $6\ \Omega$ load to the reference. Using superposition, the node voltage V is: [1 mark]



(A) 4 V

(B) 6 V

(C) 9 V

(D) 3 V

- Q3.** A network is reduced to its Thevenin equivalent with $V_{th} = 30\text{ V}$ and $R_{th} = 15\ \Omega$. When a load resistance is chosen for maximum power transfer, the maximum power delivered to the load, $P_{\max} = \frac{V_{th}^2}{4R_{th}}$, is: [1 mark]


(A) 15 W

(B) 30 W

(C) 7.5 W

(D) 60 W

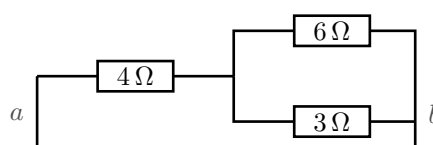- Q4.** For the resistive network shown, all sources have been deactivated. The Thevenin (equivalent) resistance seen between terminals a and b , formed by $4\ \Omega$ in series with the parallel combination of $6\ \Omega$ and $3\ \Omega$, is: [1 mark]



- (A) $4\ \Omega$
- (B) $2\ \Omega$
- (C) $6\ \Omega$
- (D) $9\ \Omega$


Q5. A source-free series RL circuit has $L = 0.5\text{ H}$ and $R = 10\ \Omega$. The time constant of the natural (transient) response, $\tau = L/R$, is: [1 mark]

- (A) 50 ms
- (B) 5 ms
- (C) 20 ms
- (D) 100 ms

Q6. When a load is matched to a source for maximum power transfer ($R_L = R_{th}$), the fraction of the total power (drawn from the source) that reaches the load, i.e. the power-transfer efficiency, is: [1 mark]

- (A) 100%
- (B) 50%
- (C) 75%
- (D) 25%

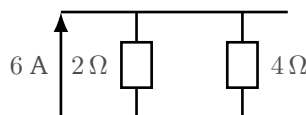Q7. An ideal 6 A current source feeds two resistors of $2\ \Omega$ and $4\ \Omega$ connected in parallel, as shown. By the current-divider rule the current flowing through the $2\ \Omega$ resistor is: [1 mark]




- (A) 4 A
- (B) 2 A
- (C) 6 A
- (D) 3 A



Electromagnetic Fields

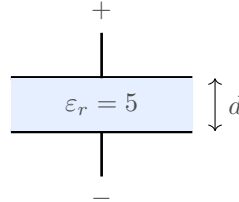- Q8.** A parallel-plate capacitor of plate area $A = 0.01 \text{ m}^2$ and separation $d = 0.5 \text{ mm}$ is completely filled with a dielectric of relative permittivity $\epsilon_r = 5$, as shown. Using $C = \frac{\epsilon_0 \epsilon_r A}{d}$, the capacitance is nearest to: [1 mark]




- (A) 885 pF
(B) 177 pF
(C) 88.5 pF
(D) 1770 pF
- Q9.** At a point in free space the electric field intensity is $E = 1 \times 10^6 \text{ V/m}$. The electrostatic energy density stored in the field, $u = \frac{1}{2} \epsilon_0 E^2$, is nearest to: [1 mark]
- (A) 8.85 J/m³
(B) 2.21 J/m³
(C) 17.7 J/m³
(D) 4.43 J/m³
- Q10.** A capacitor is charged so that it stores 8 J of electrostatic energy, and it is then disconnected from the source (so its charge Q stays fixed). A dielectric slab of relative permittivity $\epsilon_r = 4$ is now inserted, completely filling the gap. The new stored energy, from $W = \frac{Q^2}{2C}$ with $C \rightarrow 4C$, is: [1 mark]
- (A) 32 J
(B) 8 J
(C) 4 J



(D) 2 J

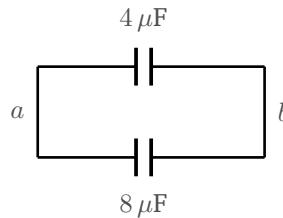
- Q11.** Two capacitors of $4\ \mu\text{F}$ and $8\ \mu\text{F}$ are connected in parallel between terminals a and b , as shown. The equivalent capacitance of the combination is: [1 mark]



- (A) $2.67\ \mu\text{F}$
 (B) $4\ \mu\text{F}$
 (C) $12\ \mu\text{F}$
 (D) $32\ \mu\text{F}$

Signals and Systems

- Q12.** A continuous-time signal is band-limited so that its spectrum $X(f)$ is zero for $|f| > 4\ \text{kHz}$, as sketched. According to the sampling theorem, the minimum (Nyquist) sampling rate needed to avoid aliasing is: [1 mark]

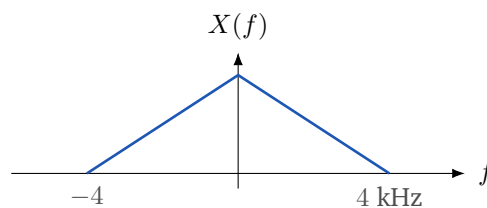

- (A) 4 kHz
 (B) 8 kHz
 (C) 2 kHz
 (D) 16 kHz

- Q13.** Let $x(t)$ have Fourier transform $X(\omega)$. By the time-shifting property, the Fourier transform of the delayed signal $x(t - t_0)$ is: [1 mark]



- (A) $X(\omega - \omega_0)$
- (B) $X(\omega) e^{+j\omega t_0}$
- (C) $X(\omega) e^{-j\omega t_0}$
- (D) $X(-\omega)$

Q14. A pure sinusoid of frequency 5 kHz is sampled at a rate of 8 kHz, which is below its Nyquist rate. The (aliased) frequency at which it appears in the sampled signal, $f_a = |f - f_s|$, is: [1 mark]

- (A) 3 kHz
- (B) 5 kHz
- (C) 8 kHz
- (D) 13 kHz

Q15. Using the standard analysis convention, the Fourier transform of the unit impulse $\delta(t)$ is: [1 mark]


- (A) $\delta(\omega)$
- (B) $2\pi \delta(\omega)$
- (C) $\frac{1}{j\omega}$
- (D) 1

Q16. A periodic signal is $x(t) = 3 + 2 \cos(\omega_0 t) + \sin(2\omega_0 t)$. Its average (d.c.) value over one full period, which is the a_0 Fourier-series coefficient, is: [1 mark]

- (A) 2
- (B) 3
- (C) 5
- (D) 0



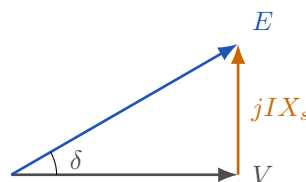- Q17.** A 6-pole, three-phase synchronous generator (alternator) is driven at a speed of 1000 rpm. The frequency of the generated e.m.f., $f = \frac{PN}{120}$, is: [1 mark]
- (A) 50 Hz
(B) 60 Hz
(C) 100 Hz
(D) 25 Hz
- Q18.** A three-phase, 8-pole synchronous motor is supplied from a 50 Hz source. Its synchronous (running) speed, $N_s = \frac{120f}{P}$, is: [1 mark]
- (A) 1000 rpm
(B) 1500 rpm
(C) 750 rpm
(D) 3000 rpm
- Q19.** A synchronous generator has an open-circuit (no-load) e.m.f. of $E = 250$ V and, when loaded, a terminal voltage of $V = 220$ V. Its percentage voltage regulation, $\frac{E - V}{V} \times 100\%$, is nearest to: [1 mark]
- (A) 12%
(B) 13.6%
(C) 30%
(D) 88%
- Q20.** A cylindrical-rotor synchronous generator has excitation e.m.f. $E = 1.2$ pu, terminal voltage $V = 1.0$ pu, synchronous reactance $X_s = 0.6$ pu and load (power) angle $\delta = 30^\circ$, as illustrated by the phasor diagram. The real power delivered, $P = \frac{EV}{X_s} \sin \delta$, is: [1 mark]



- (A) 1.0 pu
- (B) 0.5 pu
- (C) 2.0 pu
- (D) 0.6 pu


Q21. A three-phase induction motor has a synchronous speed of 1500 rpm and runs at a per-unit slip of $s = 0.04$. Its actual rotor speed, $N = N_s(1 - s)$, is: [2 marks]

- (A) 1500 rpm
- (B) 1440 rpm
- (C) 60 rpm
- (D) 1460 rpm

Q22. A synchronous generator delivers an output power of 100 kW while its total losses (core plus copper plus friction) amount to 5 kW. Its efficiency, $\eta = \frac{P_{out}}{P_{out} + P_{loss}}$, is nearest to: [2 marks]

- (A) 90%
- (B) 98%
- (C) 94%
- (D) 95.2%

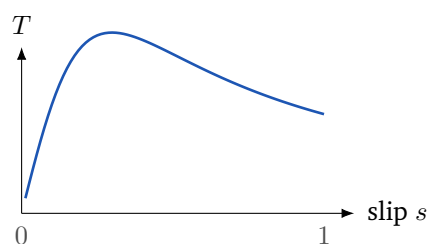Q23. A three-phase induction motor is supplied from a 50 Hz source and operates at a per-unit slip of $s = 0.05$, on the stable part of the torque-slip curve shown. The frequency of the rotor (slip) currents, $f_r = sf$, is: [2 marks]



- (A) 50 Hz



- (B) 0.5 Hz
- (C) 2.5 Hz
- (D) 5 Hz

Power Systems

Q24. A short transmission line with total series impedance Z is represented by its $ABCD$ (transmission) parameters. For a short line these are $A = 1$, $B = Z$, $C = 0$, $D = 1$. The value of the A parameter is therefore: [2 marks]

- (A) 1
- (B) 0
- (C) Z
- (D) Y

Q25. A short transmission line has a total series impedance $Z = (10 + j40) \Omega$ and negligible shunt admittance. In its $ABCD$ representation ($A = D = 1$, $C = 0$), the value of the B parameter is: [2 marks]


- (A) 1
- (B) 0
- (C) $(40 + j10) \Omega$
- (D) $(10 + j40) \Omega$

Q26. The $ABCD$ (transmission) parameters of any passive, reciprocal two-port network representing a transmission line obey a fixed determinant condition. The value of $AD - BC$ for such a line is: [2 marks]


- (A) 0
- (B) Z
- (C) Y
- (D) 1



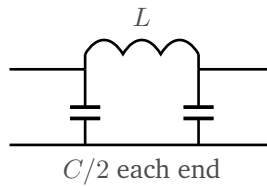- Q27.** A lossless transmission line, modelled by the π -section shown, has a series inductance $L = 1.6$ mH/km and a shunt capacitance $C = 0.01$ μ F/km. Its surge (characteristic) impedance $Z_c = \sqrt{L/C}$ is: [2 marks]



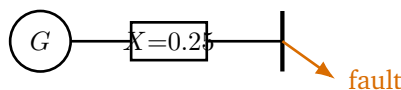- (A) 400 Ω
 (B) 200 Ω
 (C) 300 Ω
 (D) 160 Ω
- Q28.** Two buses of a lossless line are held at $V_1 = V_2 = 1.0$ pu with a line reactance $X = 0.25$ pu, and the load (power) angle is $\delta = 30^\circ$. The real power transmitted, $P = \frac{V_1 V_2}{X} \sin \delta$, is: [2 marks]
- (A) 1 pu
 (B) 2 pu
 (C) 4 pu
 (D) 0.5 pu
- Q29.** A generator with reactance $X = 0.25$ pu (on a 100 MVA base) and pre-fault e.m.f. $E = 1.0$ pu feeds the bus shown. For a balanced three-phase fault at the bus the per-unit fault current, $I_f = \frac{E}{X}$, is: [2 marks]



- (A) 0.25 pu
 (B) 4 pu
 (C) 2 pu
 (D) 1 pu



Q30. A per-unit study chooses a base of 200 MVA and 20 kV. The base impedance,

$$Z_{base} = \frac{(kV_{base})^2}{MVA_{base}}, \text{ is:} \quad [2 \text{ marks}]$$

- (A) 0.5Ω
- (B) 10Ω
- (C) 2Ω
- (D) 20Ω

Control Systems

Q31. A linear system is described in state-space form with system matrix $A =$

$$\begin{bmatrix} 0 & 1 \\ -2 & -3 \end{bmatrix}. \text{ The poles (eigenvalues), i.e. the roots of } \det(sI - A) = s^2 + 3s + 2 = 0, \text{ are:} \quad [2 \text{ marks}]$$

- (A) $-1, -3$
- (B) $0, -3$
- (C) $-1, -2$
- (D) $-2, -3$

Q32. A second-order system has $A = \begin{bmatrix} 0 & 1 \\ 0 & -2 \end{bmatrix}$ and $B = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$. Its controllability

matrix is $Q_c = [B \ AB] = \begin{bmatrix} 0 & 1 \\ 1 & -2 \end{bmatrix}$, with $\det Q_c = -1 \neq 0$. The system is therefore: [2 marks]

- (A) completely controllable
- (B) uncontrollable
- (C) unstable
- (D) marginally stable

Q33. A standard second-order system has the characteristic equation $s^2 + 4s + 16 = 0$. Comparing with $s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$, the damping ratio ζ is: [2 marks]

- (A) 1




- (B) 0.25
- (C) 0.5
- (D) 0.4

Q34. The state matrix A of a linear time-invariant system has eigenvalues at $s = -2$ and $s = +1$. Judging stability from the location of these eigenvalues (poles) in the s -plane, the system is: [2 marks]

- (A) stable
- (B) marginally stable
- (C) critically damped
- (D) unstable

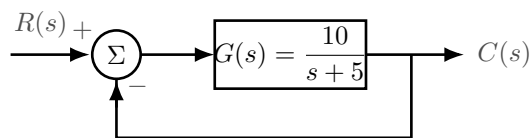Q35. For the unity-feedback control system shown, the forward-path transfer function is $G(s) = \frac{10}{s+5}$. The d.c. gain of the closed-loop transfer function $\frac{C(s)}{R(s)} = \frac{G(s)}{1+G(s)}$ (its value at $s = 0$) is nearest to: [2 marks]




- (A) 10
- (B) 2
- (C) 1
- (D) 0.667

Analog, Digital and Measurements

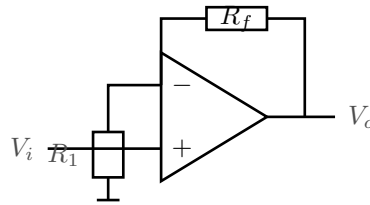
Q36. For the ideal-op-amp non-inverting amplifier shown, $R_1 = 10 \text{ k}\Omega$ and $R_f = 20 \text{ k}\Omega$. Its closed-loop voltage gain $\frac{V_o}{V_i} = 1 + \frac{R_f}{R_1}$ is: [2 marks]





- (A) 2
- (B) 20
- (C) 3
- (D) 0.5

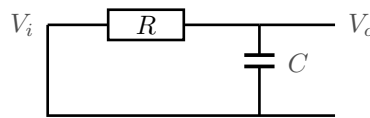Q37. A first-order RC low-pass filter has $R = 1 \text{ k}\Omega$ and $C = 1 \mu\text{F}$, as shown. Its -3 dB cut-off frequency, $f_c = \frac{1}{2\pi RC}$, is nearest to: [2 marks]



- (A) 1000 Hz
- (B) 6.28 Hz
- (C) 100 Hz
- (D) 159 Hz

Q38. An 8-bit analog-to-digital converter (ADC) has a full-scale input range of 5.12 V. Its resolution (the voltage change corresponding to one LSB), $\Delta = \frac{V_{FS}}{2^n}$, is: [2 marks]

- (A) 20 mV
- (B) 5 mV
- (C) 256 mV
- (D) 40 mV

Q39. An n -bit analog-to-digital converter produces 2^n distinct output codes (quantization levels). The number of quantization levels of a 4-bit ADC is: [2 marks]



- (A) 4
- (B) 8
- (C) 16
- (D) 32

Q40. Applying De Morgan's theorem, the Boolean expression $\overline{A + B}$ simplifies to: [2 marks]

- (A) $\bar{A} + \bar{B}$
- (B) $A \cdot B$
- (C) $\bar{A} \cdot B$
- (D) $\bar{A} \cdot \bar{B}$


Q41. A pure sinusoidal voltage is applied to a measurement circuit. The form factor of the waveform, defined as $\frac{V_{rms}}{V_{avg}}$ where V_{avg} is the average of the full-wave rectified value $\left(= \frac{2V_m}{\pi}\right)$ and $V_{rms} = \frac{V_m}{\sqrt{2}}$, is nearest to: [2 marks]

- (A) 1.0
- (B) 1.11
- (C) 1.57
- (D) 0.707

Power Electronics

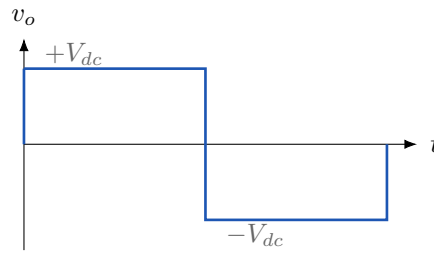Q42. A single-phase full-bridge (square-wave) voltage-source inverter operates from a d.c. input of $V_{dc} = 200$ V, producing the square-wave output shown that swings between $+V_{dc}$ and $-V_{dc}$. The r.m.s. value of this output voltage is: [2 marks]






- (A) 200 V
- (B) 141 V
- (C) 100 V
- (D) 283 V

Q43. A single-phase half-bridge (square-wave) inverter operates from a d.c. input of $V_{dc} = 200$ V, so its output swings between $+V_{dc}/2$ and $-V_{dc}/2$. The r.m.s. value of this output voltage is: [2 marks]

- (A) 200 V
- (B) 100 V
- (C) 141 V
- (D) 50 V

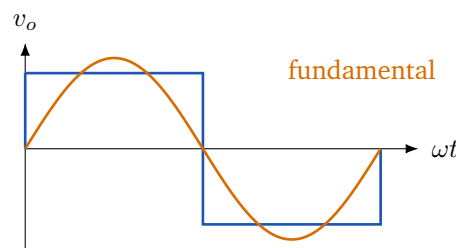Q44. A single-phase full-bridge square-wave inverter has an output that swings between $+V_{dc}$ and $-V_{dc}$ with $V_{dc} = 100$ V. From Fourier analysis the r.m.s. value of the fundamental component, $V_{1,rms} = \frac{4}{\pi} \cdot \frac{V_{dc}}{\sqrt{2}} \approx 0.9 V_{dc}$, is: [2 marks]




- (A) 100 V
- (B) 90 V
- (C) 45 V



(D) 127 V

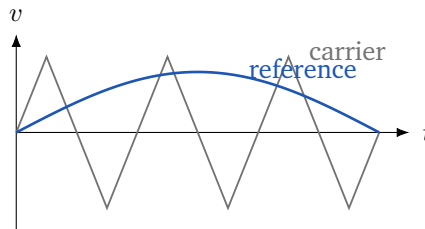- Q45.** In a single-phase sinusoidal-PWM (SPWM) inverter, a sinusoidal reference (modulating) signal of peak 8 V is compared with a triangular carrier of peak 10 V, as sketched. The amplitude modulation index, $m_a = \frac{\hat{V}_{control}}{\hat{V}_{tri}}$, is: [2 marks]



- (A) 1.25
 (B) 10
 (C) 0.2
 (D) 0.8
- Q46.** A single-phase square-wave inverter produces a fundamental output at 50 Hz. Since the square wave contains only odd harmonics, the lowest-order harmonic present is the third; its frequency, $f_3 = 3f_1$, is: [2 marks]
- (A) 50 Hz
 (B) 150 Hz
 (C) 100 Hz
 (D) 250 Hz



Detailed Solutions

Q1.

Solution

Concept – maximum power transfer theorem: A resistive load draws maximum power from a source network when the load resistance is made equal to the Thevenin resistance of that network, $R_L = R_{th}$.

Step 1 – read the Thevenin data: $V_{th} = 20 \text{ V}$, $R_{th} = 10 \Omega$.

Step 2 – apply the matching condition: The maximum-power condition is independent of V_{th} and depends only on R_{th} .

Step 3 – set the load equal to the Thevenin resistance: $R_L = R_{th} = 10 \Omega$

Step 4 – interpret: With $R_L = 10 \Omega$ the source and load impedances are matched, giving the largest possible load power.

Final Answer: $R_L = 10 \Omega \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q1](#)

Q2.

Solution

Concept – superposition theorem: The response at the node is the algebraic sum of the responses produced by each independent source acting alone, with the other voltage sources short-circuited.

Step 1 – keep the 12 V source, short the 6 V source: The node then sees its own 6Ω load in parallel with the shorted branch's 6Ω .

Step 2 – combine that parallel pair: $6 \parallel 6 = \frac{6 \times 6}{6 + 6} = 3 \Omega$

Step 3 – form the divider for the 12 V source through its series 6Ω : $V' = 12 \times \frac{3}{6 + 3} = 12 \times \frac{3}{9} = 4 \text{ V}$

Step 4 – keep the 6 V source, short the 12 V source: By identical symmetry the node again sees $6 \parallel 6 = 3 \Omega$ facing the series 6Ω .

Step 5 – form the divider for the 6 V source: $V'' = 6 \times \frac{3}{6 + 3} = 6 \times \frac{3}{9} = 2 \text{ V}$

Step 6 – add the two contributions: $V = V' + V'' = 4 + 2 = 6 \text{ V}$

Final Answer: $V = 6 \text{ V} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q2](#)



Q3.

Solution

Concept – power delivered at maximum power transfer: When $R_L = R_{th}$, the power delivered to the load is $P_{\max} = \frac{V_{th}^2}{4R_{th}}$.

Step 1 – list the data: $V_{th} = 30 \text{ V}$, $R_{th} = 15 \Omega$.

Step 2 – square the Thevenin voltage: $V_{th}^2 = 30^2 = 900$

Step 3 – form the denominator: $4R_{th} = 4 \times 15 = 60$

Step 4 – divide: $P_{\max} = \frac{900}{60}$

$P_{\max} = 15 \text{ W}$

Final Answer: $P_{\max} = 15 \text{ W} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q3](#)

Q4.

Solution

Concept – Thevenin resistance by reduction: With all independent sources deactivated, series and parallel combinations are reduced step by step to a single equivalent resistance across the terminals.

Step 1 – combine the two parallel resistors: $6 \parallel 3 = \frac{6 \times 3}{6 + 3} = \frac{18}{9} = 2 \Omega$

Step 2 – add the series 4Ω in front of that parallel block: $R_{th} = 4 + 2$

Step 3 – evaluate: $R_{th} = 6 \Omega$

Step 4 – sanity check: The 2Ω parallel block plus the 4Ω series element must exceed 4Ω , and $6 > 4$, so the result is consistent.

Final Answer: $R_{th} = 6 \Omega \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q4](#)

Q5.

Solution

Concept – time constant of an RL circuit: For a first-order RL circuit the time constant is $\tau = \frac{L}{R}$.

Step 1 – list the data: $L = 0.5 \text{ H}$, $R = 10 \Omega$.

Step 2 – substitute: $\tau = \frac{0.5}{10}$

Step 3 – evaluate: $\tau = 0.05 \text{ s}$



Step 4 – convert to milliseconds: $\tau = 50 \text{ ms}$

Final Answer: $\tau = 50 \text{ ms} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q5](#)

Q6.

Solution

Concept – efficiency at maximum power transfer: At the matched condition the load and the source (Thevenin) resistances are equal, so the total series current dissipates equal power in each.

Step 1 – write the two dissipations: Load power $= I^2 R_L$ and internal loss $= I^2 R_{th}$, with the same current I .

Step 2 – use the matching condition $R_L = R_{th}$: Both dissipations are therefore equal.

Step 3 – form the efficiency: $\eta = \frac{I^2 R_L}{I^2 R_L + I^2 R_{th}} = \frac{R_L}{R_L + R_{th}}$

Step 4 – substitute $R_L = R_{th}$: $\eta = \frac{R_{th}}{2R_{th}} = \frac{1}{2}$

Step 5 – express as a percentage: $\eta = 50\%$

Why the other options are wrong:

- A, 100%: would need zero source resistance, which contradicts matching.
- C and D: neither 75% nor 25% corresponds to equal load and source resistances.

Final Answer: $\eta = 50\% \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q6](#)

Q7.

Solution

Concept – current-divider rule: For two resistors in parallel fed by a current source, the current in one branch is the source current times the *opposite* resistor over the sum, $I_1 = I_s \frac{R_2}{R_1 + R_2}$.

Step 1 – identify the branches: $R_1 = 2 \Omega$ (the branch of interest), $R_2 = 4 \Omega$, $I_s = 6 \text{ A}$.

Step 2 – form the denominator: $R_1 + R_2 = 2 + 4 = 6 \Omega$



Step 3 – apply the divider using the opposite resistance: $I_{2\Omega} = 6 \times \frac{4}{6}$

Step 4 – evaluate: $I_{2\Omega} = 4 \text{ A}$

Step 5 – sanity check: The smaller resistor carries the larger share, so its current (4 A) exceeds half of 6 A; consistent.

Final Answer: $I_{2\Omega} = 4 \text{ A} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q7](#)

Q8.

Solution

Concept – parallel-plate capacitor with a dielectric: $C = \frac{\epsilon_0 \epsilon_r A}{d}$, where ϵ_r is the relative permittivity of the filling dielectric.

Step 1 – list the data in base units: $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$, $\epsilon_r = 5$, $A = 0.01 \text{ m}^2$, $d = 0.5 \text{ mm} = 0.5 \times 10^{-3} \text{ m}$.

Step 2 – form the numerator $\epsilon_0 \epsilon_r A$: $\epsilon_0 \epsilon_r A = (8.854 \times 10^{-12}) \times 5 \times 0.01$
 $\epsilon_0 \epsilon_r A = 4.427 \times 10^{-13}$

Step 3 – divide by the separation: $C = \frac{4.427 \times 10^{-13}}{0.5 \times 10^{-3}}$

Step 4 – combine the numbers and powers of ten: $C = 8.854 \times 10^{-10} \text{ F}$

Step 5 – convert to picofarads: $C = 885.4 \text{ pF} \approx 885 \text{ pF}$

Final Answer: $C \approx 885 \text{ pF} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q8](#)

Q9.

Solution

Concept – electrostatic energy density: The energy stored per unit volume of an electric field in free space is $u = \frac{1}{2} \epsilon_0 E^2$.

Step 1 – list the data: $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$, $E = 1 \times 10^6 \text{ V/m}$.

Step 2 – square the field: $E^2 = (1 \times 10^6)^2 = 1 \times 10^{12} \text{ V}^2/\text{m}^2$

Step 3 – substitute into the energy-density formula: $u = \frac{1}{2} \times (8.854 \times 10^{-12}) \times (1 \times 10^{12})$

Step 4 – combine the powers of ten: $(8.854 \times 10^{-12}) \times (1 \times 10^{12}) = 8.854$

Step 5 – take one-half: $u = \frac{1}{2} \times 8.854 = 4.427 \text{ J/m}^3 \approx 4.43 \text{ J/m}^3$



Final Answer: $u \approx 4.43 \text{ J/m}^3 \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q9](#)

Q10.

Solution

Concept – energy of an isolated (charge-fixed) capacitor with a dielectric: For a capacitor whose charge Q is held constant, $W = \frac{Q^2}{2C}$. Inserting a dielectric of relative permittivity ϵ_r multiplies the capacitance by ϵ_r , so the energy falls by the factor ϵ_r .

Step 1 – note the initial energy: $W_1 = 8 \text{ J}$, with charge Q fixed after disconnection.

Step 2 – write how capacitance changes: The dielectric $\epsilon_r = 4$ raises the capacitance to $C' = 4C$.

Step 3 – write how the energy changes at fixed Q : $W_2 = \frac{Q^2}{2C'} = \frac{Q^2}{2(4C)} = \frac{1}{4} \cdot \frac{Q^2}{2C} = \frac{W_1}{4}$

Step 4 – substitute the number: $W_2 = \frac{8}{4}$

Step 5 – evaluate: $W_2 = 2 \text{ J}$

Why the other options are wrong:

- A, 32 J: multiplies rather than divides by ϵ_r (that is the constant-voltage case, wrong here).
- C, 4 J: uses a factor of 2 instead of 4.

Final Answer: $W_2 = 2 \text{ J} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q10](#)

Q11.

Solution

Concept – capacitors in parallel: Capacitances in parallel add directly, $C_{eq} = C_1 + C_2$.

Step 1 – list the data: $C_1 = 4 \mu\text{F}$, $C_2 = 8 \mu\text{F}$.

Step 2 – add the two values: $C_{eq} = 4 + 8$

Step 3 – evaluate: $C_{eq} = 12 \mu\text{F}$



Step 4 – sanity check: A parallel combination is always larger than either capacitor, and $12 > 8$, so the result is consistent.

Final Answer: $C_{eq} = 12 \mu\text{F} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q11](#)

Q12.

Solution

Concept – Nyquist sampling theorem: A band-limited signal with highest frequency f_m must be sampled at a rate of at least $f_s = 2f_m$ to allow exact reconstruction without aliasing.

Step 1 – read the maximum frequency: $f_m = 4 \text{ kHz}$ (the spectrum is zero beyond this).

Step 2 – apply the Nyquist criterion: $f_s = 2f_m = 2 \times 4$

Step 3 – evaluate: $f_s = 8 \text{ kHz}$

Step 4 – interpret: Sampling any slower than 8 kHz would fold the high-frequency content back into the baseband (aliasing).

Final Answer: $f_s = 8 \text{ kHz} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q12](#)

Q13.

Solution

Concept – time-shifting property of the Fourier transform: A delay in time corresponds to multiplication by a linear-phase term in frequency, $x(t - t_0) \longleftrightarrow X(\omega) e^{-j\omega t_0}$.

Step 1 – start from the definition of the transform of the shifted signal:

$$\mathcal{F}\{x(t - t_0)\} = \int_{-\infty}^{\infty} x(t - t_0) e^{-j\omega t} dt$$

Step 2 – substitute $\tau = t - t_0$ (so $t = \tau + t_0$, $dt = d\tau$): $= \int_{-\infty}^{\infty} x(\tau) e^{-j\omega(\tau + t_0)} d\tau$

Step 3 – pull the constant phase factor out of the integral: $= e^{-j\omega t_0} \int_{-\infty}^{\infty} x(\tau) e^{-j\omega \tau} d\tau$

Step 4 – recognise the remaining integral as $X(\omega)$: $= X(\omega) e^{-j\omega t_0}$

Step 5 – interpret: A pure time delay changes only the phase (not the magnitude) of the spectrum.



Why the other options are wrong:

- A, $X(\omega - \omega_0)$: that is the frequency-shift (modulation) property.
- B, $e^{+j\omega t_0}$: has the wrong sign, corresponding to a time *advance*.
- D, $X(-\omega)$: that is the time-reversal property.

Final Answer: $X(\omega) e^{-j\omega t_0} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q13](#)

Q14.

Solution

Concept – aliasing due to under-sampling: When a sinusoid of frequency f is sampled at $f_s < 2f$, it appears at the folded frequency $f_a = |f - f_s|$ (for this range).

Step 1 – list the data: $f = 5$ kHz, $f_s = 8$ kHz.

Step 2 – check that aliasing occurs: The Nyquist rate would be $2 \times 5 = 10$ kHz, and $8 < 10$, so the signal is under-sampled.

Step 3 – compute the alias frequency: $f_a = |5 - 8|$

Step 4 – evaluate: $f_a = 3$ kHz

Step 5 – interpret: The 5 kHz tone masquerades as a 3 kHz tone in the sampled data.

Final Answer: $f_a = 3$ kHz $\Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q14](#)

Q15.

Solution

Concept – Fourier transform of the unit impulse: Using the sifting property, the impulse has a flat (constant) spectrum equal to unity for all ω .

Step 1 – write the defining integral: $\mathcal{F}\{\delta(t)\} = \int_{-\infty}^{\infty} \delta(t) e^{-j\omega t} dt$

Step 2 – apply the sifting property (the impulse picks the value at $t = 0$):
 $= e^{-j\omega \cdot 0}$

Step 3 – evaluate the exponential at $t = 0$: $= e^0 = 1$

Step 4 – interpret: The impulse contains every frequency in equal measure, so its transform is the constant 1.

Why the other options are wrong:



- A and B: $\delta(\omega)$ and $2\pi\delta(\omega)$ are the transforms of a constant (d.c.) signal, the reverse pair.
- C, $1/j\omega$: is (part of) the transform of the unit step, not the impulse.

Final Answer: $\mathcal{F}\{\delta(t)\} = 1 \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q15](#)

Q16.

Solution

Concept – d.c. (average) value of a Fourier series: The average value of a periodic signal over one period equals the constant term a_0 ; every pure sinusoid averages to zero over a whole number of cycles.

Step 1 – identify the terms of $x(t)$: Constant part = 3; oscillatory parts = $2\cos(\omega_0 t)$ and $\sin(2\omega_0 t)$.

Step 2 – average each sinusoid over one fundamental period: $\langle 2\cos(\omega_0 t) \rangle = 0$ and $\langle \sin(2\omega_0 t) \rangle = 0$.

Step 3 – average the constant term: $\langle 3 \rangle = 3$

Step 4 – add the averages: $\bar{x} = 3 + 0 + 0$

Step 5 – state the result: $\bar{x} = 3$

Final Answer: average value = 3 $\Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q16](#)

Q17.

Solution

Concept – frequency of a synchronous generator: The generated frequency is linked to poles P and speed N (rpm) by $f = \frac{PN}{120}$.

Step 1 – list the data: $P = 6$, $N = 1000$ rpm.

Step 2 – form the product PN : $PN = 6 \times 1000 = 6000$

Step 3 – divide by 120: $f = \frac{6000}{120}$

Step 4 – evaluate: $f = 50$ Hz

Final Answer: $f = 50$ Hz $\Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q17](#)



Q18.

Solution

Concept – synchronous speed: A synchronous machine runs exactly at $N_s = \frac{120f}{P}$.

Step 1 – list the data: $f = 50 \text{ Hz}$, $P = 8$.

Step 2 – form the numerator $120f$: $120 \times 50 = 6000$

Step 3 – divide by the number of poles: $N_s = \frac{6000}{8}$

Step 4 – evaluate: $N_s = 750 \text{ rpm}$

Final Answer: $N_s = 750 \text{ rpm} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q18](#)

Q19.

Solution

Concept – voltage regulation of a synchronous generator: Percentage regulation compares the no-load e.m.f. with the full-load terminal voltage, $\text{Reg}\% = \frac{E - V}{V} \times 100$.

Step 1 – list the data: $E = 250 \text{ V}$, $V = 220 \text{ V}$.

Step 2 – find the voltage drop $E - V$: $E - V = 250 - 220 = 30 \text{ V}$

Step 3 – divide by the terminal voltage: $\frac{30}{220} = 0.1364$

Step 4 – convert to a percentage: $\text{Reg}\% = 0.1364 \times 100 = 13.64\% \approx 13.6\%$

Why the other options are wrong:

- C, 30%: takes the raw 30 V drop as a percentage, forgetting to divide by V .
- D, 88%: is V/E , an unrelated ratio.

Final Answer: $\text{Reg} \approx 13.6\% \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q19](#)



Q20.

Solution

Concept – power-angle relation of a cylindrical-rotor generator: The real power delivered is $P = \frac{EV}{X_s} \sin \delta$.

Step 1 – list the data: $E = 1.2$ pu, $V = 1.0$ pu, $X_s = 0.6$ pu, $\delta = 30^\circ$.

Step 2 – evaluate $\sin \delta$: $\sin 30^\circ = 0.5$

Step 3 – form the numerator $EV \sin \delta$: $1.2 \times 1.0 \times 0.5 = 0.6$

Step 4 – divide by the synchronous reactance: $P = \frac{0.6}{0.6}$

Step 5 – evaluate: $P = 1.0$ pu

Final Answer: $P = 1.0$ pu $\Rightarrow$ **A**

Answer: (A) [Go Back to Q20](#)

Q21.

Solution

Concept – slip and rotor speed of an induction motor: The rotor runs slower than the synchronous field by the slip, $N = N_s(1 - s)$.

Step 1 – list the data: $N_s = 1500$ rpm, $s = 0.04$.

Step 2 – form $(1 - s)$: $1 - 0.04 = 0.96$

Step 3 – multiply by the synchronous speed: $N = 1500 \times 0.96$

Step 4 – evaluate: $N = 1440$ rpm

Step 5 – sanity check: The running speed must be just below N_s , and $1440 < 1500$; consistent.

Final Answer: $N = 1440$ rpm $\Rightarrow$ **B**

Answer: (B) [Go Back to Q21](#)

Q22.

Solution

Concept – efficiency of a machine: Efficiency is output over input, and input equals output plus losses, $\eta = \frac{P_{out}}{P_{out} + P_{loss}}$.

Step 1 – list the data: $P_{out} = 100$ kW, $P_{loss} = 5$ kW.

Step 2 – form the input power: $P_{in} = 100 + 5 = 105$ kW



Step 3 – form the efficiency ratio: $\eta = \frac{100}{105}$

Step 4 – evaluate: $\eta = 0.952$

Step 5 – convert to a percentage: $\eta = 95.2\%$

Final Answer: $\eta = 95.2\% \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q22](#)

Q23.

Solution

Concept – rotor (slip) frequency: The frequency of the currents induced in the rotor is the supply frequency scaled by the slip, $f_r = sf$.

Step 1 – list the data: $s = 0.05$, $f = 50$ Hz.

Step 2 – multiply: $f_r = 0.05 \times 50$

Step 3 – evaluate: $f_r = 2.5$ Hz

Step 4 – sanity check: At small slip the rotor frequency is only a few hertz, far below the 50 Hz stator frequency; consistent.

Final Answer: $f_r = 2.5$ Hz $\Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q23](#)

Q24.

Solution

Concept – ABCD parameters of a short line: A short line is modelled by a single series impedance Z with no shunt branch, giving $A = 1$, $B = Z$, $C = 0$, $D = 1$.

Step 1 – recall the two-port relations: $V_S = AV_R + BI_R$ and $I_S = CV_R + DI_R$.

Step 2 – apply the short-line assumptions (no shunt admittance): The sending-end and receiving-end currents are equal, so $C = 0$ and $D = 1$.

Step 3 – relate the voltages through the series drop: $V_S = V_R + ZI_R$, which matches $A = 1$ and $B = Z$.

Step 4 – read off the A parameter: $A = 1$

Final Answer: $A = 1 \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q24](#)



Q25.

Solution

Concept – the B parameter of a short line: For a short line B equals the total series impedance Z (it has units of ohms).

Step 1 – read the series impedance: $Z = (10 + j40) \Omega$.

Step 2 – identify the B parameter: From $V_S = AV_R + BI_R$ with $A = 1$, the coefficient of I_R is the series impedance.

Step 3 – write the value: $B = Z = (10 + j40) \Omega$

Why the other options are wrong:

- A and B: 1 and 0 are the (dimensionless) A/D and C values, not B .
- C, $(40 + j10) \Omega$: swaps the real and imaginary parts of Z .

Final Answer: $B = (10 + j40) \Omega \Rightarrow \boxed{D}$

Answer: (D) [Go Back to Q25](#)

Q26.

Solution

Concept – determinant property of $ABCD$ parameters: For any passive, reciprocal (bilateral) two-port, the transmission parameters satisfy $AD - BC = 1$.

Step 1 – state the reciprocity condition: A transmission line is a passive reciprocal network.

Step 2 – apply the property: $AD - BC = 1$

Step 3 – verify with the short-line values ($A = D = 1$, $B = Z$, $C = 0$):
 $AD - BC = (1)(1) - (Z)(0) = 1 - 0 = 1$

Step 4 – state the result: The determinant is 1 regardless of the line length.

Final Answer: $AD - BC = 1 \Rightarrow \boxed{D}$

Answer: (D) [Go Back to Q26](#)



Q27.

Solution

Concept – surge (characteristic) impedance: For a lossless line $Z_c = \sqrt{L/C}$, using per-kilometre values of L and C .

Step 1 – list the data in base units: $L = 1.6 \text{ mH/km} = 1.6 \times 10^{-3} \text{ H/km}$,
 $C = 0.01 \text{ } \mu\text{F/km} = 1 \times 10^{-8} \text{ F/km}$.

Step 2 – form the ratio L/C : $\frac{L}{C} = \frac{1.6 \times 10^{-3}}{1 \times 10^{-8}}$

Step 3 – combine the powers of ten: $\frac{L}{C} = 1.6 \times 10^5$

Step 4 – take the square root: $Z_c = \sqrt{1.6 \times 10^5} = \sqrt{160000}$

Step 5 – evaluate: $Z_c = 400 \text{ } \Omega$

Final Answer: $Z_c = 400 \text{ } \Omega \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q27](#)

Q28.

Solution

Concept – power transfer across a reactance: The real power sent over a lossless line is $P = \frac{V_1 V_2}{X} \sin \delta$.

Step 1 – list the data: $V_1 = V_2 = 1.0 \text{ pu}$, $X = 0.25 \text{ pu}$, $\delta = 30^\circ$.

Step 2 – evaluate $\sin \delta$: $\sin 30^\circ = 0.5$

Step 3 – form the numerator $V_1 V_2 \sin \delta$: $1.0 \times 1.0 \times 0.5 = 0.5$

Step 4 – divide by the reactance: $P = \frac{0.5}{0.25}$

Step 5 – evaluate: $P = 2 \text{ pu}$

Final Answer: $P = 2 \text{ pu} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q28](#)

Q29.

Solution

Concept – three-phase (symmetrical) fault current: For a bolted three-phase fault fed through a reactance X from source e.m.f. E , the per-unit fault current is $I_f = \frac{E}{X}$.

Step 1 – list the data: $E = 1.0 \text{ pu}$, $X = 0.25 \text{ pu}$.



Step 2 – form the ratio: $I_f = \frac{1.0}{0.25}$

Step 3 – evaluate: $I_f = 4$ pu

Step 4 – interpret: A per-unit fault current of 4 means four times the base current flows into the fault.

Final Answer: $I_f = 4$ pu $\Rightarrow$ **B**

Answer: (B) [Go Back to Q29](#)

Q30.

Solution

Concept – base impedance in per-unit analysis: $Z_{base} = \frac{(kV_{base})^2}{MVA_{base}}$.

Step 1 – list the data: $kV_{base} = 20$ kV, $MVA_{base} = 200$ MVA.

Step 2 – square the base voltage: $(20)^2 = 400$

Step 3 – divide by the base MVA: $Z_{base} = \frac{400}{200}$

Step 4 – evaluate: $Z_{base} = 2 \Omega$

Final Answer: $Z_{base} = 2 \Omega \Rightarrow$ **C**

Answer: (C) [Go Back to Q30](#)

Q31.

Solution

Concept – poles from the state matrix: The poles (natural modes) of a state-space system are the eigenvalues of A , i.e. the roots of $\det(sI - A) = 0$.

Step 1 – form $sI - A$: $sI - A = \begin{bmatrix} s & -1 \\ 2 & s+3 \end{bmatrix}$

Step 2 – take the determinant: $\det(sI - A) = s(s+3) - (-1)(2)$

Step 3 – expand: $= s^2 + 3s + 2$

Step 4 – factor the characteristic polynomial: $s^2 + 3s + 2 = (s+1)(s+2)$

Step 5 – read the roots: $s = -1$ and $s = -2$

Final Answer: poles at $-1, -2 \Rightarrow$ **C**

Answer: (C) [Go Back to Q31](#)



Q32.

Solution

Concept – controllability test: A system of order n is completely controllable if its controllability matrix $Q_c = [B \ AB \ \dots \ A^{n-1}B]$ has full rank n (equivalently, a non-zero determinant for a square Q_c).

Step 1 – compute AB : $AB = \begin{bmatrix} 0 & 1 \\ 0 & -2 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 1 \\ -2 \end{bmatrix}$

Step 2 – assemble the controllability matrix: $Q_c = [B \ AB] = \begin{bmatrix} 0 & 1 \\ 1 & -2 \end{bmatrix}$

Step 3 – evaluate its determinant: $\det Q_c = (0)(-2) - (1)(1) = -1$

Step 4 – test the rank: $\det Q_c = -1 \neq 0$, so Q_c has full rank 2.

Step 5 – conclude: The system is completely controllable.

Final Answer: completely controllable $\Rightarrow$ **A**

Answer: (A) [Go Back to Q32](#)

Q33.

Solution

Concept – damping ratio of a second-order system: Comparing $s^2 + 2\zeta\omega_n s + \omega_n^2$ with the given polynomial gives ω_n and then ζ .

Step 1 – match the constant term to ω_n^2 : $\omega_n^2 = 16 \Rightarrow \omega_n = 4 \text{ rad/s}$

Step 2 – match the middle term to $2\zeta\omega_n$: $2\zeta\omega_n = 4$

Step 3 – substitute $\omega_n = 4$: $2\zeta(4) = 4 \Rightarrow 8\zeta = 4$

Step 4 – solve for ζ : $\zeta = \frac{4}{8} = 0.5$

Step 5 – interpret: $\zeta = 0.5$ describes an under-damped response ($0 < \zeta < 1$).

Final Answer: $\zeta = 0.5 \Rightarrow$ **C**

Answer: (C) [Go Back to Q33](#)

Q34.

Solution

Concept – stability from eigenvalue location: A linear time-invariant system is stable only if every eigenvalue of A lies in the left half of the s -plane (negative real part). A single eigenvalue with positive real part makes it unstable.

Step 1 – list the eigenvalues: $s_1 = -2$ (left half-plane) and $s_2 = +1$ (right half-



plane).

Step 2 – test each against the stability requirement: $s_1 = -2$ is fine, but $s_2 = +1$ has a positive real part.

Step 3 – apply the stability rule: Even one right-half-plane pole produces an unbounded growing mode (e^{+t}).

Step 4 – conclude: The system is unstable.

Final Answer: unstable $\Rightarrow$ D

Answer: (D) [Go Back to Q34](#)

Q35.

Solution

Concept – d.c. gain of a closed-loop system: The closed-loop transfer function is $\frac{G(s)}{1 + G(s)}$; its d.c. gain is that expression evaluated at $s = 0$.

Step 1 – evaluate $G(0)$: $G(0) = \frac{10}{0 + 5} = \frac{10}{5} = 2$

Step 2 – form the closed-loop d.c. gain: $\left. \frac{C}{R} \right|_{s=0} = \frac{G(0)}{1 + G(0)} = \frac{2}{1 + 2}$

Step 3 – add the denominator: $1 + 2 = 3$

Step 4 – divide: $\frac{2}{3} = 0.667$

Step 5 – interpret: Feedback pulls the d.c. gain below unity toward 0.667.

Final Answer: d.c. gain = 0.667 $\Rightarrow$ D

Answer: (D) [Go Back to Q35](#)

Q36.

Solution

Concept – non-inverting amplifier gain: For an ideal op-amp in the non-inverting configuration the closed-loop gain is $A_v = 1 + \frac{R_f}{R_1}$.

Step 1 – list the data: $R_1 = 10 \text{ k}\Omega$, $R_f = 20 \text{ k}\Omega$.

Step 2 – form the resistor ratio: $\frac{R_f}{R_1} = \frac{20}{10} = 2$

Step 3 – add the unity term: $A_v = 1 + 2$

Step 4 – evaluate: $A_v = 3$

Step 5 – sanity check: A non-inverting gain is always at least 1, and $3 > 1$; consistent.



Why the other options are wrong:

- A, 2: uses only R_f/R_1 and forgets the +1 (that would be an inverting-magnitude value).
- D, 0.5: inverts the ratio.

Final Answer: $A_v = 3 \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q36](#)

Q37.

Solution

Concept – cut-off frequency of an RC low-pass filter: The -3 dB corner frequency is $f_c = \frac{1}{2\pi RC}$.

Step 1 – list the data in base units: $R = 1 \text{ k}\Omega = 1 \times 10^3 \Omega$, $C = 1 \mu\text{F} = 1 \times 10^{-6} \text{ F}$.

Step 2 – form the product RC : $RC = (1 \times 10^3) \times (1 \times 10^{-6}) = 1 \times 10^{-3} \text{ s}$

Step 3 – form $2\pi RC$: $2\pi RC = 2\pi \times 10^{-3} = 6.283 \times 10^{-3}$

Step 4 – take the reciprocal: $f_c = \frac{1}{6.283 \times 10^{-3}}$

Step 5 – evaluate: $f_c = 159.2 \text{ Hz} \approx 159 \text{ Hz}$

Why the other options are wrong:

- A, 1000 Hz: uses $1/RC$ but forgets the 2π .
- B, 6.28 Hz: is $2\pi RC$ expressed wrongly as a frequency.

Final Answer: $f_c \approx 159 \text{ Hz} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q37](#)

Q38.

Solution

Concept – ADC resolution: The smallest resolvable voltage (one LSB) is the full-scale range divided by the number of steps, $\Delta = \frac{V_{FS}}{2^n}$.

Step 1 – list the data: $V_{FS} = 5.12 \text{ V}$, $n = 8$ bits.

Step 2 – find the number of steps: $2^n = 2^8 = 256$

Step 3 – divide the full scale by the number of steps: $\Delta = \frac{5.12}{256}$



Step 4 – evaluate: $\Delta = 0.02 \text{ V}$

Step 5 – convert to millivolts: $\Delta = 20 \text{ mV}$

Final Answer: $\Delta = 20 \text{ mV} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q38](#)

Q39.

Solution

Concept – quantization levels of an ADC: An n -bit converter resolves the input into 2^n distinct levels.

Step 1 – note the number of bits: $n = 4$.

Step 2 – raise two to that power: $2^4 = 2 \times 2 \times 2 \times 2$

Step 3 – evaluate: $2^4 = 16$

Step 4 – state the result: The 4-bit ADC has 16 quantization levels.

Final Answer: 16 levels $\Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q39](#)

Q40.

Solution

Concept – De Morgan's theorem: The complement of a sum equals the product of the complements, $\overline{A + B} = \bar{A} \cdot \bar{B}$.

Step 1 – identify the operation: The bar covers the whole OR expression $A + B$.

Step 2 – apply De Morgan (OR becomes AND, complement each variable):
 $\overline{A + B} = \bar{A} \cdot \bar{B}$

Step 3 – verify with a test row ($A = 0, B = 0$): LHS = $\overline{0 + 0} = \bar{0} = 1$; RHS = $\bar{0} \cdot \bar{0} = 1 \cdot 1 = 1$. They agree.

Step 4 – state the simplified form: $Y = \bar{A} \cdot \bar{B}$

Why the other options are wrong:

- $A, \bar{A} + \bar{B}$: is $\overline{A \cdot B}$, the dual (mixes up the operator).

Final Answer: $\bar{A} \cdot \bar{B} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q40](#)



Q41.

Solution

Concept – form factor of a sinusoid: Form factor $= \frac{V_{rms}}{V_{avg}}$, where for a sinusoid $V_{rms} = \frac{V_m}{\sqrt{2}}$ and the (full-wave) average is $V_{avg} = \frac{2V_m}{\pi}$.

Step 1 – write the RMS value: $V_{rms} = \frac{V_m}{\sqrt{2}} = 0.707 V_m$

Step 2 – write the average value: $V_{avg} = \frac{2V_m}{\pi} = 0.637 V_m$

Step 3 – form the ratio (the V_m cancels): $FF = \frac{0.707 V_m}{0.637 V_m} = \frac{0.707}{0.637}$

Step 4 – evaluate: $FF = 1.11$

Step 5 – cross-check with the closed form: $\frac{\pi}{2\sqrt{2}} = \frac{3.1416}{2.828} = 1.11$; consistent.

Why the other options are wrong:

- C, 1.57: is the peak factor V_m/V_{avg} , not the form factor.
- D, 0.707: is V_{rms}/V_m , a different ratio.

Final Answer: form factor = 1.11 $\Rightarrow$ **B**

Answer: (B) [Go Back to Q41](#)

Q42.

Solution

Concept – RMS of a full-bridge square-wave inverter output: The output equals $+V_{dc}$ for one half period and $-V_{dc}$ for the other, so its magnitude is always V_{dc} ; hence the RMS value equals V_{dc} .

Step 1 – write the RMS integral for a square wave: $V_{rms} = \sqrt{\frac{1}{T} \int_0^T v_o^2 dt}$

Step 2 – note that $v_o^2 = V_{dc}^2$ throughout the period: Both half-cycles give $(\pm V_{dc})^2 = V_{dc}^2$.

Step 3 – carry out the average of a constant: $\frac{1}{T} \int_0^T V_{dc}^2 dt = V_{dc}^2$

Step 4 – take the square root: $V_{rms} = \sqrt{V_{dc}^2} = V_{dc}$

Step 5 – substitute the value: $V_{rms} = 200 \text{ V}$

Final Answer: $V_{rms} = 200 \text{ V} \Rightarrow$ **A**



Answer: (A) [Go Back to Q42](#)

Q43.

Solution

Concept – RMS of a half-bridge square-wave inverter output: A half-bridge output swings between $+V_{dc}/2$ and $-V_{dc}/2$; its magnitude is always $V_{dc}/2$, so the RMS value is $V_{dc}/2$.

Step 1 – write the peak magnitude: $|v_o| = \frac{V_{dc}}{2} = \frac{200}{2} = 100 \text{ V}$

Step 2 – note the square-wave RMS equals its magnitude: Since $v_o^2 = (V_{dc}/2)^2$ over the whole period,

Step 3 – evaluate the RMS: $V_{rms} = \frac{V_{dc}}{2} = 100 \text{ V}$

Step 4 – compare with the full-bridge case: The half-bridge delivers half the RMS voltage of a full bridge on the same V_{dc} .

Final Answer: $V_{rms} = 100 \text{ V} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q43](#)

Q44.

Solution

Concept – fundamental component of a square wave: The Fourier series of a $\pm V_{dc}$ square wave has a fundamental of peak $\frac{4V_{dc}}{\pi}$, whose RMS is $\frac{4V_{dc}}{\pi\sqrt{2}} \approx 0.9 V_{dc}$.

Step 1 – write the fundamental peak: $\hat{V}_1 = \frac{4V_{dc}}{\pi} = \frac{4 \times 100}{3.1416} = 127.3 \text{ V}$

Step 2 – convert the peak to RMS: $V_{1,rms} = \frac{\hat{V}_1}{\sqrt{2}} = \frac{127.3}{1.414}$

Step 3 – evaluate: $V_{1,rms} = 90 \text{ V}$

Step 4 – cross-check with the $0.9 V_{dc}$ shortcut: $0.9 \times 100 = 90 \text{ V}$; consistent.

Why the other options are wrong:

- A, 100 V: is the total RMS (all harmonics), not the fundamental alone.
- D, 127 V: is the fundamental *peak*, before converting to RMS.

Final Answer: $V_{1,rms} = 90 \text{ V} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q44](#)



Q45.

Solution

Concept – amplitude modulation index in SPWM: The amplitude modulation index is the ratio of the reference (control) peak to the carrier (triangle) peak,

$$m_a = \frac{\hat{V}_{control}}{\hat{V}_{tri}}.$$

Step 1 – list the data: $\hat{V}_{control} = 8 \text{ V}$, $\hat{V}_{tri} = 10 \text{ V}$.

Step 2 – form the ratio: $m_a = \frac{8}{10}$

Step 3 – evaluate: $m_a = 0.8$

Step 4 – interpret: $m_a = 0.8 < 1$, so the inverter operates in the linear (under-modulated) region.

Why the other options are wrong:

- A, 1.25: inverts the ratio (carrier over control).
- B, 10: uses only the carrier peak.

Final Answer: $m_a = 0.8 \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q45](#)

Q46.

Solution

Concept – harmonics of a square wave: An ideal square wave has half-wave symmetry, so it contains only odd harmonics (1, 3, 5, ...); the lowest above the fundamental is the third, at $f_3 = 3f_1$.

Step 1 – note the fundamental frequency: $f_1 = 50 \text{ Hz}$.

Step 2 – identify the lowest harmonic present: Even harmonics are absent, so the lowest is the third.

Step 3 – compute its frequency: $f_3 = 3 \times 50$

Step 4 – evaluate: $f_3 = 150 \text{ Hz}$

Why the other options are wrong:

- A, 50 Hz: is the fundamental itself, not a harmonic.
- C, 100 Hz: is the second harmonic, which a symmetric square wave does not contain.

Final Answer: $f_3 = 150 \text{ Hz} \Rightarrow \boxed{\text{B}}$



Answer: (B) [Go Back to Q46](#)



Answer Key

Q	Ans	Q	Ans	Q	Ans	Q	Ans	Q	Ans
1	C	2	B	3	A	4	C	5	A
6	B	7	A	8	A	9	D	10	D
11	C	12	B	13	C	14	A	15	D
16	B	17	A	18	C	19	B	20	A
21	B	22	D	23	C	24	A	25	D
26	D	27	A	28	B	29	B	30	C
31	C	32	A	33	C	34	D	35	D
36	C	37	D	38	A	39	C	40	D
41	B	42	A	43	B	44	B	45	D
46	B								

