

GATE Electrical Engineering

Sample Paper – 6

Duration: 128 Minutes


Maximum Marks: 72

Instructions

- This paper contains **46 questions** covering the core **Electrical Engineering** subject of the GATE paper conducted by the IITs and IISc (General Aptitude and Engineering Mathematics are provided as separate papers).
- **Q1–Q20 carry 1 mark each and Q21–Q46 carry 2 marks each**, for a total of **72 marks**.
- Each question carries **negative marking of one-third of its allotted marks**: a wrong 1-mark question costs **0.33** and a wrong 2-mark question costs **0.67**. Unattempted questions carry no penalty.
- Every question here is a single-correct **MCQ**. The real GATE paper also has Multiple Select (MSQ) and Numerical Answer Type (NAT) questions, and **those carry no negative marking**.
- Attempt this paper in one timed sitting of about **128 minutes**, the share this core subject earns at GATE's overall pace of 180 minutes for 65 questions. Unless stated otherwise take $\varepsilon_0 = 8.854 \times 10^{-12}$ F/m, $\mu_0 = 4\pi \times 10^{-7}$ H/m and $c = 3 \times 10^8$ m/s.

Electric Circuits

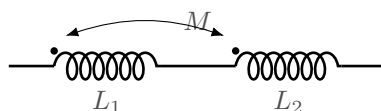- Q1.** Two magnetically coupled coils of self-inductances $L_1 = 4$ H and $L_2 = 6$ H, with a mutual inductance $M = 2$ H, are connected in **series-aiding** (their dots at the joined end), as shown. The equivalent inductance seen at the terminals is: [1 mark]



(A) 14 H




- (B) 2 H
- (C) 6 H
- (D) 10 H

Q2. Two coils have self-inductances $L_1 = 8 \text{ mH}$ and $L_2 = 2 \text{ mH}$ and a mutual inductance $M = 3 \text{ mH}$. The coefficient of coupling $k = \frac{M}{\sqrt{L_1 L_2}}$ is: [1 mark]

- (A) 0.5
- (B) 0.75
- (C) 1
- (D) 0.375

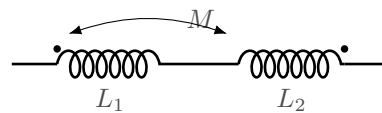Q3. The same two coupled coils, now of $L_1 = 5 \text{ H}$ and $L_2 = 7 \text{ H}$ with $M = 1.5 \text{ H}$, are connected in **series-opposing** (dots at opposite ends), as shown. The equivalent inductance is: [1 mark]



- (A) 15 H
- (B) 12 H
- (C) 6 H
- (D) 9 H

Q4. A series RLC circuit has $L = 0.5 \text{ H}$ and $C = 200 \mu\text{F}$. Its undamped resonant angular frequency $\omega_0 = \frac{1}{\sqrt{LC}}$ is: [1 mark]

- (A) 100 rad/s
- (B) 200 rad/s
- (C) 50 rad/s
- (D) 10 rad/s



Q5. A series RLC circuit has $R = 4\ \Omega$, $L = 40\text{ mH}$ and $C = 100\ \mu\text{F}$. Its quality factor at resonance, $Q = \frac{1}{R}\sqrt{\frac{L}{C}}$, is: [1 mark]


(A) 10

(B) 2.5

(C) 5

(D) 20

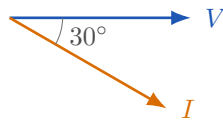Q6. A single-phase load draws a current $I = 10\angle -30^\circ\text{ A}$ when supplied with a voltage $V = 100\angle 0^\circ\text{ V}$, as the phasor diagram shows. The power factor of the load is: [1 mark]




(A) 0.866 lagging

(B) 0.5 lagging

(C) 1

(D) 0.707 lagging

Q7. In the a.c. series circuit shown, a resistance $R = 6\ \Omega$ is in series with an inductive reactance $X_L = 8\ \Omega$. The magnitude of the total impedance $|Z| = \sqrt{R^2 + X_L^2}$ is: [1 mark]

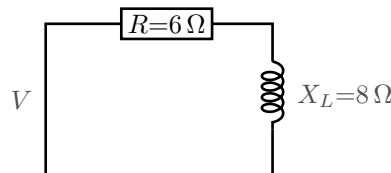

(A) $14\ \Omega$

(B) $48\ \Omega$


(C) $10\ \Omega$

(D) $2\ \Omega$

Electromagnetic Fields



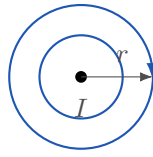- Q8.** A long straight conductor carries a steady current $I = 5$ A. By Ampere's law the magnetic flux density at a radial distance $r = 0.1$ m is $B = \frac{\mu_0 I}{2\pi r}$, as shown. Its value is: [1 mark]




- (A) $5 \mu\text{T}$
(B) $20 \mu\text{T}$
(C) $10 \mu\text{T}$
(D) $1 \mu\text{T}$
- Q9.** An inductor of $L = 2$ H carries a steady current of $I = 3$ A. The energy stored in its magnetic field, $W = \frac{1}{2}LI^2$, is: [1 mark]
- (A) 3 J
(B) 18 J
(C) 6 J
(D) 9 J
- Q10.** A parallel-plate capacitor is charged to $V = 100$ V and its plate separation is $d = 2$ mm, as shown. Assuming a uniform field, the electric field strength between the plates, $E = V/d$, is: [1 mark]



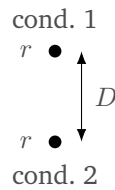- (A) 200 kV/m
(B) 0.05 kV/m
(C) 50 kV/m
(D) 100 kV/m
- Q11.** A single-phase two-wire transmission line has its capacitance between the conductors given by $C_{ab} = \frac{\pi\epsilon_0}{\ln(D/r)}$, with spacing D and radius r



arranged so that $\ln(D/r) = 1$, as shown. The line-to-line capacitance per metre is nearest to: [1 mark]




- (A) 8.85 pF/m
- (B) 55.6 pF/m
- (C) 13.9 pF/m
- (D) 27.8 pF/m

Signals and Systems

Q12. The discrete sequences $x[n] = \{1, 2, 3\}$ (for $n = 0, 1, 2$) and $h[n] = \{1, 1\}$ (for $n = 0, 1$) are linearly convolved to give $y[n] = x[n] * h[n]$. The sample $y[2]$ is: [1 mark]

- (A) 5
- (B) 3
- (C) 2
- (D) 6

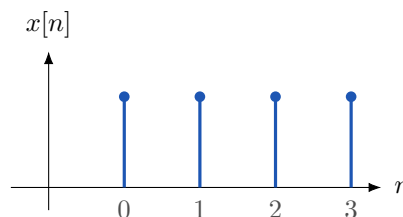Q13. The 4-point DFT of the sequence $x[n] = \{1, 1, 1, 1\}$ (shown as a stem plot below) has a zero-frequency (d.c.) coefficient $X[0] = \sum_{n=0}^3 x[n]$ equal to: [1 mark]



- (A) 4
- (B) 0



(C) 1

(D) 2

Q14. A band-limited continuous-time signal has a highest frequency component of 4 kHz. By the Nyquist sampling theorem the minimum sampling rate needed to avoid aliasing is: [1 mark]

(A) 4 kHz

(B) 2 kHz

(C) 8 kHz

(D) 16 kHz

Q15. Two finite discrete sequences of lengths 6 and 8 samples are convolved linearly. The number of samples in the resulting sequence is: [1 mark]

(A) 14

(B) 13

(C) 48

(D) 7

Q16. An $N = 8$ point DFT is computed by a radix-2 decimation-in-time FFT algorithm. The number of complex multiplications it requires, $\frac{N}{2} \log_2 N$, is: [1 mark]

(A) 64

(B) 8


(C) 24

(D) 12

Electrical Machines

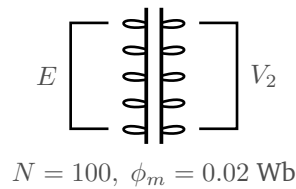Q17. A single-phase transformer has $N = 100$ primary turns and operates at $f = 50$ Hz with a maximum core flux $\phi_m = 0.02$ Wb, as shown. Its induced primary e.m.f., $E = 4.44 f N \phi_m$, is: [1 mark]





- (A) 222 V
- (B) 111 V
- (C) 888 V
- (D) 444 V

Q18. A short-circuit (SC) test on a transformer records a full-load input power of 250 W, which equals the full-load copper loss. Since copper loss varies as the square of the load fraction, the copper loss at **half** load is: [1 mark]

- (A) 125 W
- (B) 62.5 W
- (C) 250 W
- (D) 500 W

Q19. An open-circuit (OC) test on a transformer records an input power of 150 W, which is essentially the constant core (iron) loss. The iron loss when the transformer runs at **half** its rated load is: [1 mark]

- (A) 75 W
- (B) 150 W
- (C) 300 W
- (D) 37.5 W

Q20. A 10 kVA single-phase transformer has a rated secondary voltage of 400 V. Its rated (full-load) secondary current, $I_2 = \frac{\text{kVA} \times 1000}{V_2}$, is: [1 mark]

- (A) 40 A
- (B) 10 A
- (C) 25 A



(D) 4 A

Q21. A single-phase transformer delivers an output of 8 kW. Under this load its core loss is 120 W and its copper loss is 130 W. The efficiency $\eta =$

$\frac{P_{out}}{P_{out} + P_{core} + P_{cu}}$ is nearest to: [2 marks]

(A) 90%

(B) 95%

(C) 98%

(D) 96.97%

Q22. A transformer has a constant iron loss of 200 W and a full-load copper loss of 800 W. Maximum efficiency occurs when the copper loss equals the iron loss; the corresponding fraction of full load is $x = \sqrt{P_i/P_{cu, fl}}$, which is: [2 marks]


(A) 0.25

(B) 0.5

(C) 0.707

(D) 1

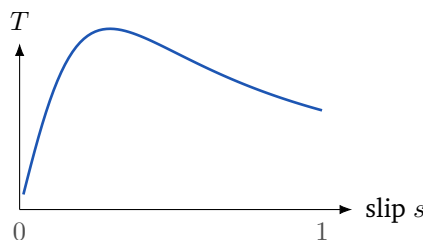Q23. A 6-pole, 50 Hz three-phase induction motor runs with a per-unit slip of $s = 0.04$; its torque-slip curve is sketched below. Using $N_s = \frac{120f}{P}$ and $N = N_s(1 - s)$, the rotor speed is: [2 marks]



(A) 960 rpm

(B) 1000 rpm


(C) 950 rpm



(D) 1440 rpm

Power Systems

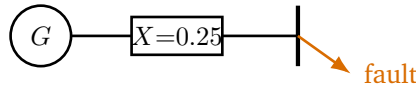- Q24.** A bus is fed from a source through a reactance of $X = 0.25$ pu on a base of 100 MVA, as the single-line diagram shows. For a three-phase symmetrical fault at the bus the short-circuit level $\text{MVA}_{\text{fault}} = \frac{\text{MVA}_{\text{base}}}{X_{\text{pu}}}$ is: [2 marks]




- (A) 250 MVA
 (B) 400 MVA
 (C) 100 MVA
 (D) 25 MVA
- Q25.** The fault level at an 11 kV bus is 400 MVA. The symmetrical short-circuit current $I_{sc} = \frac{\text{MVA}_{\text{fault}} \times 10^6}{\sqrt{3} \times V_L}$, which a switchgear at the bus must interrupt, is nearest to: [2 marks]
- (A) 21 kA
 (B) 36 kA
 (C) 12 kA
 (D) 400 kA
- Q26.** A circuit breaker is to interrupt a symmetrical fault current of 20 kA at a system voltage of 11 kV. Its three-phase symmetrical breaking capacity $S = \sqrt{3} V_L I_{sc}$ is nearest to: [2 marks]
- (A) 381 MVA
 (B) 220 MVA
 (C) 660 MVA
 (D) 127 MVA



Q27. A generator reactance is specified as 0.15 pu on a base of 50 MVA. Referred to a new base of 100 MVA at the same voltage, using $X_{new} = X_{old} \times \frac{\text{MVA}_{new}}{\text{MVA}_{old}}$, its value becomes: [2 marks]

- (A) 0.075 pu
- (B) 0.15 pu
- (C) 0.30 pu
- (D) 0.60 pu

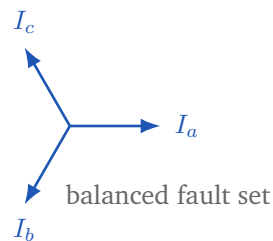Q28. An unloaded generator with pre-fault e.m.f. $E = 1.0$ pu and reactance $X = 0.2$ pu experiences a bolted three-phase symmetrical fault at its terminals; the balanced fault-current phasors are indicated below. The fault current $I_f = \frac{E}{X}$ is: [2 marks]



- (A) 0.2 pu
- (B) 10 pu
- (C) 2 pu
- (D) 5 pu

Q29. Per-unit calculations use a base of 100 MVA and a base voltage of 220 kV. The base impedance $Z_{base} = \frac{(kV_{base})^2}{\text{MVA}_{base}}$ is: [2 marks]

- (A) 484 Ω
- (B) 48.4 Ω
- (C) 242 Ω
- (D) 121 Ω




Q30. A 132 kV (line) transmission line, 100 km long, has a capacitance to neutral of $0.02 \mu\text{F}/\text{km}$ and operates at 50 Hz. Its per-phase charging current $I_c = V_{ph} \omega C$ (with $V_{ph} = 132/\sqrt{3}$ kV and C the total per-phase capacitance) is nearest to: [2 marks]

- (A) 76 A
- (B) 24 A
- (C) 48 A
- (D) 96 A

Control Systems

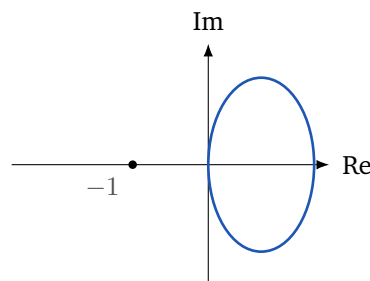Q31. A unity-feedback system has an open-loop transfer function with **no** poles in the right half of the s -plane ($P = 0$). Its Nyquist plot is sketched below and does not enclose the critical point $-1 + j0$. For closed-loop stability the required number of encirclements of -1 (by the Nyquist criterion $N = P - Z$ with $Z = 0$) is: [2 marks]



- (A) 1
- (B) 2
- (C) -1
- (D) 0

Q32. At its phase-crossover frequency (phase = -180°) the open-loop gain magnitude of a system is $|G(j\omega_{pc})| = 0.25$. The gain margin, $\text{GM} = 20 \log_{10} \frac{1}{|G|}$ dB, is: [2 marks]

- (A) 6 dB



- (B) 3 dB
- (C) 0 dB
- (D) 12 dB

Q33. A PID controller is tuned to $G_c(s) = K_p \left(1 + \frac{1}{T_i s} + T_d s \right)$ with $K_p = 5$, $T_i = 0.5$ s and $T_d = 0.1$ s. Its derivative gain, $K_d = K_p T_d$, is: [2 marks]

- (A) 5
- (B) 2.5
- (C) 0.5
- (D) 10

Q34. A unity-feedback system has the open-loop transfer function $G(s) = \frac{10}{s+5}$ (a type-0 system). For a unit-step input the steady-state error, $e_{ss} = \frac{1}{1+K_p}$ with $K_p = \lim_{s \rightarrow 0} G(s)$, is: [2 marks]

- (A) 0
- (B) 0.333
- (C) 0.5
- (D) 1


Q35. A closed-loop system has the characteristic equation $s^2 + 4s + 16 = 0$. Comparing with the standard form $s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$, the damping ratio ζ is: [2 marks]

- (A) 0.25
- (B) 0.5
- (C) 1
- (D) 0.75


Analog, Digital and Measurements



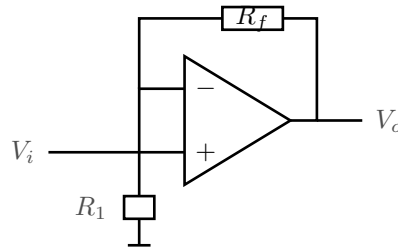- Q36.** For the ideal-op-amp **non-inverting** amplifier shown, $R_1 = 10 \text{ k}\Omega$ (to ground) and $R_f = 90 \text{ k}\Omega$ (feedback). Its closed-loop voltage gain $\frac{V_o}{V_i} = 1 + \frac{R_f}{R_1}$ is: [2 marks]



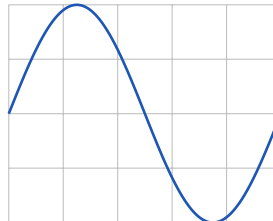- (A) 10
(B) 9
(C) 0.1
(D) 11
- Q37.** On an oscilloscope a sine wave spans 4 vertical divisions from peak to peak, with the vertical sensitivity set to 2 V/div (see the trace). The peak-to-peak voltage, $V_{pp} = (\text{divisions}) \times (\text{V/div})$, is: [2 marks]



- (A) 2 V
(B) 4 V
(C) 16 V
(D) 8 V
- Q38.** On an oscilloscope one full cycle of a periodic signal occupies 4 horizontal divisions, with the time base set to 0.5 ms/div. The signal frequency, $f = \frac{1}{(\text{divisions}) \times (\text{time/div})}$, is: [2 marks]
- (A) 500 Hz



- (B) 250 Hz
- (C) 1 kHz
- (D) 2 kHz

Q39. A decade (mod-10) counter must pass through 10 distinct states. The minimum number of flip-flops required, the smallest n with $2^n \geq 10$, is:
[2 marks]

- (A) 3
- (B) 4
- (C) 10
- (D) 5

Q40. A 3-bit binary ripple counter is clocked at 8 kHz. Each flip-flop halves the frequency, so the most-significant-bit output appears at $\frac{8 \text{ kHz}}{2^3}$, which is:
[2 marks]

- (A) 1 kHz
- (B) 4 kHz
- (C) 8 kHz
- (D) 2 kHz


Q41. The hexadecimal number $(2A)_{16}$ has the decimal (base-10) value: [2 marks]

- (A) 26
- (B) 20
- (C) 32
- (D) 42

Power Electronics

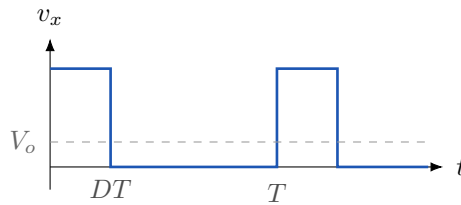Q42. A step-down (buck) DC-DC converter operates from an input of $V_s = 48$ V at a duty ratio $D = 0.25$; its switch-node waveform is shown. In continuous conduction the average output voltage $V_o = D V_s$ is: [2 marks]





- (A) 48 V
- (B) 12 V
- (C) 24 V
- (D) 6 V

Q43. A step-up (boost) DC-DC converter operates from $V_s = 20$ V at a duty ratio $D = 0.5$. In continuous conduction its average output voltage is $V_o = \frac{V_s}{1-D}$, which is: [2 marks]

- (A) 20 V
- (B) 10 V
- (C) 40 V
- (D) 80 V

Q44. A buck-boost DC-DC converter operates from $V_s = 24$ V at a duty ratio $D = 0.6$. The magnitude of its average output voltage is $|V_o| = V_s \frac{D}{1-D}$, which is: [2 marks]

- (A) 16 V
- (B) 24 V
- (C) 36 V
- (D) 14.4 V

Q45. An SMPS uses a buck converter that must produce an average output of 5 V from a 20 V input. The required duty ratio, $D = \frac{V_o}{V_s}$, is: [2 marks]


- (A) 0.5
- (B) 0.25



(C) 0.75

(D) 2

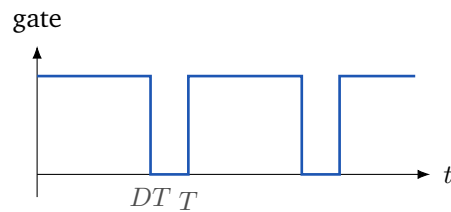Q46. A boost converter in an SMPS must step $V_s = 12\text{ V}$ up to $V_o = 48\text{ V}$, producing the pulse-train switch waveform shown. Using $V_o = \frac{V_s}{1-D}$, the required duty ratio D is: [2 marks]



(A) 0.25

(B) 0.75

(C) 0.5

(D) 0.9



Detailed Solutions

Q1.

Solution

Concept – series-aiding coupled inductors: When two mutually coupled coils are connected in series so that their fluxes add (series-aiding), the equivalent inductance is $L_{eq} = L_1 + L_2 + 2M$.

Step 1 – list the data: $L_1 = 4 \text{ H}$, $L_2 = 6 \text{ H}$, $M = 2 \text{ H}$.

Step 2 – add the two self-inductances: $L_1 + L_2 = 4 + 6 = 10 \text{ H}$

Step 3 – form the mutual term: $2M = 2 \times 2 = 4 \text{ H}$

Step 4 – add the mutual term (aiding is +): $L_{eq} = 10 + 4$

$$L_{eq} = 14 \text{ H}$$

Step 5 – sanity check: Series-aiding must exceed the plain series sum of 10 H, and $14 > 10$, so the sign is right.

Final Answer: $L_{eq} = 14 \text{ H} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q1](#)

Q2.

Solution

Concept – coefficient of coupling: The coupling coefficient links the mutual inductance to the two self-inductances through $k = \frac{M}{\sqrt{L_1 L_2}}$, and always satisfies $0 \leq k \leq 1$.

Step 1 – list the data: $L_1 = 8 \text{ mH}$, $L_2 = 2 \text{ mH}$, $M = 3 \text{ mH}$.

Step 2 – form the product of self-inductances: $L_1 L_2 = 8 \times 2 = 16 \text{ mH}^2$

Step 3 – take the square root: $\sqrt{L_1 L_2} = \sqrt{16} = 4 \text{ mH}$

Step 4 – divide the mutual inductance by that root: $k = \frac{3}{4}$

$$k = 0.75$$

Step 5 – validity check: 0.75 lies between 0 and 1, so it is a physically valid coupling.

Final Answer: $k = 0.75 \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q2](#)



Q3.

Solution

Concept – series-opposing coupled inductors: When the two coil fluxes oppose (series-opposing), the mutual term is subtracted: $L_{eq} = L_1 + L_2 - 2M$.

Step 1 – list the data: $L_1 = 5 \text{ H}$, $L_2 = 7 \text{ H}$, $M = 1.5 \text{ H}$.

Step 2 – add the self-inductances: $L_1 + L_2 = 5 + 7 = 12 \text{ H}$

Step 3 – form the mutual term: $2M = 2 \times 1.5 = 3 \text{ H}$

Step 4 – subtract the mutual term (opposing is –): $L_{eq} = 12 - 3$

$$L_{eq} = 9 \text{ H}$$

Step 5 – sanity check: Series-opposing must be less than the plain series sum of 12 H, and $9 < 12$, so the sign is right.

Final Answer: $L_{eq} = 9 \text{ H} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q3](#)

Q4.

Solution

Concept – resonant frequency of a series RLC: At resonance the inductive and capacitive reactances cancel, giving $\omega_0 = \frac{1}{\sqrt{LC}}$.

Step 1 – convert the data to base units: $L = 0.5 \text{ H}$

$$C = 200 \mu\text{F} = 200 \times 10^{-6} \text{ F}$$

Step 2 – form the product LC: $LC = 0.5 \times 200 \times 10^{-6}$

$$LC = 100 \times 10^{-6} = 1 \times 10^{-4}$$

Step 3 – take the square root: $\sqrt{LC} = \sqrt{1 \times 10^{-4}} = 1 \times 10^{-2}$

Step 4 – take the reciprocal: $\omega_0 = \frac{1}{1 \times 10^{-2}}$

$$\omega_0 = 100 \text{ rad/s}$$

Final Answer: $\omega_0 = 100 \text{ rad/s} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q4](#)



Q5.

Solution

Concept – quality factor of a series RLC : The sharpness of resonance is measured by $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$.

Step 1 – convert the data to base units: $R = 4 \, \Omega$, $L = 40 \, \text{mH} = 0.04 \, \text{H}$, $C = 100 \, \mu\text{F} = 100 \times 10^{-6} \, \text{F}$.

Step 2 – form the ratio L/C : $\frac{L}{C} = \frac{0.04}{100 \times 10^{-6}}$

$$\frac{L}{C} = \frac{0.04}{1 \times 10^{-4}} = 400$$

Step 3 – take the square root: $\sqrt{L/C} = \sqrt{400} = 20$

Step 4 – divide by the resistance: $Q = \frac{1}{4} \times 20$

$$Q = 5$$

Final Answer: $Q = 5 \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q5](#)

Q6.

Solution

Concept – power factor from the current angle: The power factor is the cosine of the phase angle between voltage and current, $\text{pf} = \cos \phi$, and it is lagging when the current lags the voltage.

Step 1 – identify the phase angle: $V = 100 \angle 0^\circ \, \text{V}$ and $I = 10 \angle -30^\circ \, \text{A}$, so the current lags the voltage by $\phi = 30^\circ$.

Step 2 – take the cosine of the angle: $\cos 30^\circ = \frac{\sqrt{3}}{2}$

Step 3 – evaluate: $\cos 30^\circ = 0.866$

Step 4 – state the sense: Because the current lags the voltage, the power factor is 0.866 lagging.

Why the other options are wrong:

- B, 0.5: this is $\cos 60^\circ$, the wrong angle.
- C, 1: unity would need $\phi = 0^\circ$ (a purely resistive load).
- D, 0.707: this is $\cos 45^\circ$, not $\cos 30^\circ$.

Final Answer: $\text{pf} = 0.866 \text{ lagging} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q6](#)



Q7.

Solution

Concept – magnitude of a series R - L impedance: The resistance and reactance add as perpendicular components, so $|Z| = \sqrt{R^2 + X_L^2}$.

Step 1 – list the data: $R = 6 \Omega$, $X_L = 8 \Omega$.

Step 2 – square each component: $R^2 = 6^2 = 36$

$$X_L^2 = 8^2 = 64$$

Step 3 – add the squares: $R^2 + X_L^2 = 36 + 64 = 100$

Step 4 – take the square root: $|Z| = \sqrt{100}$

$$|Z| = 10 \Omega$$

Step 5 – recognise the pattern: This is the 6–8–10 right triangle, confirming the result.

Final Answer: $|Z| = 10 \Omega \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q7](#)

Q8.

Solution

Concept – field of a long straight current-carrying wire: By Ampere's law the magnetic flux density around a long straight conductor is $B = \frac{\mu_0 I}{2\pi r}$.

Step 1 – list the data: $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$, $I = 5 \text{ A}$, $r = 0.1 \text{ m}$.

Step 2 – form the numerator $\mu_0 I$: $\mu_0 I = (4\pi \times 10^{-7}) \times 5 = 20\pi \times 10^{-7}$

Step 3 – form the denominator $2\pi r$: $2\pi r = 2\pi \times 0.1 = 0.2\pi$

Step 4 – divide (the π cancels): $B = \frac{20\pi \times 10^{-7}}{0.2\pi} = 100 \times 10^{-7}$

Step 5 – express in convenient units: $B = 1 \times 10^{-5} \text{ T} = 10 \mu\text{T}$

Final Answer: $B = 10 \mu\text{T} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q8](#)



Q9.

Solution

Concept – energy stored in an inductor: The energy held in the magnetic field of an inductor is $W = \frac{1}{2}LI^2$.

Step 1 – list the data: $L = 2 \text{ H}$, $I = 3 \text{ A}$.

Step 2 – square the current: $I^2 = 3^2 = 9 \text{ A}^2$

Step 3 – multiply by the inductance: $LI^2 = 2 \times 9 = 18$

Step 4 – take one-half: $W = \frac{1}{2} \times 18$

$W = 9 \text{ J}$

Final Answer: $W = 9 \text{ J} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q9](#)

Q10.

Solution

Concept – uniform field between parallel plates: For closely spaced parallel plates the field is uniform and equals the voltage divided by the gap, $E = \frac{V}{d}$.

Step 1 – convert the data to base units: $V = 100 \text{ V}$, $d = 2 \text{ mm} = 2 \times 10^{-3} \text{ m}$.

Step 2 – substitute into the field equation: $E = \frac{100}{2 \times 10^{-3}}$

Step 3 – divide the numbers: $E = \frac{100}{0.002} = 50000 \text{ V/m}$

Step 4 – express in kV/m: $E = 50 \text{ kV/m}$

Final Answer: $E = 50 \text{ kV/m} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q10](#)

Q11.

Solution

Concept – capacitance of a two-wire line: The capacitance between the two conductors of a single-phase line is $C_{ab} = \frac{\pi\epsilon_0}{\ln(D/r)}$.

Step 1 – list the data: $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$ and $\ln(D/r) = 1$.

Step 2 – substitute the logarithm: $C_{ab} = \frac{\pi\epsilon_0}{1} = \pi\epsilon_0$

Step 3 – multiply out: $C_{ab} = 3.1416 \times 8.854 \times 10^{-12}$

Step 4 – evaluate: $C_{ab} = 27.8 \times 10^{-12} \text{ F/m}$



Step 5 – express in picofarads: $C_{ab} = 27.8 \text{ pF/m}$

Final Answer: $C_{ab} \approx 27.8 \text{ pF/m} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q11](#)

Q12.

Solution

Concept – discrete linear convolution: The convolution sum is $y[n] = \sum_k x[k] h[n - k]$; each output sample gathers the products whose indices add up to n .

Step 1 – list the two sequences: $x[0] = 1, x[1] = 2, x[2] = 3$ and $h[0] = 1, h[1] = 1$.

Step 2 – write the terms contributing to $y[2]$ (indices k and $2 - k$): $y[2] = x[0]h[2] + x[1]h[1] + x[2]h[0]$

Step 3 – note that $h[2]$ does not exist (it is 0): $x[0]h[2] = 1 \times 0 = 0$

Step 4 – evaluate the remaining products: $x[1]h[1] = 2 \times 1 = 2$

$x[2]h[0] = 3 \times 1 = 3$

Step 5 – add the contributions: $y[2] = 0 + 2 + 3 = 5$

Final Answer: $y[2] = 5 \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q12](#)

Q13.

Solution

Concept – d.c. (zero-frequency) DFT coefficient: The first DFT sample is the plain sum of all the time samples, $X[0] = \sum_{n=0}^{N-1} x[n]$, because the twiddle factor is unity at $k = 0$.

Step 1 – list the sequence: $x[0] = 1, x[1] = 1, x[2] = 1, x[3] = 1$.

Step 2 – write the $X[0]$ sum: $X[0] = x[0] + x[1] + x[2] + x[3]$

Step 3 – add the samples: $X[0] = 1 + 1 + 1 + 1$

$X[0] = 4$

Step 4 – interpret: A constant sequence has all its energy at d.c., so only $X[0]$ is non-zero, consistent with the value found.

Final Answer: $X[0] = 4 \Rightarrow \boxed{\text{A}}$



Answer: (A) [Go Back to Q13](#)

Q14.

Solution

Concept – Nyquist sampling theorem: To reconstruct a band-limited signal without aliasing, it must be sampled at a rate of at least twice its highest frequency, $f_s \geq 2f_{max}$.

Step 1 – identify the highest frequency: $f_{max} = 4$ kHz.

Step 2 – apply the Nyquist criterion: $f_{s,min} = 2f_{max}$

Step 3 – substitute the value: $f_{s,min} = 2 \times 4$ kHz

$$f_{s,min} = 8 \text{ kHz}$$

Final Answer: $f_{s,min} = 8$ kHz $\Rightarrow$ **C**

Answer: (C) [Go Back to Q14](#)

Q15.

Solution

Concept – length of a linear convolution: Convolution of sequences of lengths L_1 and L_2 produces an output of length $L_1 + L_2 - 1$.

Step 1 – list the lengths: $L_1 = 6, L_2 = 8$.

Step 2 – add the lengths: $L_1 + L_2 = 6 + 8 = 14$

Step 3 – subtract one: $L = 14 - 1$

$$L = 13$$

Step 4 – sanity check: The output must be longer than either input, and $13 > 8$, which is consistent.

Final Answer: $L = 13$ samples $\Rightarrow$ **B**

Answer: (B) [Go Back to Q15](#)

Q16.

Solution

Concept – complex multiplications in a radix-2 FFT: A radix-2 FFT reduces the DFT cost from N^2 to $\frac{N}{2} \log_2 N$ complex multiplications.

Step 1 – list the transform size: $N = 8$.



Step 2 – form $N/2$: $\frac{N}{2} = \frac{8}{2} = 4$

Step 3 – form $\log_2 N$: $\log_2 8 = 3$

Step 4 – multiply the two factors: $\frac{N}{2} \log_2 N = 4 \times 3 = 12$

Step 5 – contrast with the direct DFT: A direct DFT would need $N^2 = 64$; the FFT's 12 shows the saving.

Final Answer: 12 complex multiplications $\Rightarrow$ D

Answer: (D) [Go Back to Q16](#)

Q17.

Solution

Concept – e.m.f. equation of a transformer: The r.m.s. induced e.m.f. in a winding is $E = 4.44 f N \phi_m$, where ϕ_m is the peak core flux.

Step 1 – list the data: $f = 50$ Hz, $N = 100$ turns, $\phi_m = 0.02$ Wb.

Step 2 – multiply the constant by the frequency: $4.44 \times 50 = 222$

Step 3 – multiply by the number of turns: $222 \times 100 = 22200$

Step 4 – multiply by the peak flux: $E = 22200 \times 0.02$

$$E = 444 \text{ V}$$

Final Answer: $E = 444 \text{ V} \Rightarrow$ D

Answer: (D) [Go Back to Q17](#)

Q18.

Solution

Concept – copper loss and the short-circuit test: The short-circuit test is done at rated current, so its input power equals the full-load copper loss. Because copper loss follows I^2 , at a load fraction x it becomes $P_{cu} = x^2 P_{cu, fl}$.

Step 1 – identify the full-load copper loss: $P_{cu, fl} = 250 \text{ W}$ (the SC test reading).

Step 2 – set the load fraction: Half load means $x = 0.5$.

Step 3 – square the load fraction: $x^2 = (0.5)^2 = 0.25$

Step 4 – scale the copper loss: $P_{cu} = 0.25 \times 250$

$$P_{cu} = 62.5 \text{ W}$$

Final Answer: $P_{cu} = 62.5 \text{ W} \Rightarrow$ B



Answer: (B) [Go Back to Q18](#)

Q19.

Solution

Concept – core loss and the open-circuit test: The open-circuit test applies rated voltage, so its input power is the core (iron) loss. Iron loss depends on voltage and frequency, *not* on load, so it stays constant as the load changes.

Step 1 – identify the core loss from the OC test: $P_{core} = 150 \text{ W}$ at rated voltage.

Step 2 – note the load dependence: Core loss is independent of the load current.

Step 3 – evaluate at half load: Since the supply voltage is unchanged, P_{core} at half load is still 150 W.

Step 4 – contrast with copper loss: Only the copper loss would fall with load; the iron loss does not.

Final Answer: $P_{core} = 150 \text{ W} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q19](#)

Q20.

Solution

Concept – rated current from the kVA rating: The apparent power fixes the current through $S = V I$, so $I = \frac{S}{V}$.

Step 1 – convert the rating to volt-amperes: $S = 10 \text{ kVA} = 10000 \text{ VA}$.

Step 2 – list the secondary voltage: $V_2 = 400 \text{ V}$.

Step 3 – divide to get the current: $I_2 = \frac{10000}{400}$

Step 4 – evaluate: $I_2 = 25 \text{ A}$

Final Answer: $I_2 = 25 \text{ A} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q20](#)

Q21.

Solution

Concept – transformer efficiency: Efficiency is output power divided by input power, where input is output plus the total loss: $\eta = \frac{P_{out}}{P_{out} + P_{core} + P_{cu}}$.

Step 1 – list the data: $P_{out} = 8000 \text{ W}$, $P_{core} = 120 \text{ W}$, $P_{cu} = 130 \text{ W}$.



Step 2 – add the losses: $P_{loss} = 120 + 130 = 250 \text{ W}$

Step 3 – form the input power: $P_{in} = 8000 + 250 = 8250 \text{ W}$

Step 4 – divide output by input: $\eta = \frac{8000}{8250}$

Step 5 – evaluate and convert to per cent: $\eta = 0.9697 = 96.97\%$

Final Answer: $\eta \approx 96.97\% \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q21](#)

Q22.

Solution

Concept – load for maximum efficiency: Maximum efficiency occurs when the variable copper loss equals the fixed iron loss. Setting $x^2 P_{cu, fl} = P_i$ gives the load

fraction $x = \sqrt{\frac{P_i}{P_{cu, fl}}}$.

Step 1 – list the data: $P_i = 200 \text{ W}$, $P_{cu, fl} = 800 \text{ W}$.

Step 2 – form the loss ratio: $\frac{P_i}{P_{cu, fl}} = \frac{200}{800} = 0.25$

Step 3 – take the square root: $x = \sqrt{0.25}$

$x = 0.5$

Step 4 – interpret: Maximum efficiency occurs at half (50%) of full load.

Final Answer: $x = 0.5 \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q22](#)

Q23.

Solution

Concept – slip and rotor speed of an induction motor: The synchronous speed is $N_s = \frac{120f}{P}$ and the rotor runs slower by the slip, $N = N_s(1 - s)$.

Step 1 – compute the synchronous speed: $N_s = \frac{120 \times 50}{6}$

$N_s = \frac{6000}{6} = 1000 \text{ rpm}$

Step 2 – form the running factor: $1 - s = 1 - 0.04 = 0.96$

Step 3 – multiply to get the rotor speed: $N = 1000 \times 0.96$

$N = 960 \text{ rpm}$

Step 4 – sanity check: The rotor speed must be just below the synchronous 1000



rpm, and $960 < 1000$, which is consistent.

Final Answer: $N = 960 \text{ rpm} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q23](#)

Q24.

Solution

Concept – short-circuit (fault) MVA: For a fault fed through a per-unit reactance, the fault level is $\text{MVA}_{\text{fault}} = \frac{\text{MVA}_{\text{base}}}{X_{pu}}$.

Step 1 – list the data: $\text{MVA}_{\text{base}} = 100$, $X_{pu} = 0.25$.

Step 2 – substitute into the fault-level equation: $\text{MVA}_{\text{fault}} = \frac{100}{0.25}$

Step 3 – evaluate the division: $\text{MVA}_{\text{fault}} = 400$

Step 4 – interpret: A smaller reactance would give a larger fault level; 0.25 pu yields 400 MVA.

Final Answer: $\text{MVA}_{\text{fault}} = 400 \text{ MVA} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q24](#)

Q25.

Solution

Concept – fault current from fault MVA: For a three-phase system the short-circuit current is $I_{sc} = \frac{\text{MVA}_{\text{fault}} \times 10^6}{\sqrt{3} V_L}$.

Step 1 – list the data: $\text{MVA}_{\text{fault}} = 400$, $V_L = 11 \text{ kV} = 11000 \text{ V}$.

Step 2 – form the denominator: $\sqrt{3} \times 11000 = 1.732 \times 11000 = 19052$

Step 3 – form the numerator: $400 \times 10^6 = 4 \times 10^8$

Step 4 – divide: $I_{sc} = \frac{4 \times 10^8}{19052}$

Step 5 – evaluate: $I_{sc} \approx 20990 \text{ A} \approx 21 \text{ kA}$

Final Answer: $I_{sc} \approx 21 \text{ kA} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q25](#)



Q26.

Solution

Concept – breaking capacity of a circuit breaker: The three-phase symmetrical breaking capacity is the apparent power at the interrupted current, $S = \sqrt{3} V_L I_{sc}$.

Step 1 – list the data: $V_L = 11 \text{ kV} = 11000 \text{ V}$, $I_{sc} = 20 \text{ kA} = 20000 \text{ A}$.

Step 2 – multiply voltage and current: $V_L I_{sc} = 11000 \times 20000 = 2.2 \times 10^8$

Step 3 – multiply by $\sqrt{3}$: $S = 1.732 \times 2.2 \times 10^8$

Step 4 – evaluate: $S = 3.81 \times 10^8 \text{ VA} = 381 \text{ MVA}$

Final Answer: $S \approx 381 \text{ MVA} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q26](#)

Q27.

Solution

Concept – changing the MVA base of a per-unit reactance: At the same voltage base a per-unit reactance scales directly with the MVA base, $X_{new} = X_{old} \times \frac{\text{MVA}_{new}}{\text{MVA}_{old}}$.

Step 1 – list the data: $X_{old} = 0.15 \text{ pu}$, $\text{MVA}_{old} = 50$, $\text{MVA}_{new} = 100$.

Step 2 – form the MVA ratio: $\frac{\text{MVA}_{new}}{\text{MVA}_{old}} = \frac{100}{50} = 2$

Step 3 – multiply: $X_{new} = 0.15 \times 2$

$X_{new} = 0.30 \text{ pu}$

Step 4 – interpret: Doubling the MVA base doubles the per-unit reactance, as found.

Final Answer: $X_{new} = 0.30 \text{ pu} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q27](#)

Q28.

Solution

Concept – three-phase symmetrical fault current in per-unit: For a bolted three-phase fault the per-unit current is the pre-fault voltage divided by the reactance, $I_f = \frac{E}{X}$.

Step 1 – list the data: $E = 1.0 \text{ pu}$, $X = 0.2 \text{ pu}$.

Step 2 – substitute into the fault equation: $I_f = \frac{1.0}{0.2}$

Step 3 – evaluate: $I_f = 5 \text{ pu}$



Step 4 – interpret: A 0.2 pu reactance permits five times rated current to flow during the fault.

Final Answer: $I_f = 5 \text{ pu} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q28](#)

Q29.

Solution

Concept – base impedance: For a chosen voltage and power base the base impedance is $Z_{base} = \frac{(kV_{base})^2}{\text{MVA}_{base}}$.

Step 1 – list the data: $kV_{base} = 220 \text{ kV}$, $\text{MVA}_{base} = 100$.

Step 2 – square the base voltage: $(220)^2 = 48400$

Step 3 – divide by the base MVA: $Z_{base} = \frac{48400}{100}$

Step 4 – evaluate: $Z_{base} = 484 \Omega$

Final Answer: $Z_{base} = 484 \Omega \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q29](#)

Q30.

Solution

Concept – charging current of a line's capacitance: The shunt capacitance of a line draws a charging current $I_c = V_{ph} \omega C$, where V_{ph} is the phase voltage and C the total per-phase capacitance.

Step 1 – find the total per-phase capacitance: $C = 0.02 \mu\text{F}/\text{km} \times 100 \text{ km} = 2 \mu\text{F} = 2 \times 10^{-6} \text{ F}$

Step 2 – find the angular frequency: $\omega = 2\pi f = 2\pi \times 50 = 314.16 \text{ rad/s}$

Step 3 – find the phase voltage: $V_{ph} = \frac{132000}{\sqrt{3}} = 76210 \text{ V}$

Step 4 – form the susceptance ωC : $\omega C = 314.16 \times 2 \times 10^{-6} = 6.283 \times 10^{-4} \text{ S}$

Step 5 – multiply by the phase voltage: $I_c = 76210 \times 6.283 \times 10^{-4}$

Step 6 – evaluate: $I_c \approx 47.9 \text{ A} \approx 48 \text{ A}$

Final Answer: $I_c \approx 48 \text{ A} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q30](#)



Q31.

Solution

Concept – Nyquist stability criterion: The criterion states $N = P - Z$, where N is the number of clockwise encirclements of -1 , P the open-loop right-half-plane poles, and Z the closed-loop right-half-plane poles. For stability we need $Z = 0$.

Step 1 – list what is given: The open-loop system has $P = 0$ right-half-plane poles.

Step 2 – impose stability: Stability requires $Z = 0$.

Step 3 – substitute into $N = P - Z$: $N = 0 - 0$

$$N = 0$$

Step 4 – interpret with the sketch: The Nyquist plot must *not* encircle -1 ; the sketch shows the locus staying clear of -1 , so the system is indeed stable.

Final Answer: $N = 0$ encirclements $\Rightarrow$ D

Answer: (D) [Go Back to Q31](#)

Q32.

Solution

Concept – gain margin: The gain margin is the reciprocal of the open-loop gain at the phase-crossover frequency, expressed in decibels: $GM = 20 \log_{10} \frac{1}{|G|}$.

Step 1 – list the data: $|G(j\omega_{pc})| = 0.25$.

Step 2 – take the reciprocal: $\frac{1}{|G|} = \frac{1}{0.25} = 4$

Step 3 – take the base-10 logarithm: $\log_{10} 4 = 0.602$

Step 4 – multiply by 20: $GM = 20 \times 0.602$

$$GM = 12.04 \text{ dB} \approx 12 \text{ dB}$$

Step 5 – interpret: A positive gain margin of 12 dB indicates a stable system with comfortable headroom.

Final Answer: $GM \approx 12 \text{ dB} \Rightarrow$ D

Answer: (D) [Go Back to Q32](#)



Q33.

Solution

Concept – derivative gain of a PID controller: Writing the PID law as $G_c = K_p \left(1 + \frac{1}{T_i s} + T_d s\right)$, the derivative-path gain is $K_d = K_p T_d$.

Step 1 – list the tuning constants: $K_p = 5$, $T_d = 0.1$ s.

Step 2 – form the product $K_p T_d$: $K_d = 5 \times 0.1$

Step 3 – evaluate: $K_d = 0.5$

Step 4 – note: The integral time $T_i = 0.5$ s sets the integral gain and does not enter the derivative gain.

Final Answer: $K_d = 0.5 \Rightarrow \boxed{C}$

Answer: (C) [Go Back to Q33](#)

Q34.

Solution

Concept – steady-state error of a type-0 system to a step: For a unit-step input the position error constant is $K_p = \lim_{s \rightarrow 0} G(s)$ and the steady-state error is $e_{ss} = \frac{1}{1 + K_p}$.

Step 1 – evaluate the position error constant: $K_p = \lim_{s \rightarrow 0} \frac{10}{s + 5} = \frac{10}{5} = 2$

Step 2 – substitute into the error formula: $e_{ss} = \frac{1}{1 + 2}$

Step 3 – add in the denominator: $e_{ss} = \frac{1}{3}$

Step 4 – evaluate: $e_{ss} = 0.333$

Step 5 – note the type: Since G has no pole at the origin it is type-0, so a finite step error is expected.

Final Answer: $e_{ss} = 0.333 \Rightarrow \boxed{B}$

Answer: (B) [Go Back to Q34](#)

Q35.

Solution

Concept – damping ratio from the characteristic equation: Comparing $s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$ with the given equation, first read off ω_n from the constant term, then ζ from the middle term.



Step 1 – read the constant term: $\omega_n^2 = 16$

Step 2 – take the square root: $\omega_n = \sqrt{16} = 4 \text{ rad/s}$

Step 3 – match the middle coefficient: $2\zeta\omega_n = 4$

Step 4 – solve for ζ : $\zeta = \frac{4}{2\omega_n} = \frac{4}{2 \times 4}$

Step 5 – evaluate: $\zeta = \frac{4}{8} = 0.5$

Step 6 – interpret: $\zeta = 0.5 < 1$, so the system is underdamped.

Final Answer: $\zeta = 0.5 \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q35](#)

Q36.

Solution

Concept – gain of a non-inverting amplifier: For an ideal op-amp in the non-inverting configuration the closed-loop gain is $\frac{V_o}{V_i} = 1 + \frac{R_f}{R_1}$.

Step 1 – list the data: $R_f = 90 \text{ k}\Omega$, $R_1 = 10 \text{ k}\Omega$.

Step 2 – form the resistor ratio: $\frac{R_f}{R_1} = \frac{90}{10} = 9$

Step 3 – add one: $\frac{V_o}{V_i} = 1 + 9$

Step 4 – evaluate: $\frac{V_o}{V_i} = 10$

Why the other options are wrong:

- B, 9: this is the inverting gain R_f/R_1 , which drops the “1+”.
- C, 0.1: this is R_1/R_f , the ratio inverted.
- D, 11: over-counts by adding an extra unit.

Final Answer: $\frac{V_o}{V_i} = 10 \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q36](#)



Q37.

Solution

Concept – reading a voltage on an oscilloscope: The peak-to-peak voltage equals the number of vertical divisions the trace spans multiplied by the vertical sensitivity, $V_{pp} = (\text{div}) \times (\text{V/div})$.

Step 1 – list the data: Vertical span = 4 divisions, sensitivity = 2 V/div.

Step 2 – multiply: $V_{pp} = 4 \times 2$

Step 3 – evaluate: $V_{pp} = 8 \text{ V}$

Step 4 – cross-check the amplitude: The amplitude is half of this, 4 V, and the RMS would be $4/\sqrt{2} = 2.83 \text{ V}$, all consistent.

Final Answer: $V_{pp} = 8 \text{ V} \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q37](#)

Q38.

Solution

Concept – measuring frequency on an oscilloscope: The period equals the horizontal divisions per cycle times the time base; the frequency is its reciprocal, $f = \frac{1}{(\text{div}) \times (\text{time/div})}$.

Step 1 – find the period: $T = 4 \text{ div} \times 0.5 \text{ ms/div}$

$$T = 2 \text{ ms} = 2 \times 10^{-3} \text{ s}$$

Step 2 – take the reciprocal: $f = \frac{1}{2 \times 10^{-3}}$

Step 3 – evaluate: $f = 500 \text{ Hz}$

Final Answer: $f = 500 \text{ Hz} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q38](#)

Q39.

Solution

Concept – flip-flops for a counter modulus: An n -bit counter has 2^n states, so the number of flip-flops needed for a modulus M is the smallest n with $2^n \geq M$.

Step 1 – state the requirement: $M = 10$, so we need $2^n \geq 10$.

Step 2 – test $n = 3$: $2^3 = 8 < 10$ (not enough).

Step 3 – test $n = 4$: $2^4 = 16 \geq 10$ (sufficient).



Step 4 – conclude: The smallest adequate count is $n = 4$ flip-flops.

Final Answer: $n = 4 \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q39](#)

Q40.

Solution

Concept – frequency division by a ripple counter: Each flip-flop of a binary ripple counter divides the frequency by 2, so an n -bit counter divides the clock by 2^n at its most-significant output.

Step 1 – list the data: $n = 3$ bits, clock = 8 kHz.

Step 2 – form the division factor: $2^n = 2^3 = 8$

Step 3 – divide the clock frequency: $f_{out} = \frac{8 \text{ kHz}}{8}$

Step 4 – evaluate: $f_{out} = 1 \text{ kHz}$

Final Answer: $f_{out} = 1 \text{ kHz} \Rightarrow \boxed{\text{A}}$

Answer: (A) [Go Back to Q40](#)

Q41.

Solution

Concept – hexadecimal to decimal conversion: Each hex digit carries a weight that is a power of 16; the value is $d_1 \times 16^1 + d_0 \times 16^0$, with $A_{16} = 10$.

Step 1 – identify the digits: $(2A)_{16}$ has $d_1 = 2$ and $d_0 = A = 10$.

Step 2 – weight the most-significant digit: $2 \times 16 = 32$

Step 3 – weight the least-significant digit: $10 \times 1 = 10$

Step 4 – add the two contributions: $32 + 10 = 42$

Final Answer: $(2A)_{16} = 42 \Rightarrow \boxed{\text{D}}$

Answer: (D) [Go Back to Q41](#)



Q42.

Solution

Concept – output of a buck converter: In continuous conduction the average output of a step-down converter is the input scaled by the duty ratio, $V_o = D V_s$.

Step 1 – list the data: $V_s = 48 \text{ V}$, $D = 0.25$.

Step 2 – multiply: $V_o = 0.25 \times 48$

Step 3 – evaluate: $V_o = 12 \text{ V}$

Step 4 – sanity check: A buck output must be below the input, and $12 < 48$, which is consistent.

Final Answer: $V_o = 12 \text{ V} \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q42](#)

Q43.

Solution

Concept – output of a boost converter: A step-up converter in continuous conduction produces $V_o = \frac{V_s}{1 - D}$.

Step 1 – list the data: $V_s = 20 \text{ V}$, $D = 0.5$.

Step 2 – form the factor $1 - D$: $1 - D = 1 - 0.5 = 0.5$

Step 3 – divide: $V_o = \frac{20}{0.5}$

Step 4 – evaluate: $V_o = 40 \text{ V}$

Step 5 – sanity check: A boost output must exceed the input, and $40 > 20$, which is consistent.

Final Answer: $V_o = 40 \text{ V} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q43](#)

Q44.

Solution

Concept – output of a buck-boost converter: The magnitude of the average output of a buck-boost converter is $|V_o| = V_s \frac{D}{1 - D}$.

Step 1 – list the data: $V_s = 24 \text{ V}$, $D = 0.6$.

Step 2 – form the factor $1 - D$: $1 - D = 1 - 0.6 = 0.4$

Step 3 – form the ratio $D/(1 - D)$: $\frac{0.6}{0.4} = 1.5$



Step 4 – multiply by the input: $|V_o| = 24 \times 1.5$

Step 5 – evaluate: $|V_o| = 36 \text{ V}$

Final Answer: $|V_o| = 36 \text{ V} \Rightarrow \boxed{\text{C}}$

Answer: (C) [Go Back to Q44](#)

Q45.

Solution

Concept – duty ratio of a buck converter: Since $V_o = D V_s$, the duty ratio needed for a target output is $D = \frac{V_o}{V_s}$.

Step 1 – list the data: $V_o = 5 \text{ V}$, $V_s = 20 \text{ V}$.

Step 2 – form the ratio: $D = \frac{5}{20}$

Step 3 – evaluate: $D = 0.25$

Step 4 – validity check: $0 < 0.25 < 1$, so it is a realisable duty ratio.

Final Answer: $D = 0.25 \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q45](#)

Q46.

Solution

Concept – duty ratio of a boost converter: From $V_o = \frac{V_s}{1 - D}$, the required duty ratio is found by rearranging to $1 - D = \frac{V_s}{V_o}$.

Step 1 – list the data: $V_s = 12 \text{ V}$, $V_o = 48 \text{ V}$.

Step 2 – form the voltage ratio: $\frac{V_s}{V_o} = \frac{12}{48} = 0.25$

Step 3 – set $1 - D$ equal to that ratio: $1 - D = 0.25$

Step 4 – solve for D : $D = 1 - 0.25$

Step 5 – evaluate: $D = 0.75$

Step 6 – sanity check: A large step-up ratio needs a high duty ratio, and 0.75 is consistent with a fourfold boost.

Final Answer: $D = 0.75 \Rightarrow \boxed{\text{B}}$

Answer: (B) [Go Back to Q46](#)



Answer Key

Q	Ans	Q	Ans	Q	Ans	Q	Ans	Q	Ans
1	A	2	B	3	D	4	A	5	C
6	A	7	C	8	C	9	D	10	C
11	D	12	A	13	A	14	C	15	B
16	D	17	D	18	B	19	B	20	C
21	D	22	B	23	A	24	B	25	A
26	A	27	C	28	D	29	A	30	C
31	D	32	D	33	C	34	B	35	B
36	A	37	D	38	A	39	B	40	A
41	D	42	B	43	C	44	C	45	B
46	B								

