

Electric Current

Rate of flow of charge across any cross-section of a conductor.

$$\bar{I} = dq / dt$$

<- instantaneous
<- current

Average current : $\bar{I}_{avg} = q / t$

SI unit : ampere (A) = C / s.

Dimensional formula : $[A] = [M^0 L^0 T^{-1} A]$

Direction Convention

Conventional current : direction of ~~electron~~ motion of positive charge.

Electron current : opposite to it.

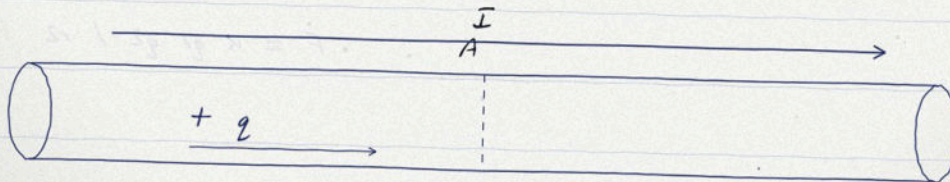


Fig. : charge crossing area A in time dt

Note : \bar{I} is scalar (algebraic ; sign tells direction).

Current in a Conductor

A metal has a sea of free electrons. They move in random directions with thermal speeds

10^5 m/s, colliding with the lattice.

No external $E \rightarrow$ no net current (vectors of v cancel out on average).

(a) No field - random

(b) With field $E \rightarrow$ drift

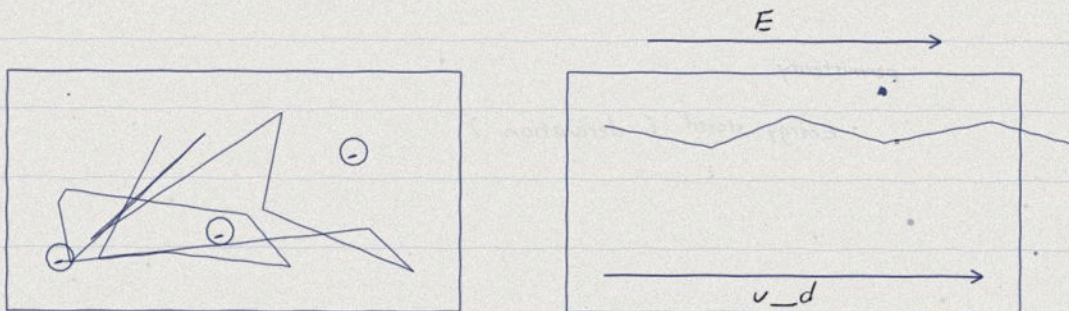


Fig. random motion vs. drift in an E field

Drift Velocity v_d

Average velocity acquired by free electrons in the direction opposite to E .

Typical magnitude : v_d a few mm/s (slow !), but bulb glows instantly because field travels at c .

Drift Velocity - Derivation

Apply E along the wire. Force on each free electron : $F = -eE$

$$a = -eE / m$$

<- acceleration

<- during free flight

Relaxation Time *

Average time between two successive

collisions of an electron with ions : T

(T denotes relaxation time ; 10^{-14} s)

Drift Velocity Formula

If v_i = random velocity of i -th electron just after a collision, and t_i = time elapsed since then, then velocity now =

$$v_i = v_i + a t_i$$

Average over all electrons : $\langle v \rangle = 0$,

$\langle t \rangle = T$ (relaxation time)

$$v_d = -eET / m$$

<- v_d opposite

<- to E

Magnitude : $v_d = eET / m$

Higher $E \rightarrow$ larger v_d ; higher $T \rightarrow$ larger v_d .

Current in terms of Drift Velocity

Setup

Conductor of cross-section A , length L .

n = number of free electrons per unit volume.

v_d = drift velocity (all electrons same v_d).

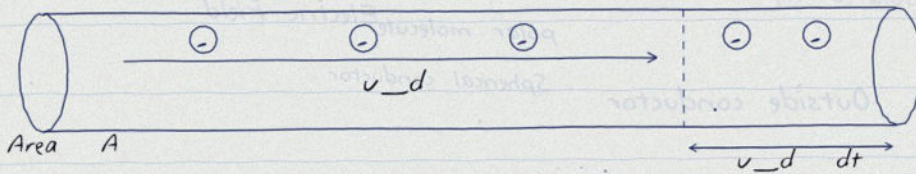


Fig. electrons cross A in time dt

Derivation

Volume of slice in time dt : $A v_d dt$

No. of electrons in slice : $n A v_d dt$

Charge crossing in dt : $e n A v_d dt$

So $I = dq / dt = n e A v_d$

$$I = n e A v_d$$

<- the famous
<- drift formula

Current density $J = I / A = n e v_d$

J is a vector : $J = n e v_d$ (along v_d).

SI unit of J : A / m^2 .

Ohm's Law

At constant physical conditions, the current through a conductor is directly proportional to the potential difference across its ends.

$$V = I R$$

<- R = constant of
<- proportionality

Resistance R

Ratio of V to I for that conductor.

SI unit : ohm (Greek capital omega).

$$1 \text{ ohm} = 1 \text{ V} / 1 \text{ A. Dim. : } [M L^2 T^3 A^{-2}]$$

Geometrical Formula

For a wire of length L and area A :

$$R = \rho L / A$$

<- rho = resistivity
<- material property

R depends on : material (rho), length L, area A, and temperature T.

Microscopic form of Ohm's law

$$J = \sigma E$$

<- sigma = conductivity
<- sigma = 1 / rho

(vector form ; valid at every point in conductor)

Origin of Resistivity

Combining $I = neA v_d$ with $v_d = eET/m$:

$$I = neA \cdot (eET/m) = ne^2 A E T / m$$

$$J = I / A = (ne^2 T / m) E$$

$$\sigma = ne^2 T / m$$

<- conductivity from
<- free-electron model

$$\rho = m / (ne^2 T)$$

<- rho is material
<- property

Important Observations

① $\rho \propto 1/n$ (more free electrons, lower resistivity). Metals : $n \approx 10^{28} / m^3$.

② $\rho \propto 1/T$; T decreases with rise in temperature for metals $\rightarrow \rho$ rises.

③ Drift current is what carries I ; the random part of velocity gives no net flow.

$$\text{Mobility : } \mu = v_d / E = e T / m$$

(μ denotes mobility ; SI unit : $m^2 V^{-1} s^{-1}$)

Limitations of Ohm's Law

$V = IR$ holds only for ohmic materials
(most metals at moderate I , const T).

Non-ohmic devices show 3 kinds of deviation :

(a) V not proportional to I

V - I curve is non-linear (e.g. GaAs).

Slope of V vs I is not constant ; $R = dV/dI$ depends on

*

(b) V depends on sign of I

Diode : large I when forward biased ,
tiny I when reverse biased.

(c) Multi-valued V for same I

Gas discharge tube , thyristor : same V can
give two different I values.

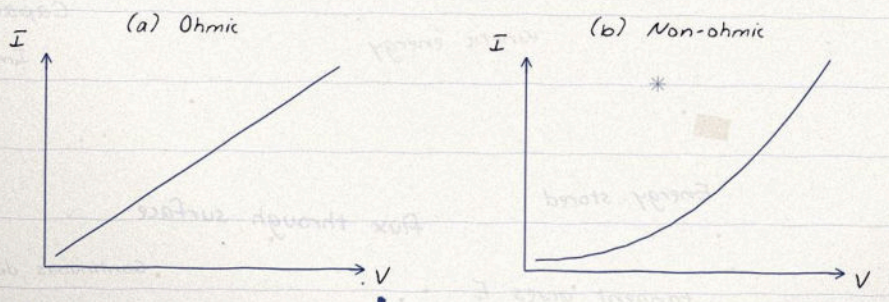


Fig. ohmic vs non-ohmic V - I behaviour

Resistivity of Materials

Materials are classified by ρ :

(1) Conductors (metals)

Many free electrons, low resistivity.

ρ 10^{-8} to 10^{-6} ohm . m

Examples : silver, copper, aluminium, gold, iron.

(2) Semiconductors

Intermediate : few charge carriers,

ρ 10^{-5} to 10^0 ohm . m

Examples : silicon, germanium.

ρ decreases with rising T (opposite of metals)

(3) Insulators

Very few free carriers, huge ρ .

ρ 10^8 to 10^{16} ohm . m

Examples : glass, rubber, wood, teflon.

Quick comparison

$\rho_{Cu} = 1.7 \times 10^{-8}$ ohm m

$\rho_{Si} = 2.3 \times 10^3$ ohm m (pure)

$\rho_{glass} = 10^{11}$ ohm m

(span of 25 orders of magnitude !)

Temperature Dependence of ρ

Over a small range :

$$\rho = \rho_0 [1 + \alpha (T - T_0)]$$

$\leftarrow \alpha = T$ - coeff
 \leftarrow of resistivity ($1/K$)

Sign of α

Metals : $\alpha > 0$ (ρ rises with T)

Reason : T decreases ; v_d falls \rightarrow ρ rises.

Semiconductors / insulators : $\alpha < 0$ *

Reason : more carriers excited at higher T .

Alloys (nichrome , manganin , constantan)

have very small $\alpha \rightarrow$ used as std resistors.


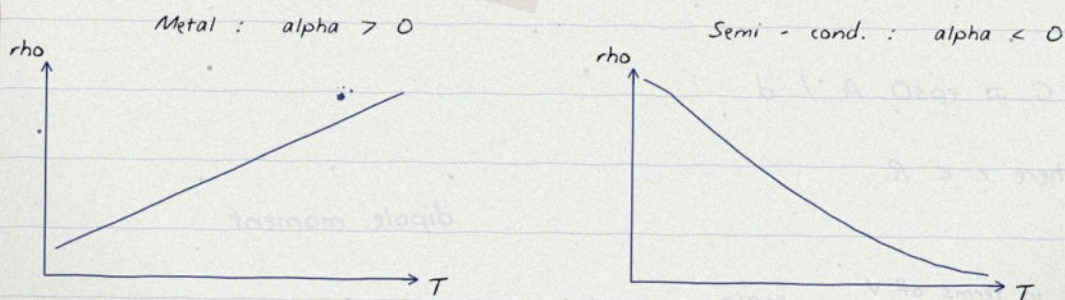


Fig. $\rho - T$ curves for metal & semiconductor

Resistors in Series

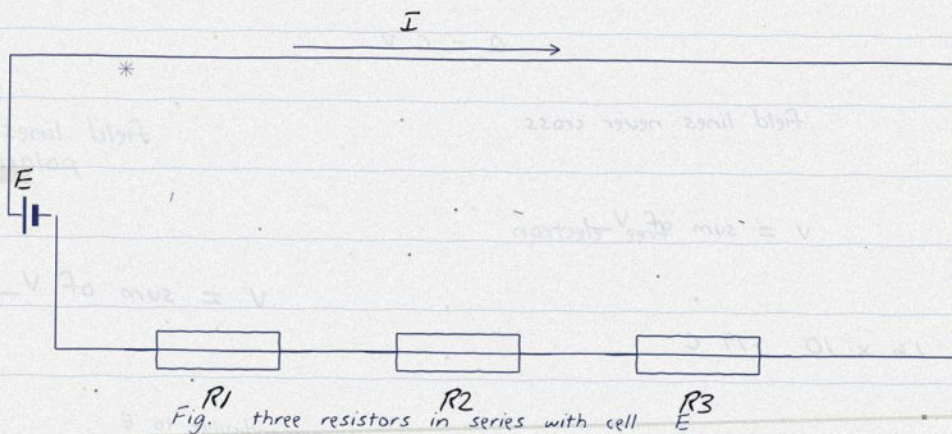End-to-end ; the same current I flows through every resistor.



Total potential drop

$$\begin{aligned} V &= V_1 + V_2 + V_3 \\ &= I R_1 + I R_2 + I R_3 \\ &= I (R_1 + R_2 + R_3) \end{aligned}$$

$$R_s = R_1 + R_2 + R_3 + \dots$$

$\leftarrow R_s \rightarrow$ any single
 $\leftarrow R$ in the chain


Two equal R in series $\rightarrow 2R$.

Use : when we want a larger R from given ones,
or to share V (potential ~~Drop~~ divider).

If one R burns / opens \rightarrow entire chain stops.

Resistors in Parallel

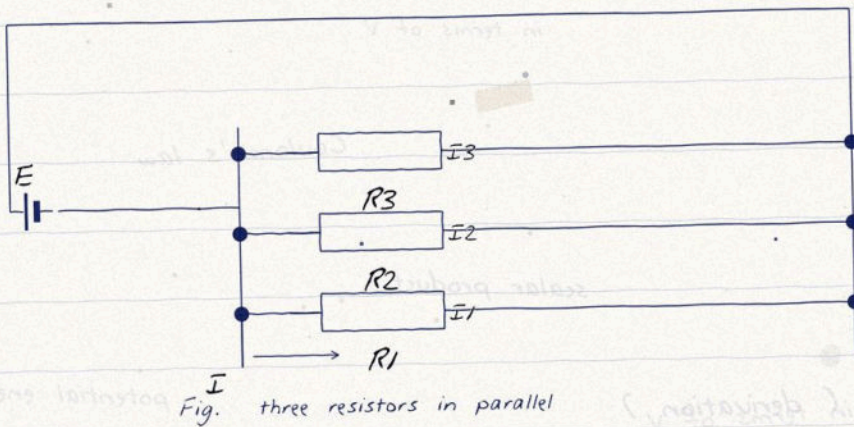All resistors share the same two nodes ;
potential difference V is the same across each.



Total current

$$I = I_1 + I_2 + I_3$$

$$= V/R_1 + V/R_2 + V/R_3$$

$$1/R_p = 1/R_1 + 1/R_2 + 1/R_3 + \dots$$

Two equal R in parallel $\rightarrow R/2$.

Use : when we want a smaller R , OR to share I
(current divider).

If one branch opens \rightarrow others still work fine.

Electrical Energy & Power

When charge q moves through potential drop V , work done $= qV$. If steady current I flows for time t , then $q = It$:

$$W = V I t$$

Power dissipated

$$P = W / t = V I$$

<- for any device
<- between its leads

Using $V = IR$, we get two more useful forms:

$$P = I^2 R$$

* <- Joule heating
<- in resistor

$$P = V^2 / R$$

<- useful when V
<- is fixed (mains)

Units of Energy

SI unit of energy: joule (J).

Commercial unit: kilowatt-hour (kWh).

$$1 \text{ kWh} = 1000 \text{ W} \times 3600 \text{ s} = 3.6 \times 10^6 \text{ J}$$

Power transmission

Send power as high V , low I to cut $I^2 R$ loss in transmission lines. Step up at source.

EMF & Internal Resistance

EMF (E)

Work done by the source in driving unit positive charge around the complete circuit ; equals open-circuit PD across cell terminals.

Internal Resistance r

Resistance of the electrolyte / cell material to its own current. Depends on size, ions, temperature.

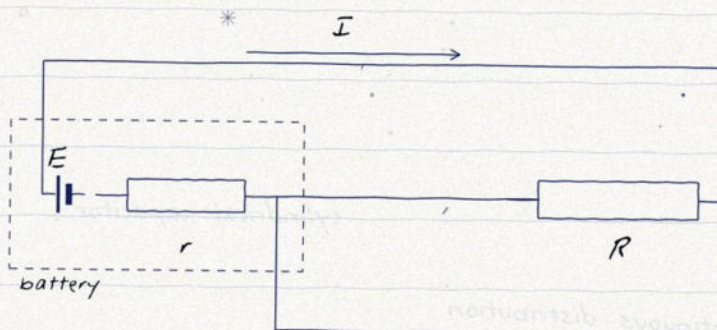


Fig. cell of EMF E , internal r , load R

Terminal Voltage V

$$V = E - I r$$

$\leftarrow V < E$ when
 $\leftarrow I$ flows out

Also $I = E / (R + r) \rightarrow V = E R / (R + r)$

Cells in Series

Two cells (E_1, r_1) and (E_2, r_2) connected so that + of one joins - of the other (aiding).

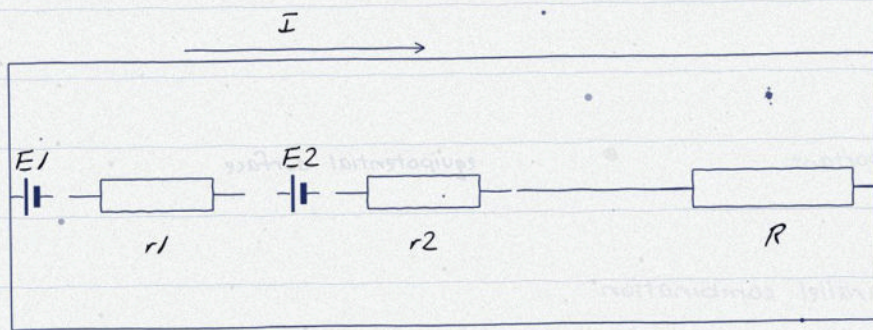


Fig. two cells aiding in series

Equivalent cell (aiding)

$$E_{eq} = E_1 + E_2$$

<- EMFs add

$$r_{eq} = r_1 + r_2$$

<- internal r add too

If one cell is reversed (opposing)

$$E_{eq} = E_1 - E_2$$

r_{eq} still = $r_1 + r_2$; use when higher EMF needed.

Cells in Parallel

Two cells (E_1, r_1) and (E_2, r_2) connected so that their + terminals are joined together and - to -.

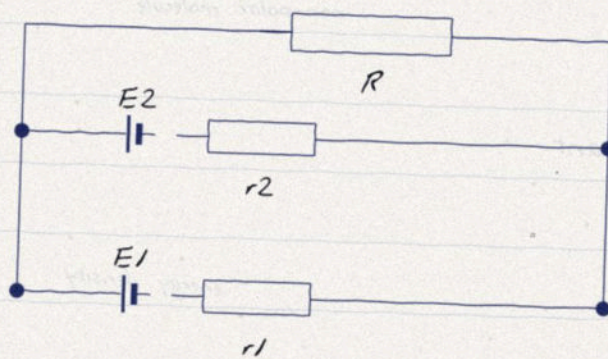


Fig. two cells in parallel with load R

Equivalent cell

$$E_{eq} / r_{eq} = E_1 / r_1 + E_2 / r_2$$

$$1 / r_{eq} = 1 / r_1 + 1 / r_2$$

<- internal r
<- add in parallel

Use parallel when : need large I , or backup in case one cell fails.

Equal cells : $E_{eq} = E$, $r_{eq} = r/n$ (n cells).

Kirchhoff's Junction Rule (KCL)

Statement

Algebraic sum of currents meeting at any junction (node) in a circuit is zero.

$$\text{Sum } I_{in} = \text{Sum } I_{out}$$

<- or $\text{Sum } I = 0$
<- with sign convention

Based on conservation of charge : no charge piles up at any junction in steady state.

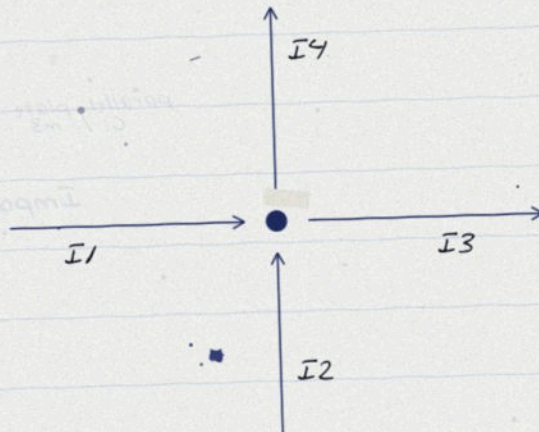


Fig. $I_1 + I_2 = I_3 + I_4$ at the junction

Sign convention

Currents entering the junction $\rightarrow +$

Currents leaving the junction $\rightarrow -$

Choose any direction for unknown I ; if the answer comes negative , true direction is opposite.

Kirchhoff's Loop Rule (KVL)

Statement

Algebraic sum of changes in potential around any closed loop in a network is zero.

$$\sum E = \sum I R$$

← EMFs balance
← IR drops

Based on conservation of energy : an electron returning to the same point has same PE.

Sign conventions

- ① Choose a loop direction (CW or CCW).
- ② Cross a resistor in direction of I : drop $-I R$. Against I : $+I R$.
- ③ Cross a cell from $-$ to $+$: gain $+E$. From $+$ to $-$: $-E$.

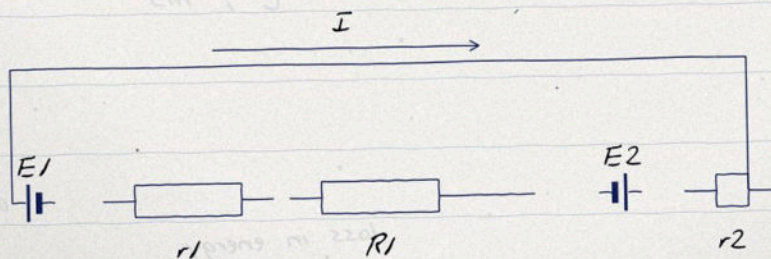


Fig. single-loop circuit ; apply $\sum E = \sum I R$

Wheatstone Bridge

Construction

Four resistors P , Q , R , S in a diamond.

Cell of EMF E between corners A and C ;

galvanometer G between corners B and D .

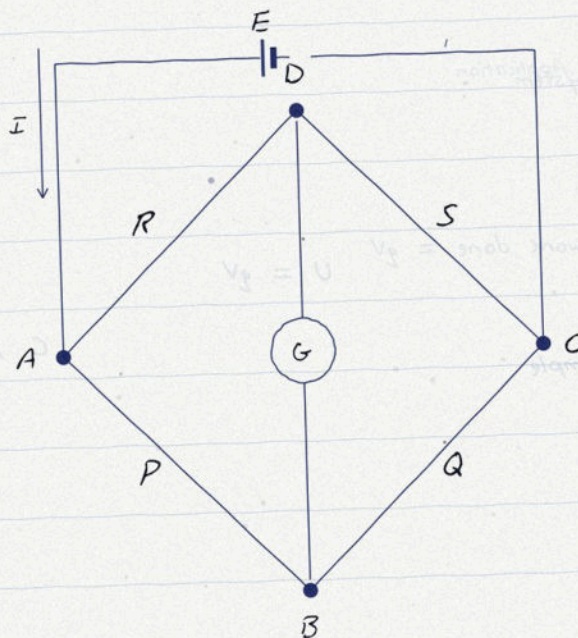


Fig. Wheatstone network ABCD with G across BD

Balance condition

$$P / Q = R / S$$

Wheatstone Bridge - Derivation

Balanced condition

At balance, galvanometer reads zero current.

$$\rightarrow V_B = V_D$$

Let I_1 flow through arm P (and Q),

I_2 flow through arm R (and S).

Loop A B D (KVL)

$$I_1 P = I_2 R \quad \dots (i)$$

Loop B C D (KVL)

$$I_1 Q = I_2 S \quad \dots (ii)$$

Divide (i) by (ii)

$$P / Q = R / S$$

<- Wheatstone
<- balance condition

Use of the bridge

- ① Measure an unknown resistance with three known ones (one variable).
- ② Bridge is most sensitive when all four arms are of comparable resistance.

If $P/Q \neq R/S$, a current flows through G.

Worked Example : KCL & KVL

Problem : In the loop below , find current I .

Take $E_1 = 10 \text{ V}$, $E_2 = 4 \text{ V}$, $r_1 = r_2 = 1 \text{ ohm}$,
 $R = 4 \text{ ohm}$. Cells aid each other.

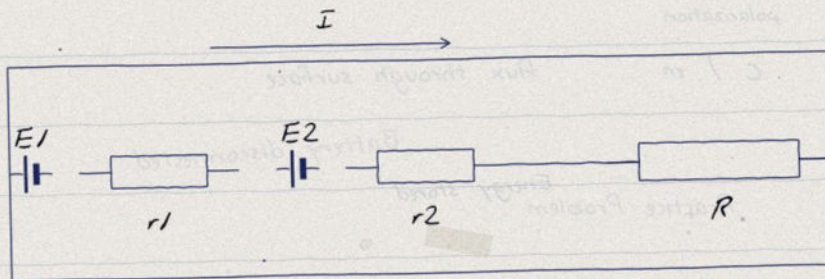


Fig. loop for the worked example

Solution (KVL clockwise)

$$\text{Sum of EMFs} - \text{Sum } I R = 0 :$$

$$(E_1 + E_2) - I(r_1 + r_2 + R) = 0$$

$$(10 + 4) - I(1 + 1 + 4) = 0$$

$$14 - 6I = 0 \rightarrow \cancel{I = 4 \text{ A}} \quad I = 7/3 \text{ A}$$

Power dissipated in R :

$$P = I^2 R = (7/3)^2 \cdot 4 = 21.8 \text{ W}$$

$$\text{Terminal V across } (E_1 + r_1) : V = 10 - (7/3)(1) = 7.67 \text{ V}$$

Worked Example : Wheatstone

Problem : In a balanced Wheatstone bridge ,
 $P = 10 \text{ ohm}$, $Q = 20 \text{ ohm}$, $R = 15 \text{ ohm}$.
Find the unknown resistance S .

Solution

Balance condition : $P / Q = R / S$

$$10 / 20 = 15 / S$$

$$1 / 2 = 15 / S$$

$$S = 30 \text{ ohm.}$$

Cross-check at junction

If I_1 flows in P - Q arm , I_2 in R - S arm :

$$I_1 P = I_2 R \quad \rightarrow \quad I_1 (10) = I_2 (15)$$

$$I_1 / I_2 = 3 / 2$$

$$\text{Also } I_1 Q = I_2 S \quad \rightarrow \quad 20 I_1 = 30 I_2$$

$$I_1 / I_2 = 3 / 2. \quad \text{Consistent !}$$

Tip : how to recognise balance

Galvanometer shows zero deflection on closing K_2
(galvanometer key) after K_1 (cell key).

If not balanced , adjust the variable resistance
until the galvanometer reads exactly zero.

Summary - Key Formulae

Definitions

$$I = dq / dt ; J = I / A ; V = I R$$

$$v_d = e E T / m \quad (\text{drift velocity})$$

$$I = n e A v_d ; m v = v_d / E$$

Material

$$R = \rho L / A ; \sigma = 1 / \rho$$

$$\sigma = n e^2 T / m ; \rho = m / (n e^2 T)$$

$$\rho = \rho_0 [1 + \alpha (T - T_0)]$$

Combinations

$$\text{Series} : R_s = R_1 + R_2 + \dots$$

$$\text{Parallel} : 1/R_p = 1/R_1 + 1/R_2 + \dots$$

Power

$$P = V I = I^2 R = V^2 / R$$

Cells

$$\text{Terminal } V : V = E - I r$$

$$\text{Series} : E_{eq} = \text{Sum } E ; r_{eq} = \text{Sum } r$$

$$\text{Parallel} : E / r_{eq} = \text{Sum } (E/r) ; 1/r_{eq} = \text{Sum } (1/r)$$

Kirchhoff & Wheatstone

$$\text{Sum } I = 0 \text{ (KCL)} ; \text{Sum } E = \text{Sum } I R \text{ (KVL)} ; P/Q =$$